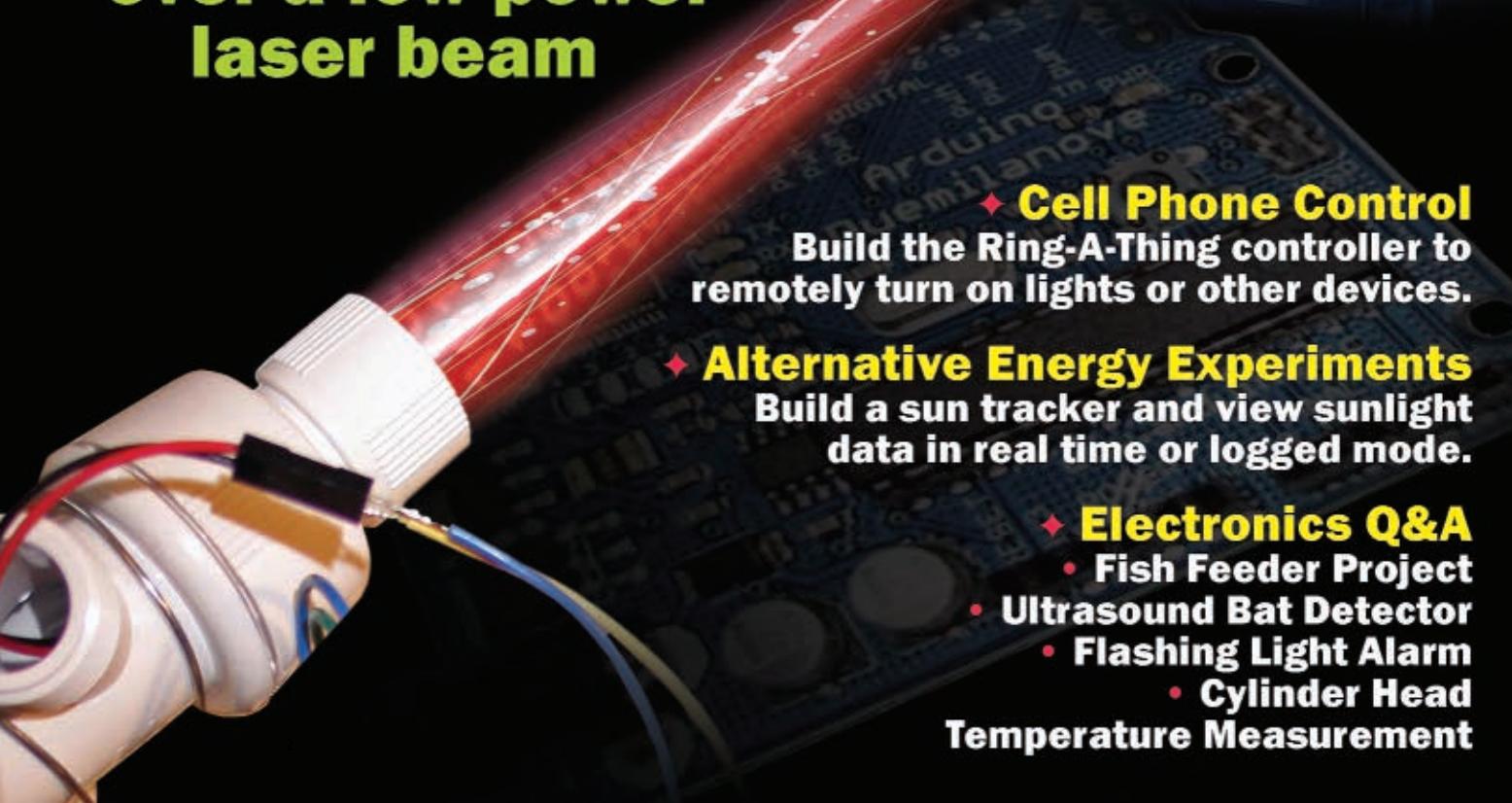


LASER POINTER Computer Link

Communicate
between computers
(or microcontrollers)
over a low power
laser beam

New!
Das BlinkenBoard Hack
Der Magnetfelder
Detektor



♦ **Cell Phone Control**
Build the Ring-A-Thing controller to
remotely turn on lights or other devices.

♦ **Alternative Energy Experiments**
Build a sun tracker and view sunlight
data in real time or logged mode.

♦ **Electronics Q&A**
• Fish Feeder Project
• Ultrasound Bat Detector
• Flashing Light Alarm
• Cylinder Head
Temperature Measurement



All displays shown are actual size

Serial**LCD**TM

NetMedia

BasicX.com

NetMedia Inc., 10940 N Stallard Pl, Tucson Arizona 85737 tel.520.544.4567 fax.520.544.0800 www.netmedia.com



Ruggedized PDA!



- ◆ Industrial-use PDA with ruggedized case!
- ◆ MEZ1000 by ACEECA runs Palm OS
- ◆ 16MB SDRAM, 4MB Flash RAM
- ◆ Measura Software Included
- ◆ 160 x 160 4-bit greyscale display
- ◆ USB, Serial, IrDA ports, 1900mAH Battery
- ◆ Original List price \$369!
- ◆ Includes cable, charger, CD, stylus
- ◆ New in OEM box, HSC 90-day warranty

HSC#22286 \$99.00

USB Speakerphone



- ◆ MV100 by MVox, talk free over the Internet!
- ◆ Compact and portable: perfect for travel!
- ◆ Powered by USB - no batteries needed
- ◆ Noise and echo canceling circuitry

HSC#22313 \$9.95

12VDC Inverters

These PowerStar Products inverters change 12 VDC into 115VAC for portable AC power anywhere! Perfect for camping, boating, field day! Brand new units in factory boxes.



- ◆ PowerStar POW-200 for 200 Watts
- ◆ Automobile Cigarette Lighter Cord built-in!

HSC#22241 \$19.50



- ◆ PowerStar UPG-400 for 400 Watts
- ◆ 11.5" x 3.125" x 3.125"

HSC#22242 \$24.50

Don't forget HSC!

Hey, remember us? We're still Silicon Valley's #1 source for electronic parts, tools, equipment, and one-of-a-kind specials! We've been buying and selling high-tech hardware since 1964, and we've been the go-to guys for technology tinkerers even before it was called "Silicon Valley". If you are in the SF Bay Area, you owe it to yourself to pay us a visit. See why savvy engineers have known us as a resource for decades!

Solar Science Fair Kit!

- ◆ Basic Solar Cell Array & demo parts
- ◆ Includes motor, wheels, fan, more!
- ◆ Can demonstrate series (for voltage) or parallel (for max. amperage) circuits
- ◆ Same panel as in Nuts & Volts Oct. Issue!

HSC#SOL021 \$15.95

Barcode Scanners!



- ◆ Metrologic Cubit IS6520 Series Scanner
- ◆ Mountable reader has 0-7 inch scan range
- ◆ OEM or Retail applications, fully automatic
- ◆ 80 char. data read, 20 scanlines
- ◆ Single cable interface to host
- ◆ Scans and decodes all standard barcodes
- ◆ Includes cable, manual, mounting bracket
- ◆ Datasheet details available on our website
- ◆ New in OEM box, HSC 90-day warranty

HSC#22283 USB \$95.00

HSC#22284 Serial \$89.00

Serial WiFi Bridge



- ◆ AirborneDirect Serial Ethernet Bridge
- ◆ 802.11b to RS232/485 serial port
- ◆ Plug & Play OEM product (no manual)
- ◆ Orig. List Price of \$195!
- ◆ Includes AC Adaptor, mounting cradle
- ◆ New in OEM box, HSC 30-day warranty


HSC#22296 \$49.00

Hobby Motors

Fabulous selection of small DC motors (and some AC, too!) for robotics, demonstrations, models, anywhere you need a small motor! This is a small sampling of our inventory:



Maxon 6VDC, 1" x 1.75"
HSC#21283 \$12.50

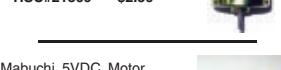

Canon 12VDC, 1" x 1"
5700rpm @ 140mA

HSC#21369 \$2.50



Mabuchi 5VDC Motor
Tiny! 1" long by .5" thick!

HSC#18136 \$1.95



Canon 12VDC, 2.3W
1.375" x 1.375"

HSC#21370 \$4.50

USB/Serial Thermal Printer



- ◆ Nanoptix "Spill Proof" Thermal Printer
- ◆ USB(mini) and Serial Ports built-in
- ◆ Small Footprint! 7.5" x 5.25"
- ◆ 203 dpi print density, 40 char. width
- ◆ Windows drivers available
- ◆ Includes setup guide, AC Adap.
- ◆ New in OEM box, HSC 30-day warranty

HSC#22295 \$95.00

1U Server Supply



- ◆ EMACS MPW-6200F Supply, 185-200W
- ◆ 5V @ 16A, 12V @ 7A, 3.3V @ 14A, also has -5V, -12V and +5VSB outputs
- ◆ New, 30-day HSC Warranty

HSC#21474 \$17.50

Helping Hands!



- ◆ Useful bench-top stand holds your work
- ◆ Magnifier lets you see smallest details
- ◆ LED Illuminator lights your way!

HSC#TLS021 \$11.50

HSC Exclusive -- Pixie2!

- ◆ Tiny QRP Xcvr rig! 200-300 mW out
- ◆ Kit incl. all board-mounted parts
- ◆ Use 'walkman' phones
- ◆ **QRP crystal pack special!**
Finally!...80, 40, 30, 20, 17, 15 & 10 meter calling freqs.

HSC#KIT240 (Pixie 2) \$9.95

HSC#80929 (xtal pack) \$14.95

12 VDC at 8.4 Amps



- ◆ Compact power supply by Mean Well
- ◆ Overall length 8.75", 2.5" x 1.25" high
- ◆ New in manufacturer plain white box

HSC#22208 \$14.95

Special Bargains!!



Mueller Test Probe
to Banana (Blue)
HSC#80912 \$1.95



Ferrite Filter, Clamp-on
HSC#18370 \$1.95



12VDC Adapt., 3.3A
HSC#21375 \$12.50



SMA-SMA, 10"
Teflon Coax
HSC#21970 \$9.75



SMA-SMA, 11"
Semi-rigid Coax
HSC#21290 \$9.50



DMM Probe Set
HSC#21542 \$7.95



Vactrol VTL3A47
Opto Module, 12V
HSC#1507 \$1.50



Heimann Pyrosensor
HSC#22268 \$1.95



Pressure Transducer
Honeywell 26PCPDFS6G
HSC#21066 \$4.95




1-Watt White LED
HSC#LED016 \$4.50



7.5" Flexi Antenna
with Mini-UHF Conn.
HSC#18845 \$7.95



DSL Line Filter
HSC#20070 \$2.95

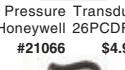

Auto Cig. Lighter Cord
HSC#21438 \$1.95



12VDC Adapt., 5A
HSC#22285 \$14.95



Palm Treo 300
CDMA Module
HSC#22037 \$2.95



Toroidal Transformer
120VAC - 3.7VAC
HSC#21848 \$6.50

You can get more info about any of these items on our website!

HSC Electronic Supply

2 Retail/Wholesale Locations:

Main Office - Mail Orders...

3500 Ryder St. Santa Clara, CA 95051

Phones:

Santa Clara 1-408-732-1573

Rohnert Park 1-707-585-7344

Silicon Valley's Electronic Marketplace

Since 1964!...
Order Toll-Free: 1-800-4-HALTED (442-5833)
or...ONLINE, AT: www.halted.com

Look for us on...





seller ID:
hscelectronicsupply



Terms: Some quantities limited; all items are subject to prior sale. **Minimum order: \$10.00 plus shipping.** Orders under \$20.00 subject to \$5.00 handling fee, in addition to shipping. All orders shipped by UPS Surface unless otherwise specified. \$9.00 UPS charge added for COD. Visit our website for detailed information on domestic and international shipping methods.

Are you up for a challenge?

What is
the missing
component?

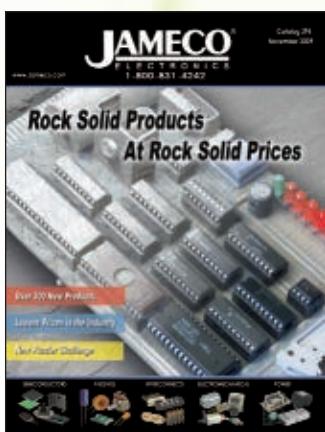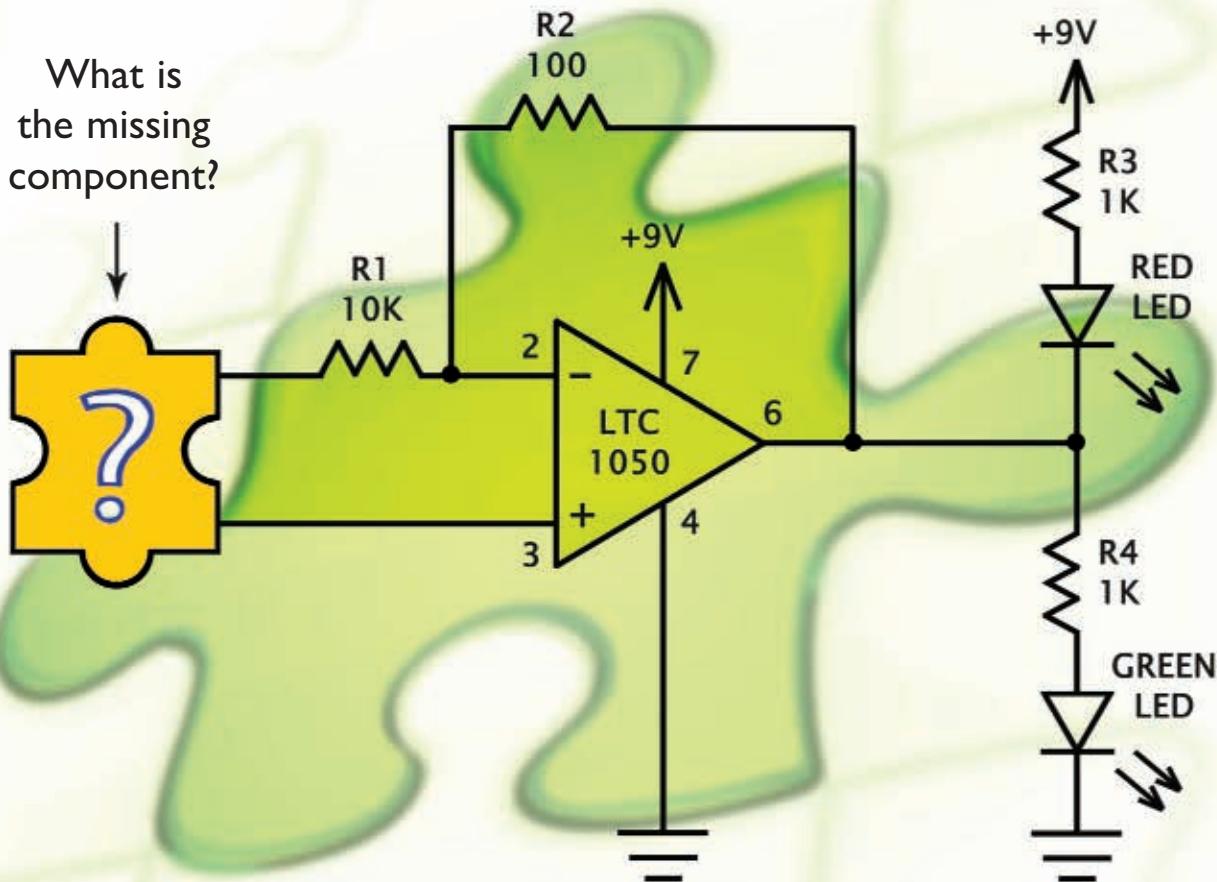

Industry guru Forrest M. Mims III has created a stumper. Video game designer Bob Wheels needed an inexpensive, counter-clockwise rotation detector for a radio-controlled car that could withstand the busy hands of a teenaged game player and endure lots of punishment. Can you figure out what's missing? Go to www.jameco.com/untangle to see if you are correct and while you are there, sign-up for our free full color catalog.

JAMECO
ELECTRONICS
1-800-831-4242

60 MHz - 1 GHz Starting from \$1,000



Experience the New LeCroy Oscilloscopes

Debug, verify, characterize, troubleshoot, analyze — oscilloscopes do it all, but LeCroy's breakthrough oscilloscopes do more. More measurements, more math, and more time-saving tools to easily make measurements in even the most challenging situations.

LeCroy

To learn more about LeCroy's full line of oscilloscopes, including the 30 GHz WaveMaster 8 Zi, the world's fastest real-time oscilloscope, visit www.lecroy.com or call 1-800-5-LeCroy



Page 40

Columns

10 TechKnowledgey 2009

Events, Advances, and News

Topics covered include tapping tree power, a dual monitor laptop, subminiature pushbutton switch, plus other stuff.

14 The Spin Zone

Adventures in Propeller Programming

Do it up with DMX.

20 Near Space

Approaching the Final Frontier

A near space environment chamber update.

28 Q & A

Reader Questions Answered Here

Fish feeder project, ferrite core search, flashing light alarm, plus more.

49 The Design Cycle

Advanced Techniques for Design Engineers

Take an IO-Warrior into your next embedded battle.

56 Getting Started With PICs

The Latest in Programming Microcontrollers

Eight-pin projects.

61 Personal Robotics

Understanding, Designing & Constructing Robots

Persistence pays off when dealing with problematic projects.

67 Smiley's Workshop

An AVR C Programming Series

Typing up some loose Arduino ends.

Projects & Features

34 Computer to Computer Link Using Laser Pointers

Establish serial communications between computers or microcontrollers over low power laser beams.

■ By Ed Ringel

40 Phone Ring-A-Thing Control

Use your cell phone and this device as a receiver/decoder system to perform remote functions.

■ By John F. Mastromoro

44 Experiments with Alternative Energy

Learn the fundamentals of renewable energy through this educational series. This month: Build a Double Wide Sun Tracker.

■ By John Gavlik



Page 44



Page 20



Page 10

Departments

08 DEVELOPING

72 NV WEBSTORE

PERSPECTIVES

76 CLASSIFIEDS

32 NEW PRODUCTS

78 TECH FORUM

33 SHOWCASE

81 AD INDEX

66 ELECTRO-NET

Nuts & Volts (ISSN 1528-9885/CDN Pub Agree #40702530) is published monthly for \$26.95 per year by T & L Publications, Inc., 430 Princeland Court, Corona, CA 92879. PERIODICALS POSTAGE PAID AT CORONA, CA AND AT ADDITIONAL MAILING OFFICES. POSTMASTER: Send address changes to **Nuts & Volts, P.O. Box 15277, North Hollywood, CA 91615** or Station A, P.O. Box 54, Windsor ON N9A 6J5; cpcreturns@nutsvolts.com.


A Low Cost Solution for
Industrial Serial to Ethernet
with Digital I/O and Analog to Digital Converters

Hardware Features

- Two TTL serial ports
- 10/100 Mbps Ethernet
- Up to 10 digital I/O
- Four 12-bit A/D converters
- Operating temperature -40 to 85 C
- Dimensions: 1.2" x 2"
- 32-bit performance

Software Features

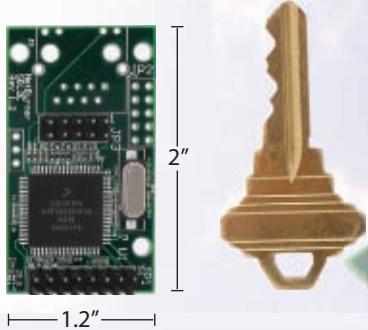- No programming required
- TCP / UDP / Telnet / HTTP modes
- DHCP / static IP support
- Web-based configuration



\$19.95
Qty. 1000

The all-new
NetBurner SBL2e
INDUSTRIAL SERIAL TO ETHERNET SOLUTION

A NetBurner Complete Hardware & Software Solution



Board Part Number | SBL2e-200IR
Information and Sales | sales@netburner.com
Web | www.netburner.com
Telephone | 1-800-695-6828





by Bryan Bergeron, Editor

DEVELOPING PERSPECTIVES

Speaker Break-In

Although I like to keep up with the latest innovations in electronics, my personal taste is toward vintage tube amps and musical instruments. I rarely take out the plastic for a new model of anything. However, I was checking out a new 100W tube amp recently and I asked for a demo. The sound was surprisingly harsh to my ears.

The salesperson's response was that this was a new floor model and that the speakers hadn't been broken in yet. Not only that, the speaker cables and the power cord were new, as well. He was confident that it would take about 30 hours of continuous use to burn in the cables, and perhaps double that for the speaker to reach "full fidelity."

This wasn't the first time I'd heard about breaking in speakers, but it was a first for the cables and power cord. When I expressed doubt about the speaker cables,

he showed me a national audiophile magazine with ads from companies selling pre-broken in audio cables. The more expensive cables were broken in 100 hours or more. According to the full page ads, both the insulation and copper wires require breaking in, again to reach "full fidelity." I thanked the well-meaning salesperson and headed home to do a little research.

It turns out that some — but not all — high-end speaker manufacturers recommend breaking in speakers. For example, Celestion (professional.celestion.com) — which manufactures high-end speakers for guitar amplifiers — recommends breaking in speakers. They suggest warming up a speaker and then playing 10-15 minutes at full volume to get it up to spec in the shortest time. Some boutique amplifier manufacturers include burn-in as part of their production process.

Breaking in a speaker makes sense, given that it's an electromechanical device. I can understand the need to get things moving to loosen up the cloth and other materials. Even so, there is no universal consensus that breaking in a speaker is needed or that it even works.

If you check the blogs, you'll see that a common perception is that the break-in period is the manufacturer's ploy to get customers used to their speakers so they won't return them. So, as far as speakers go, I'm leaning toward the break-in side.

However, I put the concept of cable break-in in the same category as multi-dimensional time travel with a phone booth. I've never seen a rational explanation for breaking in speaker cables, much less power cords. And yet, there are businesses that advertise on the web offering break-in services for your high-end cables.

For only \$39 per cable, you and your family can avoid the inconvenience of breaking in your own. Or, another company will sell you a cable cooker so that you can break in and periodically recondition your cables in the comfort of your own home.

I have no problem with someone trying to make a living by offering products and services that, while questionable, don't actively harm anyone. However, it's a disservice to well-meaning salespeople and the general public to popularize voodoo electronics.

In pulling together the articles for *Nuts & Volts*, we do our best to validate the science behind each article. But we also rely on you, the reader, to take an active role in commenting on our content — positively or negatively. The laws of physics won't be changed by group consensus, but opinions and perspectives can be shifted in the right direction. **NV**



PCBCORE
PCBCORE

China PCB Supplier (Prototype thru Production)

- ✓ 1-layer up to 30-layer
- ✓ Cost and quality
- ✓ On time delivery
- ✓ Dedicated service
- ✓ Instant Online Quote & Order
..... Day and Night

**No minimum quantity – 1 piece is welcome
Check our low price and save big \$\$\$...**

86(571)86795686 sales@pcbc.com
www.pcbc.com

NUTS AND VOLTS

Published Monthly By

T & L Publications, Inc.

430 Princeland Ct.

Corona, CA 92879-1300

(951) 371-8497

FAX (951) 371-3052

Webstore orders only 1-800-783-4624

www.nutsvolts.com

Subscriptions

Toll Free 1-877-525-2539

Outside US 1-818-487-4545

P.O. Box 15277

North Hollywood, CA 91615

FOUNDER/ASSOCIATE PUBLISHER

Jack Lemieux

PUBLISHER

Larry Lemieux

publisher@nutsvolts.com

ASSOCIATE PUBLISHER/ VP OF SALES/MARKETING

Robin Lemieux

display@nutsvolts.com

EDITOR

Bryan Bergeron

techedit@nutsvolts@yahoo.com

CONTRIBUTING EDITORS

Jeff Eckert	Russ Kincaid
Vern Graner	Fred Eady
Joe Pardue	John Gavlik
Ed Ringel	John Mastromoro
Chuck Hellebuyck	Jon Williams
L. Paul Verhage	

CIRCULATION DIRECTOR

Tracy Kerley

subscribe@nutsvolts.com

SHOW COORDINATOR

Audrey Lemieux

MARKETING COORDINATOR WEBSTORE

Brian Kirkpatrick

sales@nutsvolts.com

WEB CONTENT

Michael Kaudze

website@nutsvolts.com

ADMINISTRATIVE ASSISTANT

Debbie Stauffacher

PRODUCTION/GRAFICS

Shannon Christensen

Copyright © 2009 by T & L Publications, Inc.

All Rights Reserved

All advertising is subject to publisher's approval. We are not responsible for mistakes, misprints, or typographical errors. *Nuts & Volts Magazine* assumes no responsibility for the availability or condition of advertised items or for the honesty of the advertiser. The publisher makes no claims for the legality of any item advertised in *Nuts & Volts*. This is the sole responsibility of the advertiser. Advertisers and their agencies agree to indemnify and protect the publisher from any and all claims, action, or expense arising from advertising placed in *Nuts & Volts*. Please send all editorial correspondence, UPS, overnight mail, and artwork to: 430 Princeland Court, Corona, CA 92879.



Printed in the USA on SFI & FSC stock.

Enter into the world of PICs & Programming with this great combo!

What's an Oomlout?

a) The title for that independant film you could never quite figure out.

b) That hot new dance from the Caribbean.

You get funny looks, but you know you look cool.

c) Some dudes with a laser-cutter and an unhealthy Arduino obsession.

d) Something that'd be pretty tasty on a taco.


e) What the Ooml wants after you let it in.

f) All of the above.

C'mon, didn't you learn *anything* in school? Always answer "C!"

Solarbotics is working with Oomlout to bring simple hands-on Arduino training to your bench. Lay the template down, hook it up, and see what makes Arduino so great!

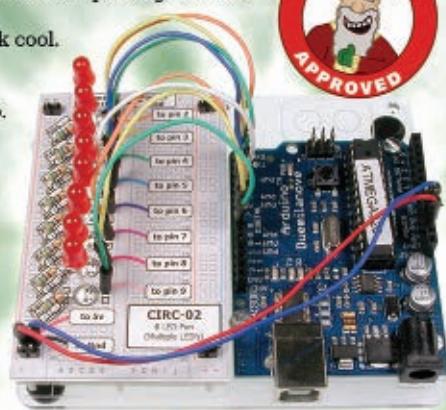Come see our Oomlout/Arduino bundles at www.solarbotics.com



SOLARBOTICS®

PS- If you chose f), I'd LOVE to see your thought process.



Full Speed

It writes your USB Code!

NEW! HIDmaker FS for Full Speed FLASH PIC18F4550

Creates complete PC and Peripheral programs that talk to each other over USB. Ready to compile and run!

- Large data Reports
- 64,000 bytes/sec per Interface
- Easily creates devices with multiple Interfaces, even multiple Identities!
- Automatically does MULTITASKING
- Makes standard or special USB HID devices

NEW! "Developers Guide for USB HID Peripherals" shows you how to make devices for special requirements.

Both PC and Peripheral programs understand your data items (even odd sized ones), and give you convenient variables to handle them.

PIC18F Compilers: PICBASIC Pro, MPASM, C18, Hi-Tech C.

PIC16C Compilers: PICBASIC Pro, MPASM, Hi-Tech C, CCS C.

PC Compilers: Delphi, C++ Builder, Visual Basic 6.


HIDmaker FS Combo: Only \$599.95



DOWNLOAD the HIDmaker FS Test Drive today!

www.TraceSystemsInc.com

301-262-0300

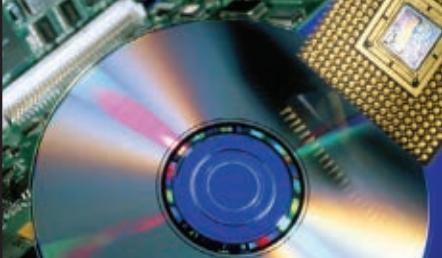

■ BY JEFF ECKERT

ADVANCED TECHNOLOGY

GaN + Si HYBRID CHIPS COMING



■ The hybrid chip under development at MIT.

It's no secret that we're approaching a dead end in terms of how small we can downsize silicon and, in fact, some other materials offer better performance. But the industry has spent billions of dollars on silicon technology and isn't overly eager to start over with something else. An obvious solution would be to combine different but complementary semiconductor materials on a single chip, but despite decades of research no one has been able to do it — until now. Apparently, MIT (www.mit.edu) researchers have come up with a solution that could help overcome some of the size and speed barriers faced by contemporary silicon technology.

Whereas you can easily put a billion transistors on a silicon chip, the technology for similar integration with other materials does not exist. It turns out that perhaps only five to 10 percent of the transistors are involved in computations and need to run at maximum speed; speed isn't so critical for the others, e.g., ones that store information. So, if you could piggy-back the faster, more exotic materials on top of silicon, you could have the best of both worlds.

Enter Prof. Tomas Palacios and

grad student Will Chung, who have created a silicon/gallium nitride hybrid chip, as described in the October issue of the IEEE journal *Electron Device Letters*. Instead of trying to grow the high performance material on top of a silicon chip as others have attempted, they embedded a GaN layer into a standard silicon substrate. This produces a faster chip that is also highly efficient — having most of the transistors operate at slower speeds minimizes power consumption. Best of all, the chips can be manufactured using standard commercial silicon technology. According to one analyst, the concept could "enable a new class of high performance, mixed signal, and digitally controlled RF circuits for use in a wide range of Department of Defense and commercial applications." In addition, the technology may be applicable to things like hybrid chips that combine lasers and electronic components on a single chip and energy-harvesting devices that can use ambient pressure and vibrations to produce enough power to run the silicon components. So far, the researchers have been able to make chips that are only about one square inch in size, so a challenge is to find a way to scale it up to match the eight- and 12-inch wafers used in conventional chip manufacture. In addition, they need to work on issues of device reliability and thermal management in the GaN transistors. Nevertheless, they hope to have it ready for commercialization within about two years.

TAPPING TREE POWER

In a development likely to make tree huggers apoplectic, some folks from the University of Washington (www.washington.edu) have figured

out a way to power (very) small electronic devices from trees, according to an article recently published in the *IEEE Transactions on Nanotechnology*. "As far as we know, this is the first peer-reviewed paper of someone powering something entirely by sticking electrodes into a tree," said co-author Babak Parviz, a UW associate professor of electrical engineering. Inspired by an earlier MIT study revealing that plants generate up to 200 mV when one electrode is plugged into the plant and the other into the soil, Parviz and co-author Carlton Himes spent the summer poking nails in trees in search of promising specimens. In the process, they discovered that bigleaf maples generate a steady stream of up to a few hundred millivolts. The next step was to have another co-author, Brian Otis, build a boost converter that stores incoming voltage until it can be discharged at an output of 1.1V — enough to run low power sensors.

Note that the tree power concept is not the same thing as the "potato effect," in which a current flow is created by a chemical reaction on two different metals. The tree power setup uses the same metal for both electrodes. So, how does it work one might ask? "It's not

■ This custom circuit collects and stores enough power from trees to run a low power sensor.



PHOTO COURTESY OF DUSTIN SCHROEDER, UNIVERSITY OF WASHINGTON.

exactly established where these voltages come from," admitted Parviz. "But there seems to be some signaling in trees, similar to what happens in the human body but with slower speed. I'm interested in applying our results as a way of investigating what the tree is doing. When you go to the doctor, the first thing they measure is your pulse. We don't really have something similar for trees." In terms of practical applications, tree power is unlikely to intrude into the realm of solar power, but it provides a low cost option for powering sensors that monitor environmental conditions. In fact, the concept has already been patented by Voltree Power LLC (www.voltreepower.com). Their first tree-powered product is the Early Wildfire Alert Network (EWAN), consisting of thousands of humidity and temperature sensor nodes distributed over remote forests.

COMPUTERS AND NETWORKING

DUAL MONITOR LAPTOP

Sometime between now and Christmas, a new laptop from a



■ The Spacebook dualscreen laptop, designed for high-end graphics users.

new source — gScreen Computer Corp. (www.gscreencorp.com) — is scheduled to hit the market. Based in Anchorage, the company has been around since 2003 but is only now coming out with its first hardware product. This isn't the first dual screen laptop to emerge, but it is the first one focused primarily on the needs of filmmakers, photographers, video and graphics designers, and CAD engineers. According to the company, "We do not yet know the exact release date, price, or specs that will be available on the first Spacebook model. We do know the specs that we are planning at the current time, but those can change and will solidify when we go into production at the end of 2009."

Some specs are available though, and both 16 inch and 17 inch models will be in the initial offering, with smaller ones to follow. Features include an Intel Dual Core2 processor (2.53 or 2.80 GHz), the Mobile Intel PM45 Express Chipset ICH9M-Enhanced, NVIDIA GeForce 9800 GT graphics with 512 MB VRAM, a 250 or 500 GB drive, an optical drive, and various I/O ports.

No official price has been announced, but rumor has it that the machines will cost you somewhere in the range of \$3,000.

DUAL MONITOR, NO LAPTOP



■ The EVGA Interview dual display.

Also geared for people who want to see double is the EVGA Interview™ Display, which features two rotatable, thin, high-res 17 inch displays supported by a single desktop stand. Designed for "business presentations, researchers, physicians, financial consultants, or creative professionals," the unit's 1440 x 900 resolution screens will flip 180 degrees on the horizontal axis and automatically invert the onscreen image to show it correctly for viewers on either side of the desk. The screens also fold 90 degrees from closed to fully open to allow workspace flexibility. It comes with two keyboards and mice so viewers can work with their image on one side while others can watch on the other side. It also sports a built-in 1.4 Mp webcam and a microphone for video conferencing. The base features three USB 2.0 ports and controls for monitor settings, the microphone, power, and DMS connections. MSRP is \$649.99, with Internet prices about \$25 less. For details, visit www.evga.com/interview.

INDUSTRY AND THE PROFESSION

"MIRACLE ROBOT" INVESTMENT OPPORTUNITY: STEP RIGHT UP

If you're sniffing around for a long-shot investment, take a whiff of an offer from Suram Robotics, an Indian firm that's looking worldwide for investors in its plan to build and market a "miracle robot." According to CEO and Project Chief Ashish Sood, "This is going to be one of the unique robots in the world." He informs

us that it can (a) be remotely controlled, e.g., functioning in the USA at the direction of an operator in India; (b) create other robots like itself, free of charge; (c) do all types of household and office work; (d) talk to any person on Earth and provide instant answers to questions; and even (e) look after your kids when you're away from home. According to Sood, "These robots will not charge anything for the work you require them to do, so you save a lot of money." Details about the robot itself are available at <http://raj6781.googlepages.com/miraclerobot>.

You can invest as little as \$100 in the project, for which you will receive a company shareholder certificate. Investors

will draw an "appropriate" portion of the profit when the robot goes on sale in world markets. Sood predicts that his aspirations (which ostensibly do not consist of a quick retirement in Brazil) can be accomplished within three months if sufficient investment capital is raised.

Curiously, interested investors are directed to www.mukeshambani.com, which doesn't seem to exist. But FYI, Mukesh Ambani is an Indian engineer and businessman, chairman and largest shareholder of Reliance Industries, and reputed to be the wealthiest Indian in the world, the wealthiest in Asia, and the seventh wealthiest in the world. One has to wonder why he hasn't kicked in enough to get the ball rolling.

ONE TOUGH HD



■ Hitachi's SimpleTOUGH drive, built for rough environments.

For people who work in harsh environments, tweet while bungee jumping, or just get drunk and fall down a lot, Hitachi has introduced the SimpleTOUGH portable USB 2.0 drive. According to the manufacturer, it is the "only water- and shock-resistant external drive available today from a global hard drive manufacturer." Engineered to sustain a 3 m (9.8 ft) drop and able to withstand being run over by a one-ton-class commercial truck, the SimpleTOUGH drive can take a

beating that's worse than a date with Chris Brown. It also includes a "never-lose" foldaway USB cable, ergonomic sides for easy carrying, and a topside power status LED. Inside is a Travelstar drive that can withstand shocks of 400 G in operation and 1,000 G when shut down. SRPs are \$99.99 for the 250 GB version, \$119.00 for the 320 GB, and \$149.99 for the 500 GB. Details are available at Hitachi Global Storage Technologies (www.hitachigst.com).


CIRCUITS AND DEVICES

SWITCHER FEATURES NO-LOAD CONSUMPTION <0.5W

If you're looking for an efficient, compact power supply,

you might consider a new series of switchers from CUI, Inc.'s, V-Infinity division (www.v-infinity.com). They feature a no-load power consumption less than 0.5W and come in 25, 50, 75, and 100W versions. The 25W unit (VGS-25) measures only 3.08 x 2.00 x 1.11 in (78.2 x 50.8 x 28.2 mm). The units are cooled by free air convection and offer efficiency ratings of up to 89 percent. They are suggested for a range of applications where energy consumption is an issue, including industrial controls, networks, general automation functions, and test and measurement equipment.

The VGS

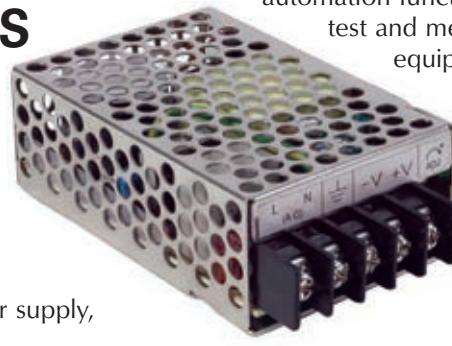

■ The V-Infinity VGS-25 compact switching power supply.

Saelig

UNIQUE PRODUCTS + SUPPORT!

7 in 1 USB Scope	Mixed-Signal Scope	50 - 300MHz DSOs
2-ch 10-bit 2MHz scope/spectrum-analyzer, 3MHz 8-bit wfm gen; 16 x I/O; Network Analyzer, Noise Generator; PWM. Windows/Linux/Mac compatible! USB-powered, great for toolbox, education, etc. CCR-101™ \$180	CleverScope - 100MHz Scope, Spectrum/Logic Analyzer for PCs. 4 or 8 Msample storage! Easy A-B, math & filters! 2 ch x 10, 12 or 14-bit, 8 dig. I/P. (Opt. 0-10 MHz SigGen. - \$299) CS328A-4 (4MS Buffer) \$1295 CS328A-8 (8MS Buffer) \$1474	60/100/200/300MHz 2 ch, 2GS/s DSO 2000 wfm/s refresh rate. High quality, ultra Compact Design with small footprint. Totally new price. DS1052E \$469 • thru • DS1302A FreeCase! \$1995
Wireless Analog	Multiparameter Loggers	I2C Xpress
4-ch analog input wireless module 433/868/915MHz. Low power serial interface. Easy configure. 24 bit ID to avoid cross-talk. 2 digital output. EmbedRF Module \$59 EmbedRF DevKit \$299	Mini-logger with built-in temp/humidity/pressure/3-axis accel sensors. Customize mstrm/recrd parameters; send data to PC after or during logging. Synchronize multiple loggers. MSR145S from \$468	Versatile USB2.0 I2C protocol exerciser/ analyzer. Ideal for all I2C bus system development and debug, it operates on standard I2C protocol interfaces in low-speed (10 kbps), standard (100 kbps) and fast (400 kbps) modes. \$699
.NET Board	EMC Spectrum Analyzers	SOMO-14D
Smallest (2.2" x2.2") lowest cost Microsoft's .NET Micro Framework development system. USB host & FAT file. Run C#, Visual Studio for programming. SD/USB memory, other I/F. USBizi-Devsys \$99	Handheld Palm PC-based 2.7GHz Spectrum Analyzer. Multiple sweep settings - store wfm, set-ups, etc. Use WiFi PC for email, reports, calculations. PSA2701T \$1990	14-pin Tiny Audio-Sound Module plays back pre-stored audio files (voice and music) from microSD card - ideal for embedded audio output. SOMO-14D \$25

Saelig www.saelig.com
unique electronics


1-888-772-3544

info@saelig.com www.saelig.com

Turn Your PC into a Real-Time Audio Spectrum Analyzer

Features

FFT to 1048576 pts
24 bit, 192kHz
1/96 Octave
Dual Channel
3-D Surface Plot
Spectrogram Plot
Digital Filtering
Signal Generation
RT-60, Leq, Delay
THD, IMD, SNR
DDE, Logging
Vibration Analysis

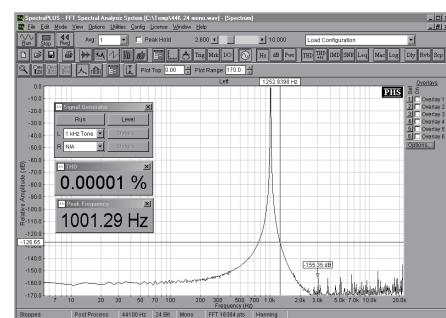

SpectraPLUS 5.0

FFT Spectral Analysis System

Download 30 day FREE trial!

www.spectraplus.com

Starting at \$295

PHS

Pioneer Hill Software
24460 Mason Rd
Poulsbo WA 98370

360 697-3472 voice
360 697-7717 fax
pioneer@telebyte.com

series offers a universal input (88 to 264 Vac) and single output voltages of 3.3, 5, 12, 15, 24, and 48 Vdc. They also include an LED on indicator, 105°C long-life electrolytic capacitors, and an operating temperature range of -25 to 70°C, derating linearly from 100% load at 50°C. They're also protected from short circuits, overloads, overvoltages, and brownouts. Best of all, you can get them in single units from Digi-Key Electronics (www.digikey.com) at prices starting at \$34.22.

SUBMINIATURE PUSHBUTTON SWITCH



■ The new SSP 129T subminiature pushbutton switch.

A new subminiature pushbutton switch has been introduced by Knitter-Switch, a Munich-based manufacturer of switches ranging from toggles to membranes to tactile switches. The SSP series is designed specifically for use with mobile multimedia devices, portable medical devices, and a variety of test and measurement instruments. The SSP 129T is a large travel alternative

to existing tactile switches that usually have a travel of only 0.25 mm and, in fact, match the PCB layout of the knitter-switch TSS309/TSS310 series tactile switches. With a footprint of just 7 x 3 mm and a longer travel of 1.6 mm, the switch is a surface-mountable device supplied in T/R packaging for automatic pick-and-place systems. Available in normally open and momentary contact versions, the

SSP 129T provides a 100,000 cycles operating life and incorporates a gold-plated contact plate for the reliable small-current switching. The company offers the switches through a network of European distributors but doesn't appear to have any North American outlets. Interested parties are advised to contact the home website at www.knitterswitch.com. **NV**

The Newest Products and Technologies are Only a Click Away!

mouser.com




- Over A Million Products Online
- More Than 390 Manufacturers
- Easy Online Ordering
- No Minimum Order
- Fast Delivery, Same-day Shipping

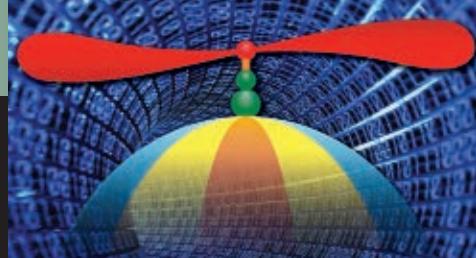(800) 346-6873



**The Newest Products
For Your Newest Designs**

Mouser and Mouser Electronics are registered trademarks of Mouser Electronics, Inc. Other products, logos, and company names mentioned herein, may be trademarks of their respective owners.



■ BY JON WILLIAMS

DO IT UP WITH DMX

Even if you've never heard of DMX512-A (DMX), chances are you've seen it in action. Where? At any large stage production. Concerts and plays are big users of DMX-controlled lighting. So, what if you're not one for concerts or the theater? Well, have you ever been to a night club with lots of crazy, dancing, pulsating lights? Then you've seen the magic of DMX.

So, what is DMX? It is, in fact, a very simple, half-duplex (one direction, controller to fixture) serial protocol that runs over a standard RS-485 hardware link. The protocol was originally designed for controlling stage lighting, but as it is so easy to implement it has been put to use in a variety of show control applications.

We can break down the protocol into four essential elements:


- Break (B)
- Mark After Break (MAB)
- Start Byte (S)
- Packet of Frames (Fx)

Figure 1 visualizes these elements as seen on the DMX RX pin of the Propeller.

The *Break* is what allows all receivers on the system to synchronize themselves with the packet; this is a space (0) on the line that lasts 88 μ s or longer. The *Mark After Break* is a short rest with the line at idle (1); the MAB is (8 μ s) or longer. The first byte that follows the MAB is called the *Start byte*; it is typically zero and ignored in many systems (though it really shouldn't be). DMX bytes are transmitted in 8N2 (eight data bits, no parity, two stop bits) format. After the *Start byte* is the *Packet of channel values* called *Frames* (0 to 255, also 8N2) which could be up to 512 bytes.

Light fades and motion are created by a master controller that streams the DMX data at a pretty swift clip: 250K baud. At this rate, the *Break*, *MAB*, *Start byte*, and 512 *Frames* can be transmitted every 22.7 milliseconds.

■ FIGURE 1. DMX Signaling.

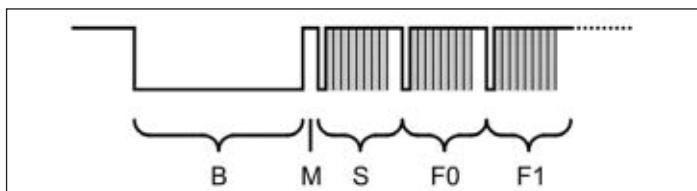

(per the DMX specification).

I've written DMX receiver code for the SX28 but it is a challenge, especially when one needs to do brightness control of LEDs as we intend to do here – there's not a lot of room left in the interrupt when running an RX UART VP at 250K. With the Propeller and a dedicated DMX receiver cog, however, it's really very simple – so much so that it makes me shake my head and smile.

What we're going to build this month is a generic DMX I/O add-on for the Propeller platform with three channels of medium current output to control devices like 12V LED circuits and small DC lamps. This will let us create a simple DMX lighting fixture using a high brightness RGB LED.

DMX HARDWARE

Figure 2 shows the schematic for a generic DMX interface – yes, this circuit can transmit, as well as receive. It would have been silly to design an add-on module for the Propeller that couldn't transmit as well, especially since the "cost" of this upgrade was a resistor and a single I/O pin. Pretty cheap price for the flexibility, don't you agree?

A quick note about JP1 and JP2: JP1 is used only when the node is the master (transmitting) and only one node will ever use JP1 (for receiver devices we leave this out). JP2 is for the end nodes (transmit or receive) on a DMX network; this resistor prevents reflections. So, if your DMX project using this circuit is the last on the DMX line then JP2 needs to be installed. For a lot of really great information on RS-485 hardware, please see Jan Axelson's book, *Serial Port Complete*.

For what it's worth, my design does, in fact, violate the DMX specification in that I'm using three-pin XLR connectors instead of the five-pin units that are normally called for. But guess what? I have a mini DMX console and a popular DMX lighting fixture here in my office, and both use three-pin XLR connectors; this "violation" is


pretty commonplace.

The circuit is a standard, half-duplex RS-485 interface that defaults to RX mode by pulling the /RE and DE lines low through resistor R4. You may be wondering why I went with a 5V device when a 3.3V device is available. Cost. There is a 5V supply on the Propeller platform and the cost of the 5V ST485BN plus resistor R3 is about half of the 3.3V device. R3 limits the current into the RX2 pin (DMX RX input) of the Propeller. R2 holds the line high (idle state) when the ST485BN is set to transmit.

mode and the RO output goes Hi-Z (this resistor is required for projects that will do bi-directional comms). Finally, we don't have to worry about direct control of the TXE line with the Propeller as the minimum V_{IH} level of the ST485BN is 2.0 volts.

Okay, let's have a look at the code. The heart of the object will, of course, run in its own cog, happily receiving DMX data on the assigned pin and writing it to an array that we can read from our top-level application. I've also added an activity output LED; this lights when receiving a frame byte so we know the line is active.

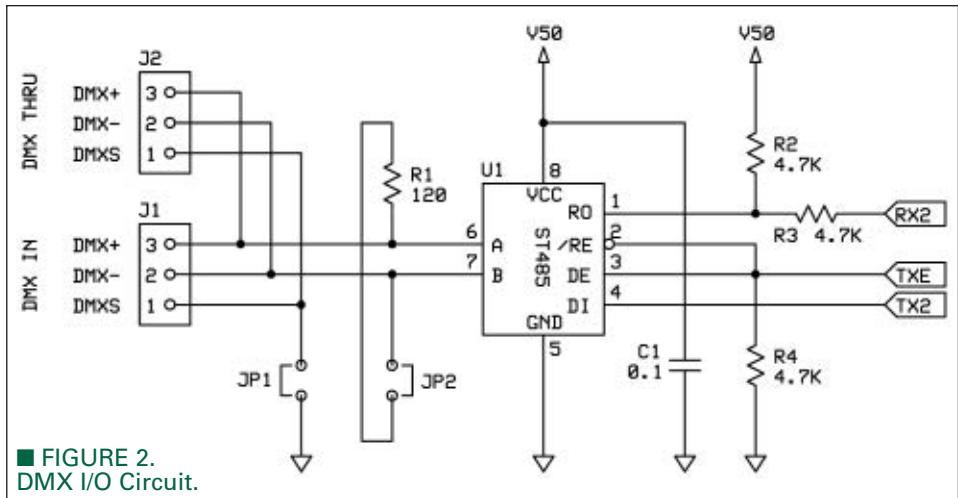From the top, here's the setup and code that monitors the DMX RX line for the Break period.



■ FIGURE 2. DMX I/O Circuit.

for the next Break, we can get into sync with the DMX stream.

After we've detected a valid break, we set up to receive up to 513 serial bytes. The first is the Start byte and will usually be zero. Still, we shouldn't ignore this byte; we should make it available to the application to check.

For review, a serial byte will have a start bit, eight data bits, and one or more stop bits; in DMX512-A, each byte has two stop bits. **Figure 3** shows the signal going into the DMX RX pin of the Propeller. The idle state of the line is high, a start bit is low (0), the data bits arrive LSB first and are read directly from the line. The stop bits are at the line's idle state (1). The value in the diagram is \$CF.

Another task to deal with is handling a short packet, that is, less than 512 frame bytes. A typical DMX controller will transmit the Start byte plus 512 frames, but it doesn't have to. For example, I have a mini, six-channel controller that sends the Start byte plus six frames, at a very low rate (every 100 ms). What I'm getting at is we'll have to smarten-up our serial receive code to detect a new break, even when we don't expect one.

getpacket	mov	bufptr, buf0
	mov	count, PACKET
rxbyte	mov	phsa, #0
	mov	rxwork, #0
	mov	rxcount, #8
	mov	rxtimer, US_006
	waitpne	rxmask, rxmask
	add	rxtimer, cnt
	or	outa, ledmask
rxbit	waitcnt	rxtimer, US_004
	test	rxmask, ina
		wc
if_c	mov	phsa, #0
	shr	rxwork, #1
	muxc	rxwork, #81000_0000
	dinz	rxcount, #rxbit



■ FIGURE 3. DMX512-A Byte Format.



breakcheck	waitcnt	rxtimer, #0	wz
	test	rxmask, ina	
	andn	outa, ledmask	
if_z	jmp	#shortpacket	
	wrbyte	rxwork, bufptr	
	add	bufptr, #1	
	djnz	count, #rxbyte	
	jmp	#waitbreak	

At the top, we set `bufptr` to the hub address of the array that will hold the DMX data and count to the number of bytes to receive (513). At `rxbyte`, the Break timer (`ctra`) is reset and we prep for receiving a serial byte that has a bit timing of 4 μ s (250K baud). The bit timer is initially set to 6 μ s (1.5 bits) so that we can position the bit sampling in the middle of the first bit; this timer will be activated (via syncing with `cnt`) on detection of the start bit. Note, too, that when the start bit is detected the LED is turned on to indicate DMX activity.

The bulk of serial receive code is at `rxbit`. After the bit timer expires, the DMX RX line is sampled with `test` and the RX bit value is moved into the C flag. If the C flag is set (1), then we can restart the Break timer – remember this is set up to auto-increment whenever the DMX RX line is low. After the Break timer is dealt with, the output value in `rxwork` is shifted right by one bit and we move the new bit from C into bit7 using `mxuc`. If there are more bits to receive, then the code loops back to `rxbit`; otherwise, it will drop through to `breakcheck`.

The program waits one more bit period (4 μ s) and then samples the line again, saving the result into the Z flag. At this point, we should be sampling a stop bit which is high. If, however, we have a new Break period then the line will be low (0) and the Z flag is set. When this happens, the program jumps back to `shortpacket` which completes and validates the timing of the new Break period.

Most of the time, though, we have a valid byte which is moved into the DMX array using `wrbyte`. Once the entire DMX packet has been received, the program

jumps back to `waitbreak` and starts all over.

So, there you have it, a DMX receiver engine in under 40 [working] lines of code. Of course, there is an interface in Spin which lets us set the RX and LED pins, and takes care of setting all the timing parameters to match the system clock. After the `init()` method, we'll use the `read()` method to grab a byte from the DMX stream. Remember, byte 0 will be the DMX Start byte; bytes 1 through 512 will be the DMX frames.

Before moving on, let me point out that there is a DMX object in the Propeller Object Exchange by Tim Swieter (www.brillidea.com) that is very advanced, providing all kinds of interesting statistics about the DMX stream (e.g., the length of the break, length of MAB, actual number of frames transmitted, etc.). If you're feeling brave, please have a look – you're sure to learn some new Propeller tricks. Tim's code will, of course, work on the P/P DMX I/O board, and is very useful for creating a DMX diagnostics device.

LED MODULATION WITH BAM

So, what is BAM? It's a Bit Angle Modulation that is a modulation strategy that uses a bit's position within a value as the basis for the timing of that position. For example, bit 0 is output and then we wait one 'period.' Next, we output bit 1 and hold for two periods. After that, we output bit 2 and wait four periods. You should start to see the pattern: The timing for a given bit is $2^{\text{bit}\#}$ periods. Following this pattern, the final bit in a byte, bit 7, has a timing value of 128 periods. In the end, the complete timing for one byte will be 255 periods, but we only had to deal with eight cycles (one per bit). The fact that we only have to deal with eight cycles (versus 256 with traditional PWM) is the source of most of the hoopla you'll find surrounding BAM.

Figure 4 shows the weighted timing in a four-bit BAM value. As you can see, bit 3 gets eight timing periods, bit 2 gets four periods, etc. In **Figure 5**, you can see what the output looks like when the BAM value is set to 10. I think it's the asymmetrical output (for most values) that helps BAM get around the LED PWM patent. (Yes, there is a patent for this.)

Most of the code you'll find on the Internet shows how to set up a variably-timed interrupt to handle the bit timing. The Propeller doesn't have or use interrupts so we're going to take another route – one that turns out to be deceptively easy. Here's my implementation of BAM for the Propeller.

bamrgb	or	dira, rmask
	or	dira, gmask
	or	dira, bmask
	min	TIX_001, #121
bamstart	mov	bitmask, #0000_0001
	mov	bitperiod, TIX_001
	mov	bittimer, bitperiod
	add	bittimer, cnt
	mov	tmp1, #0

Item	Description	Supplier/Part No.	BILL OF MATERIALS
C1	0.1 μ F	Mouser 80-C315C104M5U	
J1	XLR-3M	Mouser 523-AC3MAH-AU-B	
J2	XLR-3F	Mouser 523-AC3FAH-AU-B	
JP1-JP2	0.1 M-STRTR	Mouser 517-6111TG	
Jumpers		Mouser 517-950-00	
LED1	3 mm Green	Mouser 859-LTL-4231	
Q1-Q3	2N3904	Mouser 863-2N3904G	
Q4-Q6	TIP125	Mouser 512-TIP125	
R1	120	Mouser 293-120-RC	
R2-R4	4.7K	Mouser 291-4.7K-RC	
R5-R7	470	Mouser 291-470-RC	
R8-R10	1K	Mouser 291-1K-RC	
R11	330	Mouser 291-330-RC	
RN1	10K x 9	Mouser 71-CSC10A01-10K	
SW1	DIP x 9	Mouser 611-BD09	
TB1-TB3	5 mm Term Block	Mouser 571-2828362	
U1	ST485BN	Mouser 511-ST485BN	
X1-X4	0.1 M-STRTR	Mouser 517-6111TG	
PCB		GadgetGangster.com ExpressPCB.com	
Parts Kit		GadgetGangster.com	

getlevels	rdbyte	rlevel, rptr
	rdbyte	glevel, gptr
	rdbyte	blevel, bptr
bamloop	test	rlevel, bitmask wc
	muxc	tmp1, rmask
	test	glevel, bitmask wc
	muxc	tmp1, gmask
	test	blevel, bitmask wc
	muxc	tmp1, bmask
	mov	outa, tmp1
	shl	bitmask, #1
if_nz	and	bitmask, #\$FF wz
if_z	shl	bitperiod, #1
if_z	mov	bitmask, #0000_0001
	mov	bitperiod, TIX_001
	waitcnt	bittimer, bitperiod
if_nz	jmp	#bamloop
	jmp	#getlevels

On entry, we make the RGB pins outputs and do a quick check to ensure that the timing period is long enough to get the work done. You'll recall that using **waitcnt** is easy and convenient, but if we are short of the value and get a rollover, we end up waiting nearly a minute — not what we want to have happen here. The **min** instruction takes care of fixing a value that the user may have mismanaged in the interface section. I found the value of 121 estimating (counting cycles) and then empirical testing until it "broke."

At **bamstart**, we create a mask for bit 0, set the timing for bit 0 (one "period"), start a timer, and initialize a value that will hold the new outputs for each cycle.


The real work begins at **getlevels** where we read the RGB values from the hub. At **bamloop**, we test each color value against **bitmask**, writing the current bit value to the C flag. Using **muxc** and the channel mask for the color, the bit value is written to **tmp1** which is finally moved to the outputs. By using **tmp1**, all outputs are simultaneously updated.

The bit-under-test mask is then shifted left and **anded** with \$FF — if the result of the **and** operation is zero, then we're done with the loop; all eight bits have been processed which means we can reset the test mask and the bit period. Until this happens, we shift the value of **bitperiod** left by one which doubles its value; this is exactly what we need for the next higher bit.

After the timer expires, it is reset with **bittimer** and we jump back to **bamloop** for the next bit or to **getlevels** if it's time to start a new cycle. Done! Of course, you can add channels if you like. Just be sure to update the minimum timing for a bit period so that you can get all the work done within the cycle.

A SIMPLE DMX RGB LIGHTING FIXTURE

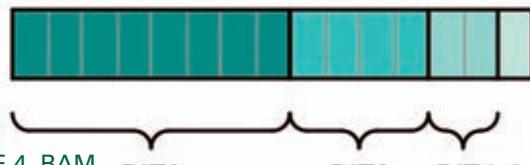With the hard work (which really wasn't very hard) out of the way, we can create a simple, three-channel DMX lighting fixture. For this, we'll need a device address



■ FIGURE 4. BAM Bit Weight Timing.

switch which corresponds to the first of our three channels — **Figure 6** shows a nine-position DIP switch wired to P0..P8 of the Propeller. No need to worry about the reverse bit order (which was done for PCB layout convenience); Spin has a neat trick which will take care of this for us.


For my first project, I wanted to drive a 1W RGB LED that a friend gave me, but I also wanted to run small DC lamps for other projects. In order to accommodate both, the circuit uses a moderate-current, high-side driver (**Figure 7**) on each output. Some of you will quickly point out that the final output transistor is missing a pull-up to Vin. Not so. This transistor is actually a TIP125 Darlington and, as you can see in **Figure 8**, the base has an internal 8.12K path to the emitter — we're covered, and with the TIP125 we can control plenty of current.

Okay, here's the code for the three-channel DMX fixture.




```
pub main | dmxstart, chan, level
  dmx.init(24, 16)
  rgb.init(9, 10, 11)
  repeat
    chan := ina[0..8]
    if (chan > 0) & (dmx.read(0) == 0)
      level := dmx.read(chan++)
      rgb.setred(rgb.ezlog(level))
      level := dmx.read(chan++)
      rgb.setgreen(rgb.ezlog(level))
      level := dmx.read(chan)
      rgb.setblue(rgb.ezlog(level))
    else
      rgb.setall(0)
```

I'm not kidding, that's all we need to knit the DMX receiver and BAM output objects together to create a DMX-compatible lighting fixture.

We start by initializing the DMX and BAM objects, and then drop into a **repeat** loop. The first line in the loop is really cool. What this does is read bits 0 through 8 of the inputs, masking off the others, and flipping their order (bit 0 to bit 8, bit 8 to bit 0). In one fell swoop, we've read the switch bits and put them into the correct order, giving us the current channel setting. Come on, you've got to think that's cool! Just so we're clear, we know that the bit

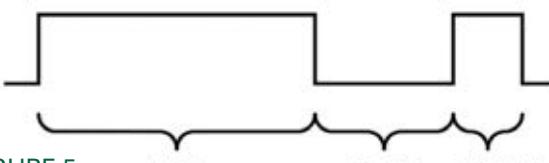

■ FIGURE 5. BAM Output OA.

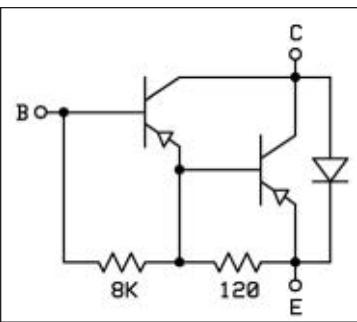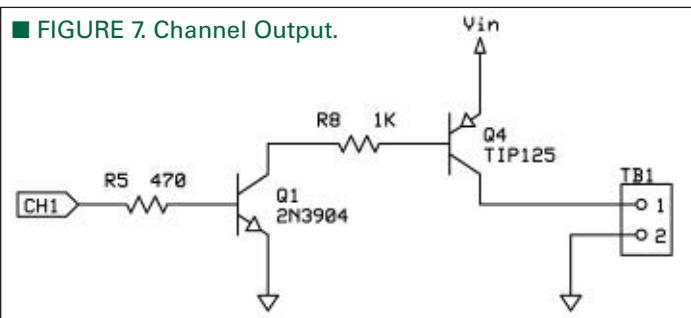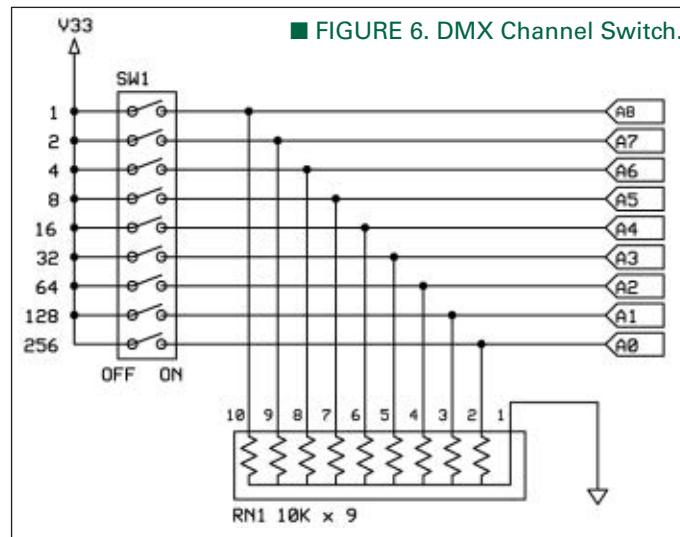

order is reversed because the LSB (0) is in the MSB position within the brackets. Another bonus that the switch could have used any set of I/O pins; so long as the group was contiguous. The only pins read are those defined within the brackets, and the result bits are flipped and shifted (to zero-align) if required. We can use this technique to read any parallel inputs and get a value that is immediately usable.

If the channel switch is valid (not zero) and the DMX

Start byte is valid (zero), then we read the channel values from the DMX array and move them to the outputs using BAM to handle the brightness modulation. You can see that Spin borrows heavily from C in that we can use

the post-increment operator (++) on *chan*; this lets us read the current channel and then update that variable before moving on.

Visually, LEDs can seem a little harsh when using straight linear values as we'd get from the DMX stream.

2.4 GHz Wireless Audio Modules

- Uncompressed digital wireless audio comms for high quality stereo
- 44.1KHz digital sampling rate with 16 bit resolution
- FSK digital modulation on 2.4GHz, +/- 100KHz stability
- Embedded antenna with diversity receiver antenna
- 8 selectable channels with 9MHz channel spacing
- 3.6Vdc to 5Vdc operation, 93mA (typ): Transmitter
- 5Vdc operation, 65mA (typ): Receiver
- Transmitter dimensions: 1.8" x 0.25"
- Receiver dimensions: 1.26" x 1.74"

TX-AUDIO-24

RX-AUDIO-24

www.abacomdirect.com

ABACOM TECHNOLOGIES


Build Your Own: THEREMIN

Theremax
The Ultimate Theremin

paia.com

PAIA Electronic Music Kits and More

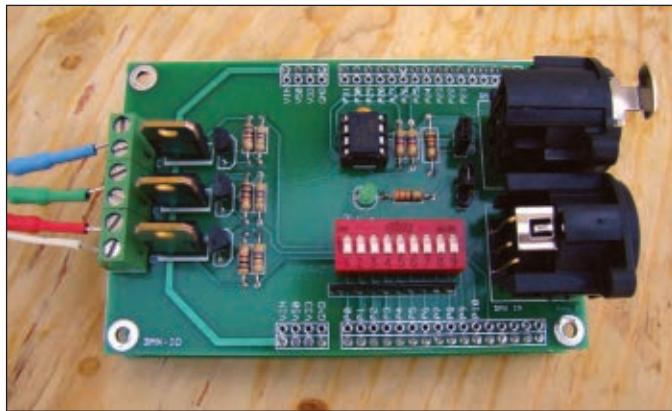Music/Tutorials/Kits
Analog Synthesizers
Guitar Effects
Tube Electronics
Studio Gear



■ FIGURE 9. DMX I/O Board.

A friend showed me a cute trick that creates a logarithmic curve: you simply square the value and then divide it by 256. Doing this makes the LED brightness output much more appealing. The math for this trick is wrapped up in a method called `.ezlog()` that is part of the BAM object. For you advanced users, there is also a method to read a value from a table which allows you to map the DMX input value to an output value as desired.

IF THREE IS GOOD, FOUR MUST BE BETTER!

My original design (see the prototype in **Figure 9**) was oriented toward RGB lighting control and as I was building it, a post in the Propeller forum vis-à-vis stepper motors got me thinking: If I added one more channel, I could control a unipolar stepper motor with the TIP125 outputs. Then, I thought: Why not add servo headers on the outputs, as well? So, for those of you who purchase the PCB or kit through Gadget Gangster (recommended; see **BOM**), you'll get the four-channel version which gives you more options for outputs. Of course, if you want to roll your own I've included the four-channel files in the PCB download at www.nutsvolts.com so you can use them as you please.

Okay, then, how about adding a little DMX to your holiday lighting arsenal? It could be a lot of fun and really make the neighbors jealous! Until next time — and next year! — here's to spinning and winning with the Propeller. **NV**

jwilliams@efx-tek.com

RF Specialists

RF Modules

From Part 15 to Part 90 Compliant
Narrow Band FM, UHF Multi-Channel




GSM/GPRS

M2M Solutions
GSM/GPRS modules and modem series



Industrial Bluetooth

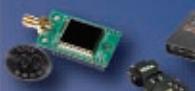OEM, Modules, Wireless Device Servers, RS-232
Long range options, low cost




Data Loggers

Stand Alone and
Wireless Mesh Networking Logger



GPS

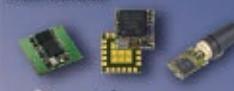OEM Modules and USB ZigBee Sticks,
Mesh Networks



ZigBee Pro

OEM Modules and USB ZigBee Sticks,
Mesh Networks



Wi-Fi

RS232 / 422 / 485 to Wi-Fi Adapter

Connect Data Acquisition Equipment through Serial Port to Wi-Fi network



LEMOS
INTERNATIONAL

www.lemosint.com
866.345.3667
sales@lemosint.com

EARN MORE MONEY!



**Be an FCC Licensed
Wireless Technician!**

**Make \$100,000 a year
with NO college degree**

**Get your "FCC Commercial Radiotelephone
License" with our proven Home-Study Course!**

- No need to quit your job or go to school.
- This course is easy, fast and low cost.
- No previous experience needed!
- Learn at home in your spare time!



**Move to the front of the employment line in Radio-TV,
Communications, Avionics, Radar, Maritime and more...
even start your own business!**

**Call now for FREE info:
1-800-932-4268**
ext. 209

Or, email us:
fcc@CommandProductions.com

Send to: **COMMAND PRODUCTIONS**
Warren Weagant's FCC License Training
P.O. BOX 3000, DEPT. 209 • SAUSALITO, CA 94966
Please rush FREE info kit today!

NAME: _____
ADDRESS: _____
CITY/STATE/ZIP: _____
You may fax your request to: 415-332-1901



■ BY L. PAUL VERHAGE

A NEAR SPACE ENVIRONMENT CHAMBER UPDATE

Sometimes it's difficult to leave things well enough alone. Occasionally, this is to my detriment as I can make things worse off than they were originally. Other times though, I end up with something better than when I started. This is the case with the near space environmental test chamber from my September column. Along with the improvements discussed in this month's column, you'll also find the results of a near space environmental test and a new vacuum pump I discovered.

BEEFING UP THE LID

During the original construction of the environmental test chamber, I experimented with three variations of vacuum chambers. They all worked except that their lids appeared to be weak. Therefore, instead of using these three chambers as they were, I settled on beefing up the lid of my largest canister. Not wanting to waste my other canisters, I later asked Dale at the Washburn Institute of Technology if he or his machining

■ I was concerned that this flour canister's original thin lid would implode under vacuum. Dale, the machining instructor, made sure I'd have one that wouldn't implode even if a truck ran over it. Best of all, it's clear and well polished. So, I can safely watch my tests under vacuum conditions.

class could create a new lid for my smallest stainless steel flour canister. Boy, did he — the new lid is one inch thick plastic. This is one serious lid. Since it's machined to the same diameter as the original wimpy lid, it uses the canister's original silicone gasket. The new lid is heavy enough that it must be held against the test chamber for a few seconds while the vacuum pump gets started.

DUAL USE

The first canister I tested when I built the environmental test chamber was a clear plastic flour canister with 1/8 inch thick walls. The cylindrical body appears to be strong enough to safely withstand a vacuum, but its thinner flat lid developed fine cracks

under vacuum. Dale recommended I use the same lid he machined for the small stainless steel chamber for this chamber. The new lid sits flat on the table and the plastic flour canister sits on top of it like a bell jar. Since this vacuum chamber is made entirely of plastic, it's not safe to chill with dry ice. Because of that, this vacuum chamber only performs vacuum tests at room temperature. However, since it's entirely clear, it's a great chamber for observing vacuum effects. After a dozen tests, I have yet to see cracks forming in the plastic, so I suspect it's safe. Just to be sure though, I won't let anyone stand next to it without wearing safety glasses.

NO MORE SWITCHING HOSES

Hose barbs are designed to prevent hoses from pulling loose. So, I can push a hose on a barb with very little difficulty, but man, it's so tough to pull the hose off that I have to resort to cutting the hose off in



■ The plastic bell jar with the thick lid as a base. The cylindrical shape of this canister makes it pretty resistant to atmospheric pressure.

tiny little pieces. Rather than waste good fuel hose every time I switch vacuum chambers, I decided to make a manifold. All the brass threads were wrapped in Teflon tape before screwing them together with a wrench (I don't plan to take this manifold apart). Since the manifold connects several vacuum chambers to a single vacuum pump, I just have to open and close the valves to evacuate the proper chamber.

To use the manifold, I turn two of the three needle valves clockwise to close off their chambers and turn the third needle valve counter-clockwise to open up its chamber. After completing the experiment, I shut off the vacuum pump and open the fourth needle valve on the very right to bleed air back into the system.

PUTTING IT ALL TOGETHER


Organizing the three environmental test chambers into a compact and easy to carry apparatus requires the Masonite, plywood, and pine rig you see in the **photo**. The vacuum stand has a base consisting of two sheets of Masonite pegboard separated with 3/4 inch thick pine. Two diagonal pine boards keep the pegboard backboard perpendicular to the base and create convenient grips for hauling it around. The manifold is nylon zip-tied to the backboard where it's easy to operate it and monitor the pressure.

MY FIRST ENGINEERING TEST

Satellite electronics need to

The base and backboard of this vacuum stand creates a unified environmental test chamber from lots of loose parts. Have vacuum will travel.

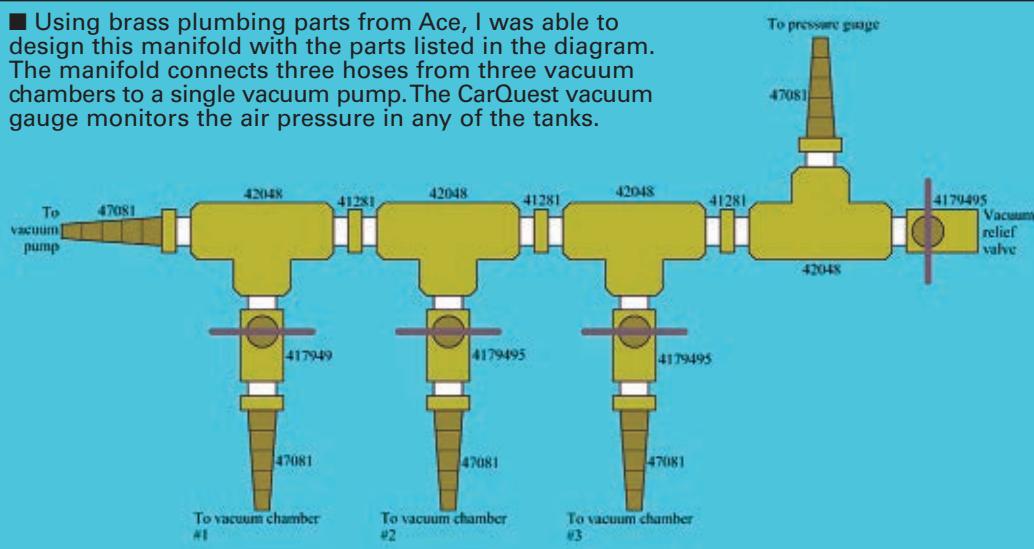■ Using brass plumbing parts from Ace, I was able to design this manifold with the parts listed in the diagram. The manifold connects three hoses from three vacuum chambers to a single vacuum pump. The CarQuest vacuum gauge monitors the air pressure in any of the tanks.



stay warm if the satellite is to properly function for 10 years or more. To maintain the proper temperature, satellites use electric heaters and insulation in the form of alternating layers of aluminized Mylar and scrim. This alternating sandwich of aluminized Mylar and scrim is called multilayer insulation (MLI) and it acts like a lightweight thermos bottle. The design of MLI helps keep the satellite warm in three ways.


First, the scrim sheets minimize contact between the Mylar sheets so very little heat flows from the warm satellite interior to the cold vacuum of space. Second, the vacuum of space removes air from between the layers to prevent heat flow via the movement of air. Finally, the thin coating of aluminum on the Mylar sheets reflects infrared radiation back into the satellite (and it keeps the intense heat of sunlight out of the satellite).

I've often used the same kind of insulation for my near spacecraft. Rather than using aerospace rated materials though, I use plastic wedding veil material for the scrim and a space blanket for the aluminized Mylar. Typically, I wrap three layers around an airframe and then tape it down with a little packaging tape. I have discovered that the layers of space blanket and wedding veil material are tough enough that I can sew them together in a blanket that I can wrap about the airframe.

MLI works in outer space with its extreme vacuum to protect satellites and it works on earth to insulate cryogenic lines and containers. However, I want to know if it really works well in near space where the vacuum isn't quite as high and the

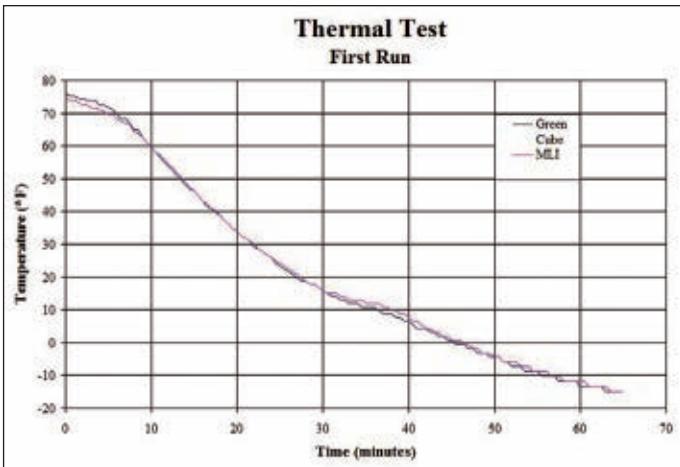■ **Two nearly identical cubes ready for their test. The one on the left is covered in three layers of MLI, while the one on the right is just covered in green tape.**





■ On the first run, both Hobo dataloggers recorded nearly the same temperature changes. So, it appears that the MLI is a waste of time and materials for near space experiments.

temperatures are not quite as low. To find out, I did a little experiment with my new environmental test chamber.

For this experiment, I built two identical cubes from 1/2 inch thick Styrofoam. One cube has a wrapping of green tape and the second a wrapping of three layers of MLI. The cubes were hollow, so a Hobo datalogger could sit inside and record the interior temperature. After loading the Hobos, the cubes were tightly taped shut. The big environmental chamber was then loaded up with dry ice and allowed to chill in preparation for the test. Both cubes were loaded inside the chamber, the door was closed, and the chamber pumped down. The test ran for about 30 minutes before the cubes were removed.

Because of the possibility that the dataloggers wouldn't record the same temperature under identical conditions, the cubes were allowed to warm up and the dataloggers were switched between cubes. The

process was run a second time for about 30 minutes. Afterwards, the Hobos were removed and their data downloaded. You can see from the charts that it was a good thing my classroom ran the experiment a second time.

Looking at these results, I suspect the Hobos are not calibrated quite the same. Perhaps it would be appropriate to average the two tests and claim the MLI covered cube remains four to five degrees warmer than a cube without MLI. I'd like to think this is the case because of the amount of time I spent covering my airframes in MLI. Before I try this test again, I'll set the Hobos out and verify that they record the same temperatures.


The only problem I ran into during this experiment is that the lid on the large environmental chamber is loose enough that air pressure outside can shift it just enough to the side to break its seal. Eventually, I'll have to have a new lid machined for the large chamber that fits a bit more snuggly.



THE HANDI-VAC

I was out grocery shopping when I saw

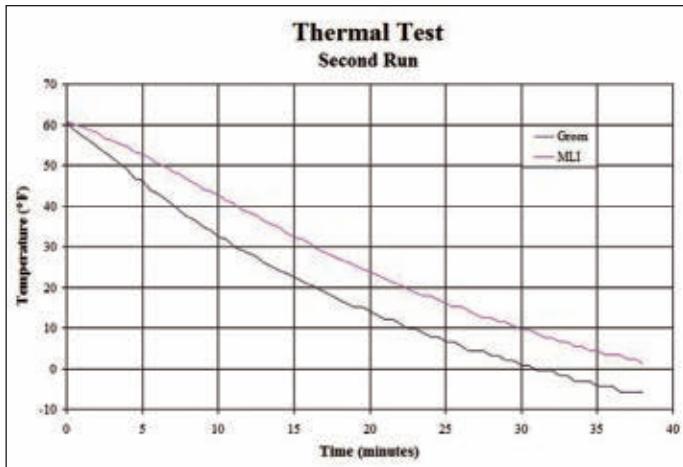■ Running a test on the Handi-Vac vacuum chamber. Inside the sealed zip lock bag is the Rubbermaid container with a pressure sensor.



■ But then again, maybe it's not a wasted effort. This chart shows that the MLI covered cube is nine degrees warmer after 35 minutes in the environmental test chamber.

Reynolds (maker of aluminum foil) developed what might be a convenient vacuum pump. Handi-Vac is a food storage system. Food is loaded into a zip-lock storage bag and then a battery-operated handheld pump evacuates the air inside. So, I thought this would make a great vacuum pump for science experiments. I purchased one and an extra set of bags in the name of science.

The Handi-Vac pump has a rubber seal in its nose (it's called the suction tip) that's placed in contact with a specific region marked on the zip-lock bags. This area has a series of tiny openings that allow air to be pulled out, but seal when air tries to flow back in.

Now, I've observed vacuum bagging before. After removing the air, the contents inside the bag are crushed by atmospheric pressure. This is good when you need to apply pressure all around an object, like when curing a composite set-up. But the crush is a disaster for the experiments I want to perform. To prevent the crush, I purchased some large Rubbermaid™ cube shaped plastic storage containers. The vacuum bag can't crush a storage container inside of them, but experiments inside the container will still experience a vacuum if holes are drilled through the container and its lid. I selected roughly cube shaped storage containers to

THE TRANSFER OF THERMAL ENERGY

Thermodynamics is a big and complex science subject. A small part of this big science that the near space community is interested in is how to keep our experiments warm during a mission. We want to keep our near spacecraft warm using lightweight, passive methods as opposed to using batteries and heaters. As this article alludes to, there are three ways to transfer thermal energy in a system and MLI helps to minimize all three.

Conduction is the net flow of heat by the physical contact of two substances that are at different temperatures. When you pour cold water in a warm cup, heat flows out of the warm cup and into the cold water. The result is that the cup cools down as the water warms up. Note that energy is really flowing in both directions between them. It's just that a lot more heat flows into the cold water than the warm cup. It actually gets a little more complicated because different substances require different amounts of thermal energy to change their temperature. So, just because a metal cup and the water inside are at the same temperature, it doesn't mean there's an equal amount of energy flowing between them to maintain their equal temperatures.

Convection occurs when matter carries energy from a hot volume into a cold volume. A good example occurs when you open the door of a hot oven. The hot air inside the oven carries some of the heat from inside the oven into the kitchen.

Radiation is like convection, but instead of the moving thermal energy by the movement of matter, thermal energy moves by the movement of photons (light). If you've ever placed your hand near an incandescent bulb (like a heat lamp), your hand has experienced heating due to radiation.

There's a lot more to heat flow and events like a phase change add additional complications. However, you don't need a Bachelor of Science in engineering to limit the amount of cooling your near spacecraft experiences on a mission. You just need to insulate it properly.

maximize the volume I would have for experiments.

To test the effectiveness of the Handi-Vac, I loaded a pressure sensor inside the container, sealed the lid over the container, placed it inside the storage bag, sealed the zip lock bag, and pumped it down. Here's the result.

The Handi-Vac pumped the zip lock bag down to just under half an atmosphere. That's not bad for a \$20

vacuum pump. However, a pressure of 500 mb is only equivalent to an altitude of 18,000 feet, so this vacuum chamber can only reach the mid to low 20,000 feet.

Therefore, I can see someone testing a rocket flight computer with the Handi-Vac. The pump removes the air, simulating the ascent of the rocket. After reaching peak altitude, the bag is opened slightly to let the air back inside,

Top Quality Hobbyist & Professional Soldering Kits

CL1481-K Hobbyist Soldering Tool Kit \$49.95

- Constant temperature soldering iron
- SOLDAPULLT® Desoldering hand tool
- Cutter & plier set
- TWIP® Solder & wick holster
- SOLDASIP® Desoldering wick
- 2-piece soldering tip kit

\$129.95 CL1481-K Professional Soldering Kit

- Temperature controlled soldering iron
- SOLDAPULLT® Desoldering hand tool
- SOLDASIP® Desoldering wick
- TWIP® Solder & wick holster
- 5-piece soldering tip kit

Made in Van Nuys, California
EDSYN®
...bringing innovative ideas to life

www.edsyn.com

(818) 989.2324


Solar, Wind and Hydrogen Renewable energy teaching aids



Visit www.learnonline.com for more info


REEL Power
Renewable Energy Education Lab

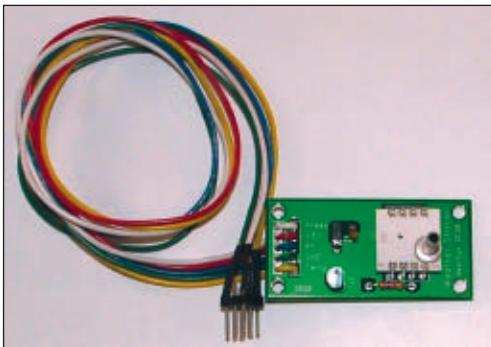Changing the way we learn
LEARNONLINE.com™



■ The NearSys Weather Station. Its PCB measures one by two inches and the kit doesn't cost much more than the pressure did originally.

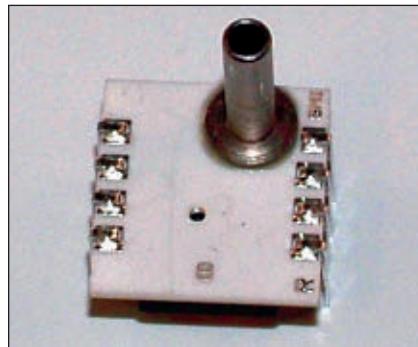simulating the descent. The bag is clear, so if the container is also clear, you can observe the experiment during the test. Events like the firing of an ejection charge can be observed if the charge is




replaced with an LED indicator.

THE PRESSURE SENSOR

I used a Silicon Microstructures (www.si-micro.com) SM5812 pressure sensor for my vacuum chamber tests and near space experiments. The sensor operates over a pressure range of zero to just over 1,000

millibars (mb), or from vacuum to the average pressure at mean sea level. The output voltage swings from 0.5 volts to 4.5 volts (a four volt swing) over

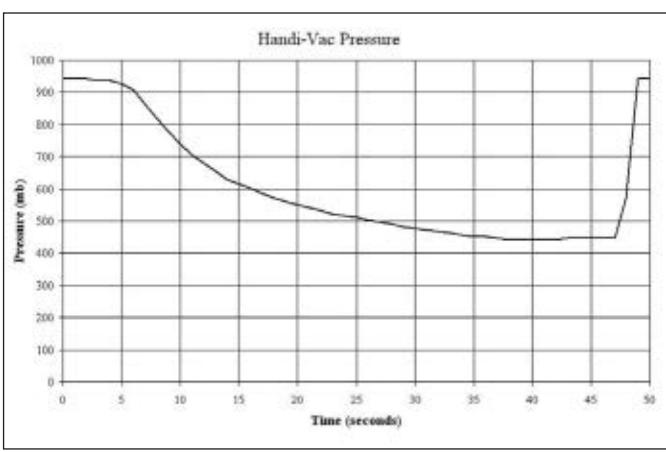■ The pressure sensor experienced a minimum of 450 mb of pressure after pumping it down. That's over half way to a vacuum.



■ This is one really sweet unit. Amplified output for a pressure swing from 0 to 1,000 mb — an entire near space mission.

this pressure range, so the SM5812 needs no amplification. This is one of the few pressure sensors I have ever found capable of producing an output over the entire range of a near space flight. Almost everything else operates over a smaller pressure range or needs amplification.

Alas, the SM5812 is at the end of its life because SMS no longer manufactures them. I managed to pick up the remaining units and have developed a near space weather station kit with this sensor. The weather station provides measurements of relative humidity, temperature, and pressure as voltage levels. Combine the weather station with a datalogger with three ADCs and you've got yourself a small, stowable, weather station. If you're interested in the weather station, the complete kit is available from NearSys for \$40 plus \$4 shipping and handling. Check NearSys.com/catalog for details and assembly directions.

Onwards and Upwards,
Your near space guide **NV**

You can watch a video on the updated environmental test chamber on my YouTube channel at www.youtube.com/nearsys.

GIZMOS THAT BRING YOUR DREAMS TO LIFE!



Robot wheel with 12v gear motor \$9 Hobby motors starting at \$2

Oregon Scientific Smart Globes make learning fun Starting at \$20



NIMH Battery Packs 8.4V 2000mAH \$2.50



Coin cell 3V batteries Starting at \$1

Weather Stations starting at \$20 Sensors and parts \$2




5797 NW Cornelius Pass Road
Hillsboro Oregon 97124




Lego Flashlights
Keychain \$7.95
Head Lamp \$11.95
7inch Lamp \$19.95
Dynamo Lamp \$21.95
Let that light shine in the next generation!

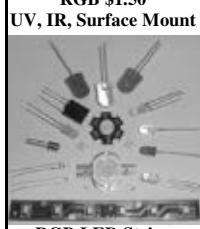1000's of LED's in stock
1.8mm, 3mm, 5mm, and 10mm from \$.40
1/2 watt \$.95
1 watt Stars \$3.60
RGB \$1.50
UV, IR, Surface Mount



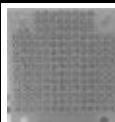RGB LED Strips
12v LED Bars
LCD Displays
Graphic and Character



Perf Boards
From .50 to \$2
830 point solderless breadboard \$8.50
Jumper wires \$6.25



4in medical grade casters
260lb capacity \$2.50
Foam robot wheels starting at \$.80
4in plastic wheels \$.50




TA8080K DC motor Controller IC
Only \$2.00
TA8261AH 40 watt 4 channel audio amp chip \$2.00

USB to IDE/SATA adaptor with power supply for easy backup of any hard drive.
Only \$20



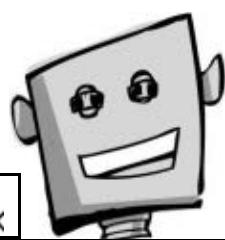Lighted switch \$3.25
Micro-reed switches only \$3.00
Limit switches starting at \$2.00
Reset switches \$.80
Aircraft toggle covers \$1.80
Arcade game buttons in many colors \$2.25



To see the best deals join our online mailing list or stop by our retail store!

www.SurplusGizmos.com
503-439-1249

THE ORIGINAL SINCE 1994

PCB-POOL®

Beta LAYOUT


Servicing your complete
PCB prototype needs :

- Low Cost - High Quality PCB Prototypes
- Easy online Ordering
- Full DRC included
- Lead-times from 24 hrs
- Optional Chemical Tin finish no extra cost

NEW!
NEW!

Watch "ur" PCB®
Follow the production of your PCB in
REALTIME

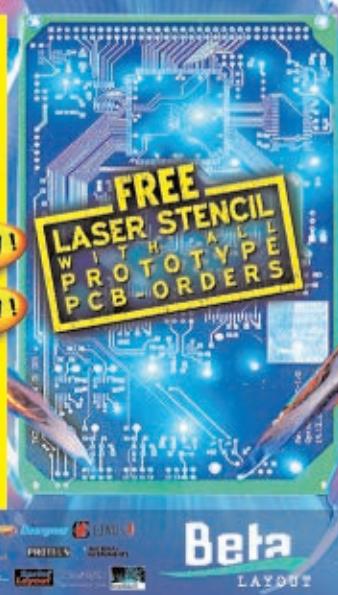email : sales@pcb-pool.com
Toll Free USA : 1 877 390 8541
www.pcb-pool.com



WIRELESS MADE SIMPLE®

BRING YOUR PRODUCT QUICKLY AND LEGALLY TO MARKET

RF Modules

Low-Cost TX, RX & TRX Modules



OEM Products

Handheld TXs



Feature Products

LOW-COST - LONG-RANGE TRANSCEIVER

- Direct serial interface
- Low power consumption
- PLL-synthesized architecture
- RSSI and power-down functions
- Compact surface-mount package
- No external RF components (except antenna)



A closer look at Linx innovation

REMOTE CONTROL TRANSCODER IC

- Up to 8 Inputs
- Bi-directional control
- Transmitter ID output
- Automatic confirmation
- Secure 2nd possible addresses
- Latched and/or momentary outputs

800-736-6677

159 Ort Lane • Merlin, OR 97532


www.linxtechnologies.com



Biped BRATs



Round 3DOF Hex

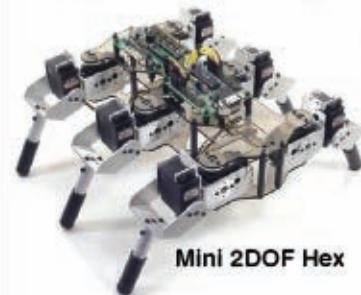


Mini 2DOF Hex

Lynxmotion


The Lynxmotion Servo Erector Set
Imagine it... Build it... Control it!

With our popular Servo Erector Set you can easily build and control the robot of your dreams. Our interchangeable aluminum brackets make the ultimate precision mechanical assemblies. Our Visual Sequencer for SSC-32 provides powerful PC, Atom, or BS2 based control.

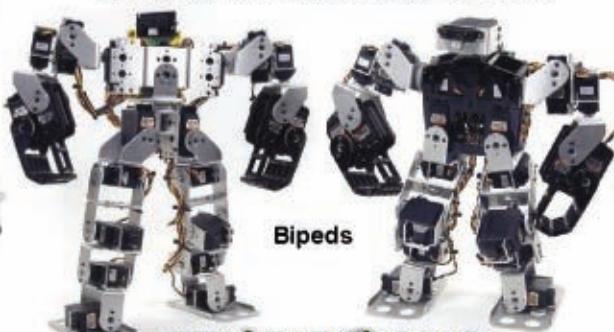
Visit our huge website to see our complete line of aluminum and Lexan based robot kits, electronics, and mechanical components.



Bipeds

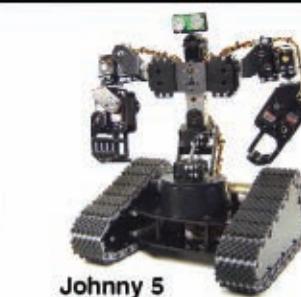

Johnny 5

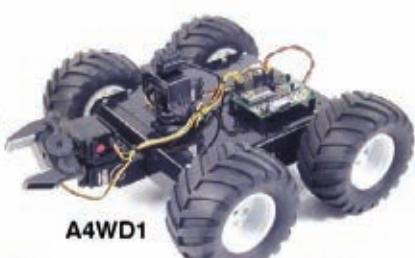

A4WD1



AL5C Arm

Images represent a fraction of what can be made!

www.lynxmotion.com
Toll Free: 866-512-1024

The SES now has 143 unique components!

Get Ready For The Holidays With a Ramsey Kit!

Passive Aircraft Monitor



Most popular new kit ever!

Our patented circuit monitors the entire aircraft band without any tuning! Passive design has no radiation, no interference, for use onboard aircraft to listen to air to ground! Great for air shows to listen to the active planes!

ABM1 Airband Rcvr Kit \$89.95

High Power LED Strobe



Super bright LED's!

The fragile glass Xenon tube is gone, replaced with high intensity LED's! Variable flash rate and built-in audio trigger input to sync to your audio. Optional display boards available. Runs on 12VDC or use our AC125 PS.

LEDS1C LED Strobe Kit \$44.95

Personal Guitar Amp



Practice in peace!

The new PGA1 allows you to practice both your regular and base guitars in peace! Also works as a great DI to feed your home stereo amplifier! CD/MP3 input allows you to play to your favorite music. Includes case shown!

PGA1 Guitar Amp Kit \$64.95

ECG Heart Monitor



Check your own heart!

Provides a visible and audible display of your heart rhythm! Variable gain, bright "beat" LED, and monitor output for display on your scope. Just like the lab! Re-usable sensors are included. Runs on a safe 9VDC battery.

ECG1C ECG/EKG Kit \$44.95

Plasma Generator



Generate 2" sparks!

Produces a stunning and shocking 25kV at 20kHz from a solid state circuit! Build your own plasma bulbs, light fluorescent tubes without wires and more! A great learning kit. Runs on 16VAC, order our PS21 power supply.

PG13 Plasma Gen Kit \$64.95

HV Ion Generator



Make a blast of fresh air!

Generates a steady state DC voltage at constant non-pulsed current at 7.5kV DC negative, 400uA. That's a LOT of ions! Learn how modern spacecraft use ions to accelerate through space. Runs on 12VDC or our AC125 PS.

IG7 Ion Gen Kit \$64.95

20W SubMini Audio Amp



20 watts and no heat!

Delivers a super clean 20W output from one SMT package! Ultra efficient class D design produces no heat. PCB can be snapped into a small circle for special applications. Runs on 18VDC for rated output, use our SPS18 PS.

UAM2 20W SMT Amp Kit \$34.95

Digital Voice Storage



Multiple message storage!

The Bullshooter-II provides up to 8 minutes of digital voice storage that can be broken down into 8 separate stored messages! Great for announcements, etc. Built-in mic plus external input. Runs on 12VDC or our AC125 PS.

BS2C Bullshooter-II Kit \$69.95

Speed Radar Gun



Now YOU can be the cop!

Our famous Speedy radar gun teaches you doppler effect the fun way! Digital readout displays in MPH, KPH, or FPS. 1/8th mile range is typical. You supply two coffee cans! Runs on 12VDC or our AC125 power supply.

SG7 Speedy Radar Kit \$69.95

Doppler Direction Finder



Find that transmitter quick!

Track down jammers and hidden transmitters with ease! 22.5 degree bearing indicator with adjustable damping, phase inversion, scan and more. Includes 5 piece antennal kit. Runs on 12VDC vehicle or battery power.

DDF1 Dir. Finder Kit \$169.95

40W Stereo Micro-Amp



40 watts of stereo in 2 1/2"!

The big brother to the UAM2, it delivers 40W of crisp clear stereo power all in a 2 1/2" board! One single SMT device operating 87% efficient creates virtually no heat! Selectable gain, pop filter and a lot more! Runs on 10-18VDC.

UAM4 40W SMT Amp Kit \$69.95

Signal Magnet Antenna



Pulls in distant stations!

Super Hi-Q ferrite rod antenna with Faraday shield eliminates noise from power lines, dimmers, static and more! Great results from 500kHz to 15MHz. Super for AM broadcast band! Includes power supply.

SM100 Sig Magnet Kit \$89.95

Mini-Kits... Holiday Themes!

LED Animated Santa

Animated Santa and reindeer display has 126 dazzling colored LEDs! Makes a great holiday sign! Animated motion makes it come alive. Runs on standard 9V battery or external power supply.

MK116 LED Santa Kit \$16.95

LED Christmas Tree

Electronic Christmas tree features 134 bright colored LEDs in the shape of a tree with 18 random flashing blinking "candles"! Runs on a 9V battery or PS.

MK117 LED Christmas Tree Kit \$18.95

LED Animated Bell

This holiday bell is animated to simulate swinging back and forth! 84 bright colored LEDs will dazzle you with holiday cheer! Includes an on/off switch. Runs on 9V.

MK122 LED Bell Display Kit \$16.95

3D LED Christmas Tree

Not your average LED display! 4 branch sections give this tree a 3D look! 16 red LEDs light it up with yellow LED's for you to customize your tree! 9V battery base.

MK130 3D LED Tree Kit \$7.95

SMT LED Christmas Tree

Build this subminiature Christmas tree and learn SMT at the same time. Small enough to wear as a badge or pendant! Extra SMT parts are included so you can't go wrong! Runs on Li-Ion cell.

MK142 SMT LED Tree Kit \$10.95

SMT LED Smiley Face

This is a great attention grabber and also teaches you the basics of SMT construction! Display your "smiley" as a pin or badge! Extra parts included!

MK141 SMT LED Smily Kit \$9.95

LED Traffic Signal

Impress your friends with this neat 4-way traffic signal! Operates just like a standard signal, and features adjustable delay. Red, yellow, and green LEDs are used just like the real thing! Runs on 9V battery.

MK131 LED Traffic Signal Kit \$7.95

LED Switcher Blinky

Run a 3V LED from 1.5V! Learn power supply switching and end up with a super bright blue Telux LED blinking at 140kHz! Runs on a single AA battery not included.

LSW1 LED Switcher Blinky Kit \$14.95

Wheel Of Fortune

Just like the casino game! Just push the button and the LEDs "rotate" and slowly come to a stop, displaying the "winner"! Push it again to start over. Runs on 9V battery.

MK152 Wheel Of Fortune Kit \$7.95

Cable Polarity Checker

You get a home theatre system for the holidays, you run cables throughout the house, how do you identify polarity? It's easy with the MK132!

MK132 Cable Polarity Checker Kit \$8.95

Water Sensor Alarm

The sump pump quits, the snow melts, the basement floods! Don't let it happen with the simple water sensor alarm. 9V battery operation with remote sensor.

MK108 Water Sensor Alarm Kit \$6.95

Did You Know...

The Solution!

It's impossible to give you full specs on these products in a 1" space!
A lot of our kits are also available "factory assembled and tested", if you don't want to build it!
We have over 350 products currently available, and all those don't fit here!

Visit www.ramseykits.com
Free Giveaways and ALL the information you ever needed!

FM Broadcasters

Fun Stuff For The Holidays!

Digital Controlled FM Stereo Transmitters

- ✓ Rock stable PLL synthesized
- ✓ Front panel digital control and display of all parameters!
- ✓ Professional metal case
- ✓ Super audio quality!
- ✓ 25mW and 1W export models!



For nearly a decade we've been the leader in hobbyist FM radio transmitters. When it became time for a new model, we started from the ground up! We told our engineers we wanted a new technology transmitter that would provide FM100 series quality without the advanced mixer features. They took it as a challenge and designed not one, but TWO transmitters!



The FM30 is designed using through-hole technology and components and is available only as a do-it-yourself kit, with a 25mW output very similar to our FM25 series. Then the engineers redesigned their brand-new design using surface mount technology (SMT) for a very special factory assembled and tested FM35WT version, with 1W output for our export-only market! Both are designed around an RF tight vinyl clad metal enclosure for noise free and interference free operation. All settings are done through the front panel digital control and LCD display! All settings are stored in non-volatile memory for future use. Both the FM30 and FM35WT operate on 13.8 to 16VDC and include a 15VDC 110/220VAC plug in power supply. The stylish black anodized aluminum case measures 5.55" W x 6.45" D x 1.5" H. and is a great match to your other equipment.

(Note: After assembly of this do-it-yourself hobby kit, the user is responsible for complying with all FCC rules & regulations within the US, or any regulations of their respective governing body. FM35BWT is for export use and can only be shipped to locations outside the continental US or valid APO/FPO addresses or valid customs brokers for end delivery outside the continental US.)

FM30B Digital FM Stereo Transmitter Kit, 0-25mW, Black \$199.95
FM35BWT Digital FM Stereo Transmitter, Assembled, 1W, Black \$299.95

Professional Synthesized Stereo FM Transmitter

- ✓ Built-in audio mixer!
- ✓ 2 line inputs, auto mic ducking!
- ✓ Dual LED bar graph meters
- ✓ Drift-free synthesized operation
- ✓ Precision brick wall audio filter!
- ✓ 25mW and 1W export models!
- ✓ Professional metal case!



The true professional workhorse of our FM Stereo transmitter line, the FM100B has become the transmitter of choice for both amateurs and professionals around the world. From the serious hobbyist to churches, drive-in theaters, colleges and schools, it continues to be the leader. Not just a transmitter, the FM100B is a fully functional radio station and provides everything but the audio input and antenna system.

This professional synthesized transmitter is adjustable directly from the front panel with a large LED digital readout of the operating frequency. Just enter the setup mode and set your frequency. Once selected and locked you are assured of a rock stable carrier with zero drift. The power output is continuously adjustable throughout the power range of the model selected. Audio quality is equally impressive. A precision active low-pass brick wall audio filter and peak level limiters give your signal maximum "punch" while preventing overmodulation.

Two sets of stereo line level inputs are provided with front panel level control for both. Dual front panel LED bargraph meters provide left and right channel audio level metering. In addition to the line level inputs, there is a separate microphone input with a built-in mic mixer to control the level.

Not enough? How about unattended microphone ducking! When enabled, the presence of mic audio automatically reduces and overrides the line level input! Just like the professional units at a fraction of the cost. The FM100B is truly a complete radio station!

(Note: After assembly of this do-it-yourself hobby kit, the user is responsible for complying with all FCC rules & regulations within the US, or any regulations of their respective governing body. FM100BWT is for export use and can only be shipped to locations outside the continental US or valid APO/FPO addresses or valid customs brokers for end delivery outside the continental US.)

FM100 Super-Pro FM Stereo Radio Station Kit, 5uW-25mW \$269.95
FM100BEX High Power Version Kit, 5uW-1Watt Output \$349.95
FM100BWT Export Only Transmitter, 5uW-1Watt, Assembled \$429.95


Get The Catalog!

Get the latest 2009 Ramsey Hobby Catalog! **96 value packed pages** of the neatest goodies around with lots of new stuff! Order yours today on line or give us a call... Or download the PDF at www.ramseykits.com/catalog



AM/FM IC Radio Training Lab

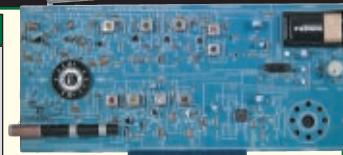- ✓ Learn all about AM and FM radio theory and circuits!!
- ✓ Build an IC based radio with great reception!
- ✓ Step-by-step assembly & test procedures!



These Superhet AM and AM/FM radio kits give you a great introduction to how AM and FM radios actually work! Plus, they are designed using integrated circuits rather than standard discrete components.

The unique design includes an integrated circuit (IC), 9 transistors, 4 diodes, and other related resistors, capacitors, coils, and misc. parts. Learn all about IC design, theory, and troubleshooting! And when you're done you have an AM or an AM/FM radio that has really great reception...that you made yourself! IC's, transistors, resistors, capacitors, coils and other parts are easily identified, and described in theory. The comprehensive manual includes step-by-step assembly and test procedures, and complete theory. The final alignment section is also provided to make sure you have a great sounding receiver! 9V battery required.

AMFM108K AM/FM Integrated Circuit Radio Learning Kit

\$34.95

Surface Mount Soldering Course & Kit

- ✓ Learn SMT soldering the easy way!
- ✓ Learn all about those tiny parts!
- ✓ End up with a neat "Decision Maker"!



You're going to have to go there some day, so it might as well be now! Virtually all electronic designs have gone to Surface Mount Technology. SMT components are small, at times the size of a pin head, and require very special skills to assemble and solder. This kit takes you through all that, including soldering, desoldering, removing, and component placement. When you're done, you have a neat electronic Decision Maker!

SM200K SMT Practical Soldering Course & Kit

\$22.95

Electronic Learning Labs

- ✓ Learn and build!
- ✓ 130, 200, 300, and 500 in one!
- ✓ Super comprehensive training manuals!



Whether you want to learn the basics of electricity, the theory of electronics, or advanced digital technology, our lab kits are for you! Starting with our PL130, we give you 130 different electronic projects, together with a comprehensive 162 page learning manual. A great start for the kids...young and old!

For the latest lab, check out the PL200! Its unique design has an integral front panel that includes controls, meter, display and more for full control of your projects!

Not enough? Next is our PL300, which gives you 300 separate electronic projects along with a 165 page learning and theory manual. The PL300 walks you through the learning phase of digital electronics.

If you're looking for the ultimate lab kit check out our PL500. Includes a whopping 500 separate projects, a 152 page starter course manual, a 78 page advanced course manual, a hinged easy to carry case, and a 140 page programming course manual! The PL500 covers everything from the basics to digital programming! Learn about electronics and digital technology the fun way and build some neat projects! Whichever one you choose, you will have hours of enjoyment!

PL130 130 In One Learning Lab Kit

\$49.95

PL200 200 In Super Fun Learning Lab Kit

\$69.95

PL300 300 In One Complete Learning Lab Kit

\$89.95

PL500 500 In One Advanced Learning Lab Kit

\$219.95

MORE than just friendly on-line ordering!

Clearance Specials, Ramsey Museum, User Forums, Dealer Information, FAQ's, FCC Info, Kit Building Guides, Downloads, Live Weather, Live Webcams, and much more!

www.ramseykits.com

800-446-2295



590 Fishers Station Drive
Victor, NY 14564
(800) 446-2295
(585) 924-4560

Where
Electronics
Always Means
Holiday Fun!

♦ Build It!
♦ Learn It!
♦ Achieve It!
♦ Enjoy It!

Prices, availability, and specifications are subject to change. According to Robin, we're not responsible for typos, mistakes, stupid, and tryptophan sleep comes from the turkey, and she writes the rules! Visit www.ramseykits.com for the latest pricing, specials, terms and conditions.

Copyright 2009 Ramsey Electronics, LLC... so there!

Q&A

WHAT'S UP:

Join us as we delve into the basics of electronics as applied to every day problems, like:

- ✓ Fish Feeder
- ✓ Ferrite Core Search
- ✓ Bat Detector

■ WITH RUSSELL KINCAID

In this column, I answer questions about all aspects of electronics, including computer hardware, software, circuits, electronic theory, troubleshooting, and anything else of interest to the hobbyist. Feel free to participate with your questions, comments, or suggestions.

Send all questions and comments to:
Q&A@nutsvolts.com

TRANSISTOR QUESTION

Q I was curious about basic semiconductors like diodes, rectifiers, and transistors. I knew that a switching transistor was an NPN junction and that diodes are PN. I was wondering if you could make an NPN transistor out of two diodes (NP-PN)? This should make a NPPN junction which would be the same as NPN.

— **A. Lingenfelter**

A I am sure that what you really want to know is why that does not work. Here is why: The P region has to be very narrow so electrons can transit across it. Current from the emitter (N) to the base (P) enables a greater current from the emitter (N) to the collector (N).

FLASHING LIGHT ALARM

Q Would you please tell me how to change a digital alarm clock from the existing piezo electric buzzer to a flashing 60 watt bulb? We are very hard of hearing and our existing KEN-TECH clock quit. It used to flash a screw-in bulb. New clocks we've seen don't have an outlet for a bulb. Thanks for any help you can give.

— **Frank Lemon**

A Opening the clock and finding the switch that turns on the buzzer might be difficult, so I think the best solution is a microphone sensor to operate the bulb. A VOX kit from Ramsey Electronics will do the job but you will also need a power supply, power socket, and relay. If you have a 12 VDC, 200 mA wall wart in your junk box, that will do, and you may find the power socket and relay at RadioShack. Otherwise, the parts list below will work.

VOX kit \$9.95 part no. VS1
www.ramseyelectronics.com

Wall wart \$13.89
418-TR1512-01-12 (2.5 MM plug)
Power socket \$0.87
16PJ221 (2.5 MM)
Relay \$3.58
817-FTR-MYAA012D
www.mouser.com

CYLINDER HEAD TEMPERATURE MEASUREMENT

Q Several years ago, I read an article on how to use a silicone diode attached to an airplane engine cylinder head for temperature measurements. I can't remember what publication I read the article, or what year it was,

and Google doesn't find any information.

Do you have any ideas on how a standard diode could be used to measure temperature while it is physically attached to a cylinder head? I always enjoyed the Q&A section by TJ Byers, and you are doing a fine job following his lead. Please keep up the good work!

— **Larry Kraemer**

A A silicon diode has a temperature coefficient of about -2 mV per degree C. For best accuracy, you would measure the diode voltage at several temperatures and draw a curve or use a lookup table.

Another option is to use an LM34 (10 mV per degree F) or LM35 (10 mV per degree C) temperature to voltage sensor. You can read the temperature directly on a DVM. The operating range is -50 to +300 degrees F.

FISH FEEDER PROJECT

Q I have to build an automatic fish feeder for my final project. I am using an 8051 microcontroller, seven segment to display the time, pushbutton to set the time, toggle switch for on-off, and a DC motor. I am now confused to build the circuit and hope you can help me.

— **Naim Romero**

A The 8051 is a 40-pin DIP with four 8-bit ports; you will have plenty of outputs for your project. The circuit is no problem, the program is what will take time and study; I can't help you with that. You only want to feed the fish once per day and the fish don't care what time it is, so I don't see the need for a display. However, if it is part of the project, you could use a 7447 BCD to seven segment decoder/driver or code the driver in software.

The pushbutton

could advance the time in hour increments until you get to the desired time to start the feeder. You will need two digits for a 24 hour display. How you drive the motor will depend on the means of delivering the food. I would expect the motor to only turn once to dump a load, so a cam and microswitch could signal that the motor should stop. A gear reduction motor that turns very slowly is indicated.

A possible circuit diagram is **Figure 1**. I show two 7447s assuming you will code the two seven segments separately rather than multiplex them because there are plenty of ports. I show inputs to port 0 because my limited perusal of the datasheet indicates that port 0 can

be an input. Q1 is a 100V, 10A logic level MOSFET (overkill but cheap). Your program will have to acknowledge that S3 (the microswitch) is closed and wait for it to open and close. There is an Intel forum that may be helpful, and the 8051 code set can be found here: www.atmel.com/dyn/resources/prod_documents/doc0509.pdf.

Good luck on your project.

FERRITE CORE SEARCH

O I am looking for Philips ferrite core, part number RM8RA250-3B9. Could you please help me find a

source to get that core or a replacement?

— S. Karas

A Philips ferrite operations were bought by Yageo which also owns Ferroxcube, so I queried Juan Carlos Gardea of Ferroxcube. He says the RM8R number is not good and 3B9 material is obsolete. Juan suggests that RM8-I-3H3-A250 or RM6R-3H3-A250 would be equivalent. Apparently, 250 is the Al in nH per turn and 3H3 is the material which is low loss and good for filter applications below 2 MHz. Unfortunately, there is no distributor for small quantities but you may be

MAILBAG

Dear Russell:

Re: Antenna Question, September, '09, page 30. The answer given to the question about "passive" AM antenna (boosters) kind-of strayed from the mark! What the originator was doubtless referring to was the large coil/tuning capacitor in a box that you place next to an AM table or portable radio.

This is simply a re-radiating, resonant, L/C circuit where the large coil can intercept more signal off the air than

a small radio's internal loopstick. Inductive coupling sends this larger signal into the radio. Tuning the capacitor in the booster peaks the desired station's signal. The comments about a "quarter wave dipole" (non-existent) made me grin. The answers about digi and high tech stuff are usually right on point, but antenna and RF basics???

Respectfully,

— John W. Davidson
Certified Wireless Technician
ETA International CET
Amateur Extra Class Ham

Response: Thanks for writing. I admit my answer did not answer the question; I had never run across such a thing as a passive signal booster and doubted that it would work. After reading your message, I built one to try it. I wound 20 turns #24 insulated hookup wire on an oatmeal box (five inches diameter). The tuning capacitor was a variable, 65 to 650 pF. I put the coil (horizontal) next to my portable radio and tuned in a weak station near 1400 kHz. Surprise! It works! I got a noticeable increase in signal by tuning the variable capacitor.

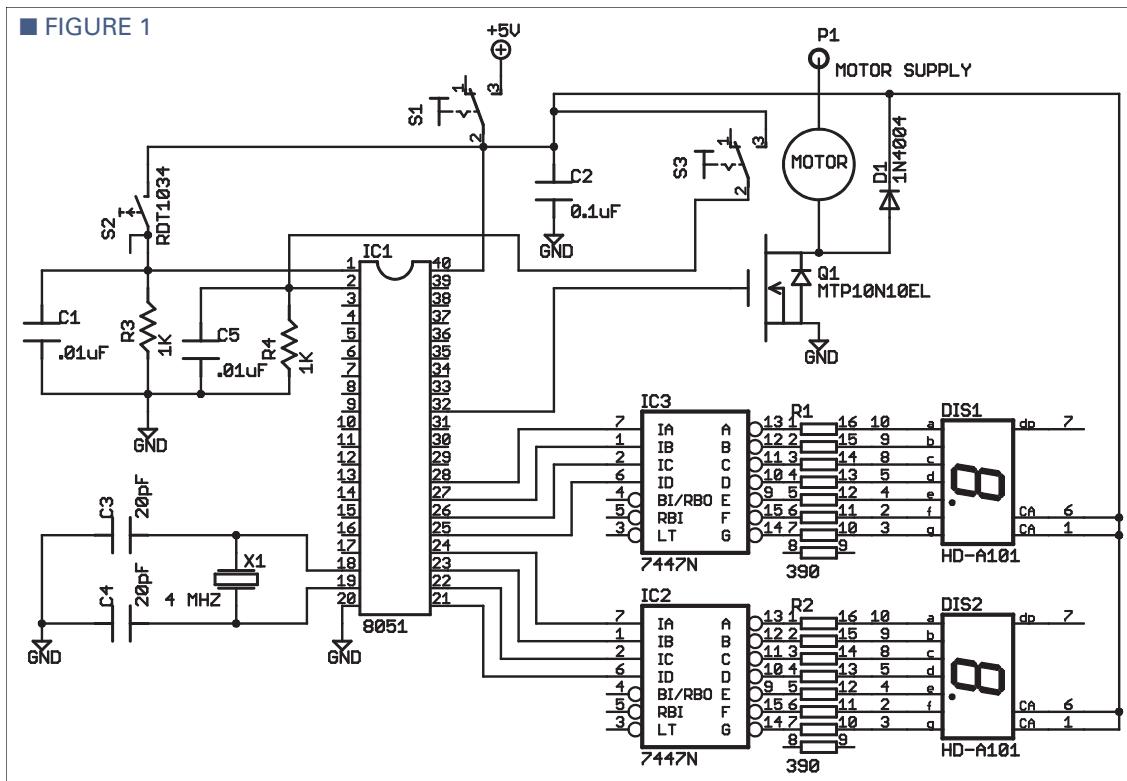
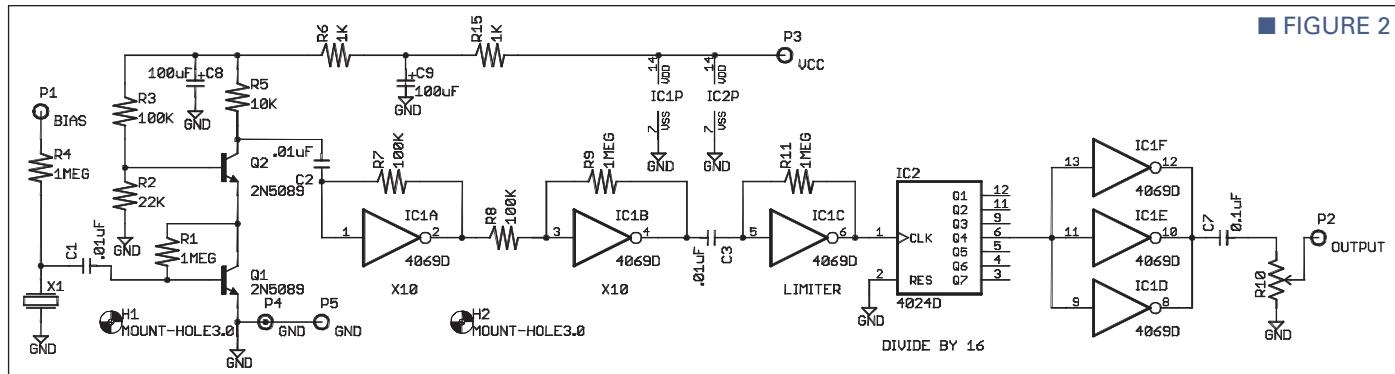


FIGURE 2

able to get a few from your local sales rep; see www.ferroxcube.com/cont/nasals.htm.

BAT DETECTOR

Q I'm trying to build an ultrasound bat detector. I've located a reasonably priced electrostatic transducer (SensComp 600 series; www.senscomp.com) with good frequency response and sensitivity. What I haven't been able to find is a suitable bias circuit (manufacturer recommends 200V) and preamp. I want to use a limiter and 16:1 frequency divider to bring the received calls down to audible range. This will be a portable detector with a 12V battery so power use

BAT DETECTOR PARTS LIST

PART	DESCRIPTION
R1 – R11	CARBON FILM, 5%, 1/4 W
R10	10K AUDIO TAPER
C1, C2, C3	0.01 μ F, 50V, 10%
C7	0.10 μ F, 50V, 10%
C8, C9	100 μ F, 16V
Q1, Q2	NPN, HI GAIN, 2N5089
IC1	HEX INVERTING BUFFER
IC2	CD4024 seven STAGE COUNTER

PART #
291-(value)-RC
313-1510F-10K
80-C322C103K1R
80-C3220C104K5R
871-B41827A4107M000
512-2N5089TF
512-CD4069UBCN
595-CD4024BE


should be minimal.

— Richard Duncan

A I built an ultrasound detector many years ago but it used a mixer to beat the frequency down to audible range. Dividing by 16 provides a wider audible frequency range but you lose some of the characteristics of the original sound. The electrostatic transducer output will be proportional to the bias

voltage and should be adequate at 12 volts. I built the circuit of **Figure 2** using nine volt battery power (a separate battery for the transducer bias) but did not have time to test it. I had to tweak the value of R1 to get the DC voltage at the Q2 collector in a linear range (3 to 5 volts). I looked for the proximity detector lamp that I used for the deer scaring circuit but did not find it. I planned to remove the sensor and use it in this circuit.

The electrostatic transducer is a current source so a current amplifier is indicated. The preamp is a cascode circuit because the low input impedance gives minimum noise and the gain-bandwidth is better than a single transistor. I expect the signal at the Q2 collector to be 10 millivolts with the lowest amplitude input. The CD4069 is a simple inverter that is stable with feedback and makes a good, low noise op-amp. I paralleled three of the inverters to provide more drive to the output. Each inverter is only guaranteed to drive one TTL load. I expect you will use high impedance earphones, 8 ohm earphones; won't work very well. The parts list is **Figure 3** (all Mouser part numbers). The circuit I built was all surface-mount but the parts list is all through hole parts.

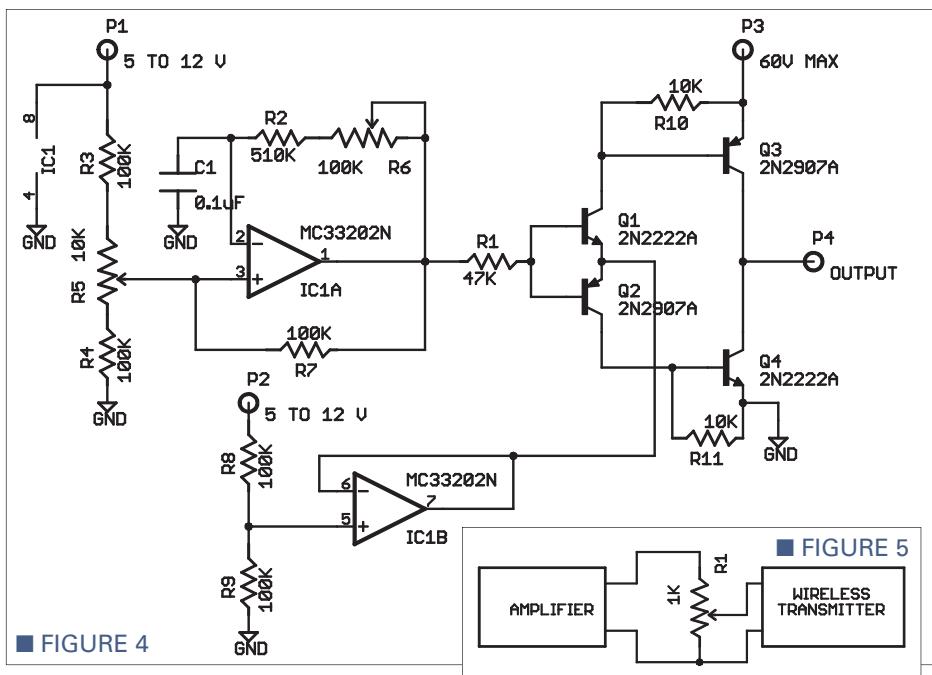

■ FIGURE 4

SQUARE WAVE GENERATOR

OI have a question: How do I generate a square waveform with 24V (not pk-pk), 15 Hz by using an op-amp? I have used an op-amp push-pull amplifier, but the frequency response of IC741 is limited. What to do?

— Anonymous

AThe frequency response of the 741 is not limited at 15 Hz unless you are trying for very high gain. The 741 is no doubt slew rate limited at 24 volts amplitude. I assume you want zero to 24 volts signal which will require a VCC/2 DC reference as in **Figure 4**. The IC1A circuit is a square wave generator. If the op-amp output is positive, C1 charges through R2 until it reaches the bias voltage on pin 3. When the charge on C1 reaches the bias voltage on pin 3, the op-amp output goes negative and the positive feedback through R7 pulls the bias voltage lower. C1 now charges down to the bias voltage on pin 3 at which point the op-amp output switches high. The high and low of the op-amp output has to be symmetrical about the bias voltage set by R5 in order to have a

symmetrical square wave. The MC33202 has rail to rail output so the R5 trim is minimum, but if an LM358 or UA741 is used, more trimming of R5 will be needed. R6 is

a frequency trim to compensate for component tolerance.

SIGNAL ATTENUATION

OI would appreciate your assistance with my problem in using a Sennheiser TR130 wireless headphone with a Philips DVD Micro Theatre MCD708 set which does not have a headphone outlet. The problem is in attenuating the output from the speaker outlet to the normal level for headphones. The volume control is inadequate for this purpose. Ideally, I need a self-regulating circuit for use between the speaker outlet and the headphone transmitter.

— Bert Williams

AI suggest a volume control between the amplifier output and the wireless transmitter (Mouser part #31VJ301-F); see **Figure 5**. **NV**



\$54.95
ASSEMBLED

UK1133
45A Digital PWM Motor Speed Controller
Optional LCD Module: \$17.95



\$39.95
ASSEMBLED

UK670CY
Digital Cyclic PIC Timer



\$34.95

CK1301
Mini USB PIC Programmer with ZIF Socket
Assembled: \$49.95



\$59.95
ASSEMBLED

UK1104
4-Port USB Relay Controller with 6-Channel Analog/Digital Interface

FM Transmitters • Timers • Audio Amplifiers • Motor Controllers • Custom Designs

www.canakit.com


1-888-540-KITS (5478)

NEW PRODUCTS

- HARDWARE
- SOFTWARE
- GADGETS
- TOOLS

JRK USB MOTOR CONTROLLER WITH FEEDBACK

Pololu announces the release of the jrk line of USB motor controllers: highly configurable, versatile devices that make it easy to add open- or closed-loop control of brushed DC motors to your computer- or microcontroller-based project. The jrk supports four interface modes: USB for PC-based control; logic-level (TTL) serial for use with embedded systems; analog voltage for simple potentiometers and joysticks; and RC pulse for radio control systems. It can perform open-loop speed control, closed-loop position control with analog voltage feedback to make your own servos, and closed-loop speed control with frequency feedback from a tachometer. The jrk 21v3 — the smaller of the two units currently available — has an operating range of 5-28V and can deliver 3A continuous output (5A

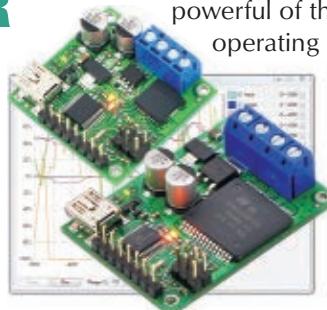

peak). The jrk 12v12 — the more powerful of the two — has an operating range of 6-16V and can deliver a continuous output of 12A (30A peak). Both devices can handle transients of up to 40V. A free configuration

program (Windows XP and Vista compatible) is available for calibrating your system. Real-time plots of variables such as control input, feedback, motor output, and current draw make it easy to fine-tune settings such as PID constants, acceleration, and current limit for your application.

The unit price is \$49.95 for the jrk 21v3 (item #1392) and \$99.95 for the jrk 12v12 (item #1393).

For more information, contact:
Pololu Corporation
 Email: www.pololu.com
 Web: www.pololu.com

NEW INNOVATION EZP-01



Edsyn Hummerworks' newest innovation — the EZP01 easy probe tweezers — all-in-one test probe/tweezer that can plug directly into a meter. Made of 301 stainless steel, the EZP01 has a very unique working surface, as well as:

- Dual pickup points — like a normal tweezer.
- Surface ground to handle the very smallest components on one edge.
- A wide edge for handling larger components with stability.
- A spacing wheel that allows the user to set a defined gap that reduces squeeze travel and can hold parts from the inside or outside.

In addition, a clear retaining cap in the back slides off easily to allow the user to separate the tweezers into a pair of independent probes. This is done without the need to remove the probes. Moreover, the spacing wheel allows the user to set a gap to a specific point so repetitive tests on multiple boards are made much easier and accurately — perfect for calibration or monitoring jobs.

For more information, contact:
EDSYN
 Web: www.edsyn.com

If you have a new product, please email a short description and a photo of your product to:
newproducts@nutsvolts.com

BUDGET ROBOTICS

THE BIG GRIPPER

SERVO-OPERATED GRIPPER WITH THREE-INCH FINGERS

- Fingers open to over 3" wide
- Rubber finger tips for extra traction
- Available with or without servo
- Included servo works with microcontroller or RC receiver
- Solid construction using injected-molded plastic for fingers, and 1/4" expanded PVC
- Easy to mount to your robot or another servo to create a wrist or arm
- Versatile design
- Build in 20 minutes or less

Just \$28.95!
 Version without servo only \$18.95

GREAT ROBOTS. GREAT PRICES.

www.BUDGETROBOTICS.COM

SHOWCASE

ezLCD – The “Smart Display” Makes integrating a GUI ez!



Call for Custom
Display Configurations

earthlcd.com

8.0" ezLCD
p/n. ezLCD+105
Versatile Programmable
LCD module ■ USB, SPI,
RS232 Interfaces ■
Bright 250 Nit LED
Display (800x600) ■
Integrated Touch
Screen ■ LUA Scripting
Language capable-
For stand alone
embedded applications ■
Memory 3.8 MB +
SD to 2G ■ ezLCD's
are also available in 2.7",
3.5", 5.6", 6.4", 10.4"

Adapt9S12DP512 Our most popular board ever!



Evaluate * Educate * Embed
www.technologicalarts.com

USB Oscilloscope for \$169.50

8+8 digital + 2 analog channels

Oscilloscope - Generator - Logic Analyzer
with UART, SPI, I2C and 1-Wire interfaces

Great for PIC and AVR projects!



www.HobbyLab.us

QKITS.COM

Power Supply:
12/24VDC
Load Voltage

**30A PWM DC Motor
Speed Control**
Control the speed of
your electric motors or
the brightness of your
DC light bulbs.

\$24.95



Quantity discounts
available.
1-888-60-4-KITS

ActiveWire® USB Simple USB Interface!



• Works with Mac OS 8.6, Win98/2K/ME/XP
FreeBSD and Linux!
• 24MHz CPU core with USB
• Firmware downloadable via USB
• 16 bit parallel Input/Output
• See web-site for add-on boards
• All drivers, manuals, demos are on our
web-site for immediate download!

\$59
plus shipping

ActiveWire, Inc.

www.activewireinc.com

ph +1.650.465.4000 fax +1.209.391.5060

www.Primecell.com

Battery rebuilding service

Dead Batteries? Don't toss them.
Send them to us - our rebuilds are
better than original specifications.



Tools
Hilti - Skil
Milwaukee
Panasonic
B&D DeWalt
Makita - All
2-36 Volts

Electronics
Bar Code
Scanners
Surveying
Printers
Laptops
Photography

Radios
APELCO
UNIDEN
G.E. ICOM
KENWOOD
MOTOROLA
MIDLAND
MAXON
YAESU
ALINCO

Visit www.primecell.com for important details
24 Hr Secure recorder tel-fax (814) 623 7000
Quotes email: info@primecell.com
Cunard Assoc. Inc. 9343 US RT 220 Bedford PA 15522



I2C RGB "Smart LED"



USB - BT - XBEE



Prototyping Supplies



Serial LCD

Save 5% with coupon code NV
FunGizmos.com

Celebrating Our 10th Year Anniversary

ALL IN ONE Scope & Generator!

USB PC Oscilloscope & Function Generator
(PCSGU250)
\$238.55



USB PC
Function Generator
(PCGU1000)
\$242.85



USB PC
Oscilloscope
(PCSU1000)
\$298.99

DesignNotes.com

What Your Electronic Hobby Stores Used To Be

1-800-957-6887

www.DesignNotes.com



Display text and graphics from
your microcontroller on standard
TV monitors with BOB-4H.



DECADE ENGINEERING

Ph: 503-743-3194 | www.decadenet.com



**Frequency
Counters**
since 1988
made in USA

www.STARTEK-USA.com

Do you know how many watts
(YOUR MONEY)
are going down the drain from
"THE PHANTOM DRAW?"

The KILL A WATT
meter is the
best way to help
you determine
your actual
energy draw
in ON and OFF
home appliances.

To order call 1 800 783-4624
or online www.nutsvolts.com
\$29.95 plus S&H





COMPUTER TO COMPUTER LINK USING LASER POINTERS

BY ED RINGEL

Readers of this magazine know that broken stuff can sometimes be an inspiration, not necessarily a disappointment. So it was with a giveaway laser pointer from a drug company. The plastic housing broke, leaving the laser module and a primitive switch mechanism. Hmm...

It turns out that it is extraordinarily easy to establish serial communication between computers (or microcontrollers) over the low power red laser modules used for pointers, carpenter's levels, and the like. It is also very inexpensive. Easily sacrificed, the modules from these pointers can be readily extracted and used for this purpose.

Aside from the laser module, each half of the communication module requires only three bipolar transistors, a phototransistor, a few resistors, one pushbutton switch, and a cheap mainstream IC.

This is a fun project, but be safe!

As with all laser projects, a word of caution is in order. The modules used are classified as Class IIIa lasers, with output fixed at < 5 mW. These are pretty safe as lasers go. Nonetheless, misuse can cause injury to the eye and can be illegal. Staring at the beam can cause retinal injury. Never, ever further focus the beam using optics unless you really know what you are doing. Shining a laser at an airplane is illegal and aiming a laser at a car is stupid. Safety goggles are appropriate. Enough said.

What do we need to know before we start?

Laser modules consist of the laser diode, power regulating circuitry, optics, and the casing. Laser diodes are operated at the extremes of the thermal and power curves for the semiconductor. There is usually a photodiode in the unit that monitors the output of the laser and provides feedback to the power regulation circuitry to prevent runaway. Optics collimate the beam (usually just a cheap plastic lens), and the metal casing dissipates heat. My initial concern in this experiment was that the on/off time for the laser unit would be too long, but it is possible to achieve 4800 baud communication. All that internal output regulation occurs very, very rapidly.

The unit stays cool, and the waveforms are sharp enough to meet serial port encoding standards.

The other piece of background has to do with phototransistors. This class of semiconductor develops current with illumination. Illumination of a phototransistor with a red laser produces a very robust response which under my experimental conditions dropped effective resistance by at least a factor of 10 (and sometimes more) in room light. This is more than enough of a change to be easily detected by a comparator. The rise time and fall time of current across the semiconductor junction with application of light is fast and can meet serial port encoding standards with the correct choice of parts.

The Basic Layout

I chose to implement communication using the conventional serial port/RS-232 encoding protocol. There were several reasons for this. First, both computers and microcontrollers have extensive hardware and software for this protocol and I would not need to reinvent the wheel. Second, speed of transmission was easily varied; if there were difficulties with maintenance of communication I could simply slow down the speed of transmission. Third, it was binary. The protocol requires no analog modulation of the signal (amateur radio types – no frequency modulation or phase modulation a la PSK-31, and much, much faster), improving reliability and ability to detect a low level signal.


I also chose to route the communication through microcontrollers. There were three major reasons for this. The first was protection of the computer. If I bungled this, I'd trash the Arduino, not the Dell. The second was extensibility. If I could establish communication between the microcontrollers, there would be a general solution that could be applied to both microcontrollers and computers. Third, use of the microcontroller permits addition of some extra functions that would require significant additional programming on a computer. These extra functions

(discussed below) simplify alignment of the units and initiation of communication.

Data flow is shown in **Figure 1**. Using a terminal program on the PC, the information is communicated through a true or virtual serial port to the microcontroller. Data is handed over within the microcontroller from the UART serial port in communication with the PC to the UART serial port in communication with the laser. The TX pin is connected to a simple bipolar transistor. I used a 2N3904 which is appropriate for radio frequency, low level signals; it certainly could handle this task. The transistor is essentially slammed on and off producing current flow which, in turn, drives the laser module. A second transistor is configured as a discrete component's inverter. This reduces the duty cycle of the laser considerably. No other circuitry is required for transmission. TX/RX signals go high (zero) to low (one). Thus, the quiescent state of the laser is on which uses energy and increases the likelihood of misadventure with the beam. By placing an inverter in the signal path, the quiescent state of the laser is off, and a logical one is high.


Reception is somewhat more complicated. The phototransistor acts as the sensor. The phototransistor is in series with a resistor, effectively creating a light modulated voltage divider. The voltage is monitored by a comparator: an LM311. The LM311 has ample bandwidth. The output of the LM311 is a TTL level signal that is fed to another discrete component's inverter to reverse the effect of the transmitting inverter. The signal is then fed to the RX pin of the receiving microcontroller. Information is handed over to the UART serial port in communication with the computer and relayed to the terminal program on the PC.

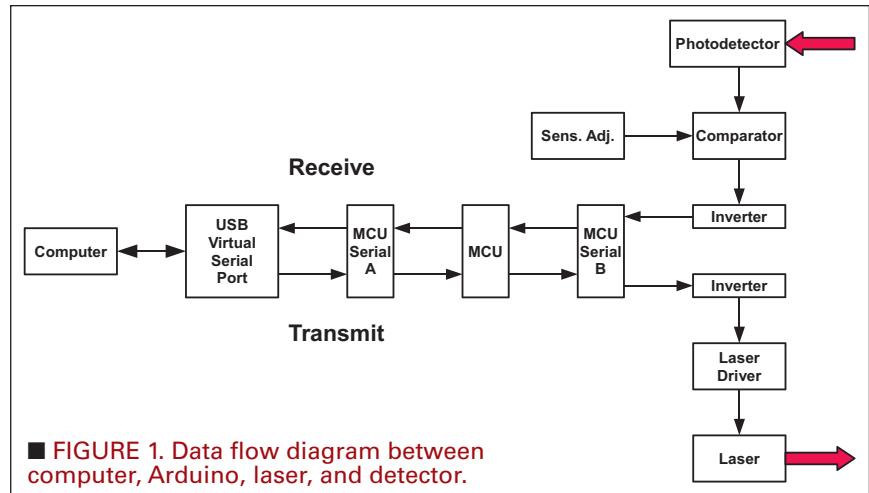Obviously, all forms of information can be relayed; the application is not limited to a terminal program. Additionally, there is no requirement for a computer. The two microcontrollers can easily just talk to each other. **Figure 2** is a schematic of one half of a communication link using an Arduino board.



Why Arduino? Several reasons. First, I really have no objection to C and its derivatives. Folks don't like C because hot dog programmers can write incomprehensible code if they want to. However, if the author so chooses, it is possible to write code in C that is as clear as a Pascal program written by Nicklaus Wirth. Second, people don't like C because it is associated with down and dirty coding; if you are writing in C you must be manipulating data bit by bit.

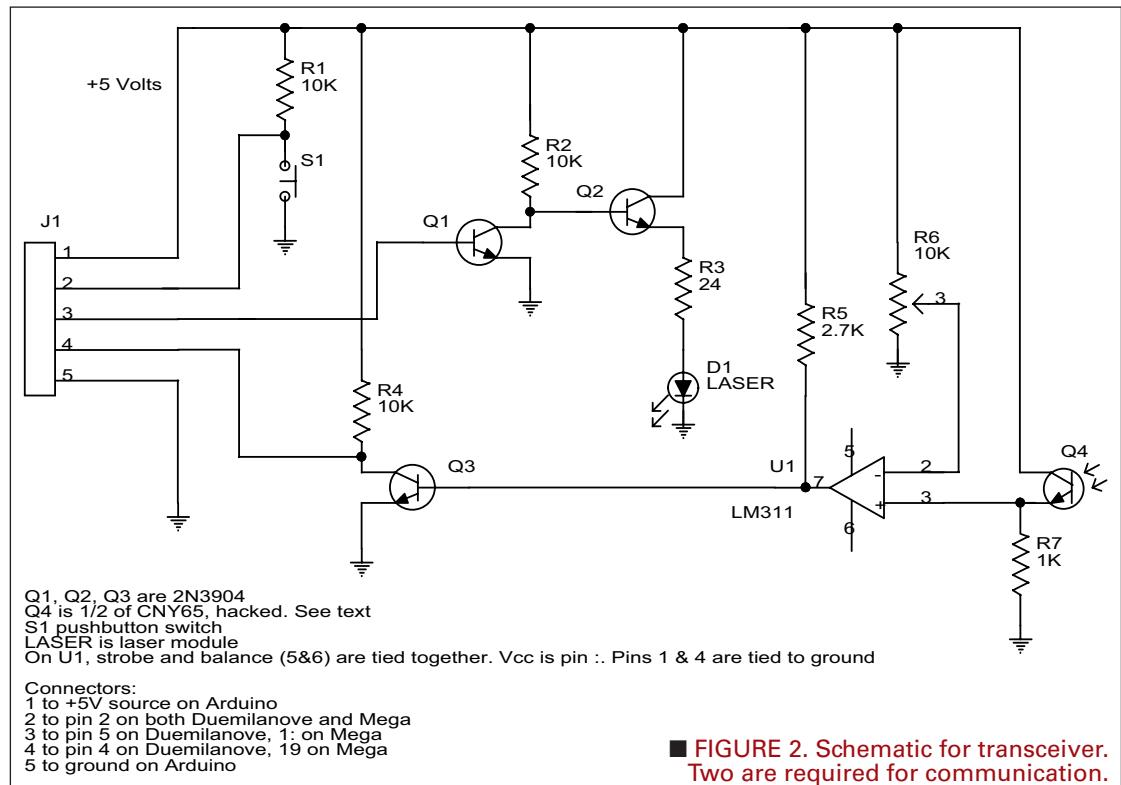The Arduino environment provides a very high level of abstraction that permits the programmer to complete the task rather than code. Second, there is a huge open source community that shares code, tips, and tricks. It is a very rich environment. I have learned a lot of both



In Practice

If you are not familiar with the Arduino, check out Smiley's Workshop that runs in NV each month. It will introduce you to this system. To use the communicator without further modification, build the board, install the Arduino software, let Windows install the virtual serial port, and choose the target board. Hook up the target board. Copy or enter the code, press compile, and then press download to board. Software setup is less than 30 minutes.


The system requires two adjustments in order to function. The first – and by far the most difficult – is aiming the laser to hit the phototransistor square on. I do not have a foolproof method for doing this. I mounted my communication units on some scrap lumber (Figure 3), then I mounted the laser unit within a ball joint type plastic shower head for even more control (Figure 4). Consideration could be given to mounting the unit on a camera tripod for even greater aiming control.

The other adjustment is setting an offset for the comparator. Depending upon ambient light, the baseline current of the phototransistor may vary considerably, and depending upon the distance from the laser to the detector, excitation may vary considerably. The negative input of the comparator is attached to a potentiometer which permits setting the comparison voltage, which enables extraction of the data. This is a simple adjustment.

Building It

The electronics are easy. I recommend point-to-point wiring on a piece of perf board. The component count is so small that the work involved does not justify a printed circuit. If you wish to be particularly careful (which I heartily recommend), attach a five volt source to Vcc and Vgnd and sniff for smoke before hooking up the Arduino. Apply a five volt signal to the base of Q1 and make sure the laser is working. If you have a multimeter, set the negative input of the comparator at approximately 1-1.5 volts. Even with the laser on, total current draw should be well under

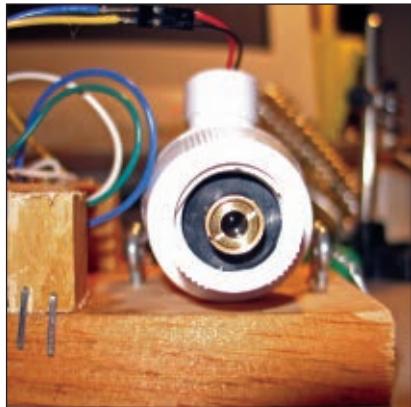■ **FIGURE 4.** Close-up of laser mounted in showerhead. The showerhead articulates in a ball and socket fashion. This particular model of showerhead had a gasket which permitted a press fit of the laser unit without further modification. Other heads may require glue or creation of a sleeve around the laser to allow a press fit. Wires follow the water path.



■ **FIGURE 5.** Close-up of photodetector consisting of hacked CNY65 optocoupler. With chip text correctly oriented for reading, as you face the chip the left side of center houses the emitter and the right side contains the detector. Using a tiny burr or milling tip, carefully start on the left of center of the chip and remove the black plastic until a white matrix is identified. On the left side of the matrix, continue to remove material until a small translucent cube is identified. This is the emitter. The detector looks almost exactly the same. Now that you know what to look for, carefully remove as much white matrix from around the detector as possible without destroying the detector plastic. This is actually quite easy, and the end result should be similar to the photo here. Only the two right side pins need to be connected. The upper right pin is high. Other optocoupler chips likely have a similar mechanical construction, but I cannot confirm that (follow schematic for appropriate hookup).

LASER SERIAL ARDUINO MEGA.TXT

```

// Use with Arduino Mega and other Arduino
// types that have multiple hardware serial ports

//used for receiving/sending characters
int scratchByte;

void setup (){
//Initialize Arduino<->Computer port
Serial.begin(9600);
// Initialize Arduino <-> Arduino port
Serial1.begin(4800);
// Attach interrupt routine to Interrupt 0 on pin 2
attachInterrupt(0, Align, CHANGE); // this is pin
2; use 4.7k pullup resistor
}

void loop (){
// if data from computer available, pass to laser
if (Serial.available() > 0){
scratchByte = Serial.read();
Serial1.print(char(scratchByte));
}

```

```


}

// if data from LED available, pass to computer
if (Serial1.available() > 0){
scratchByte = Serial1.read();
Serial.print(char(scratchByte));
}

void Align(){

pinMode(2,INPUT);
while (true)
{
Serial1.println("ABCDE");
Serial1.println("FGHIJ");
Serial1.println("KLMNO");
Serial1.println("PQRST");
Serial1.println("UVWXY");
Serial1.println("01234");
Serial1.println("56789");
if (digitalRead(2)==HIGH)
break;
}

```

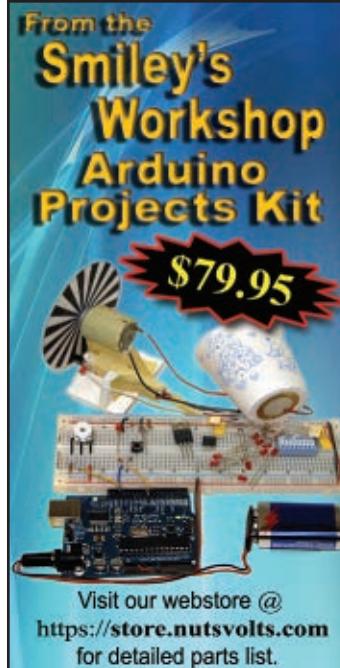

50 mA. The Arduino board has clearly marked Vgnd and +5 volt sources and they should be connected appropriately.

Output of the comparator should go to your RX pin via Q3, and Q1 should be connected to Q2 which, in turn, should be connected to the TX pin. Specific pins may vary depending upon the Arduino (or your favorite microcontroller) and how you configure your software serial port. I deliberately did not construct this unit as a shield because of the wide variety of board formats now available.

When I thought of this project, I did not have a phototransistor on hand. However, I did have a couple of optocoupler ICs left from another project. Careful work with a Dremel tool permitted me to remove the plastic and I was able to expose the semiconductor; it took all of about five minutes to do and worked very well (Figure 5). I also completed the project using a conventional phototransistor. Interestingly, the hacked optocoupler (CNY65) was much easier to adjust, and was my ultimate sensor. After reviewing product specs, I concluded that the key design parameter is rise/fall time. The hacked optocoupler is a digital, high speed device, whereas the phototransistor is a sensor. Faster is better.


Mechanical construction is a bit more challenging. If you are just going to do this over a tabletop, aiming and aligning the two units is not a big deal. If you are going to try this over several hundred feet, you need to be able to aim your laser with some precision. I suggest attaching the Arduino board and your communication board to a photo tripod. The laser itself is mounted in a plastic showerhead. This permits further manipulation of the beam independent of the tripod which may be necessary for the best signal. Depending upon the laser unit you use, some ingenuity will be necessary to provide firm mounting while retaining the ability to aim. Other ideas I entertained included a pair of helping hands.

Using It

Once you have built the two units, place them so that they are aligned as best as possible without turning the units on. If you are doing this over a distance, you may want a friend to help, and you may want to use a cell phone or short range radio to communicate with the friends. Binoculars can also be helpful. *Don't look at a laser beam coming at you using binoculars; use them only for locating the laser spot in relation to the phototransistor.*

Once manually aligned, attach the Arduino to the computer and the communication board to the Arduino. Start the terminal program of your choice and establish communication through the virtual serial port with the Arduino at 9600 baud. Now, press the button you labeled

■ **FIGURE 6.** This is an alternative front end for the photodetector. Use a conventional, low luminance non-diffused LED (can be colored, but clear) that emits the same color as the laser. The LED — when illuminated with the laser — produces a very robust voltage but minuscule current. A 2.3 megohm resistor provides enough connection to ground so that the LED is not floating. A very high input impedance FET front end op-amp buffers the signal which is then passed along to the comparator. I used an LM353 for this purpose. While this is a very robust detector, it is even more sensitive than the phototransistor, so it requires a precise direct hit of the beam — an all or nothing affair.

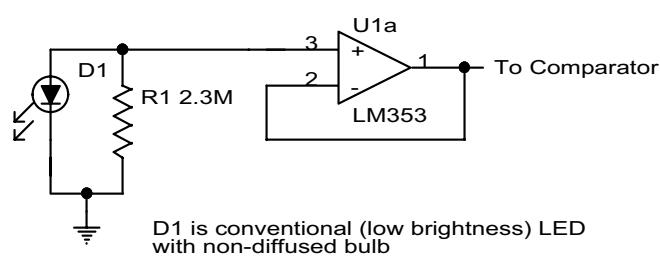

align on the communication board. This causes the Arduino to send 35 characters to the laser: the first 25 letters of the alphabet and number characters 0 through 9. Every five characters a new line command is issued, as well.

The laser will appear to be continuously on. Aim the laser at the phototransistor of the far unit so that you see

the phototransistor clearly and brightly illuminated. At that point, the receiving computer should receive the character stream. If it shows nothing or gibberish, adjust the potentiometer and send another character stream. You may need to do this several times.

If difficulty persists, you need to troubleshoot. Issues

LASER SERIAL ARDUINO DUE.TXT

//Use for Arduino Duemilanove

//NewSoftSerial Library available as a download from the Arduino website

#include <NewSoftSerial.h>

//Instantiate a new instance of the NewSoftSerial Object
NewSoftSerial LaserSerial(4,5);

//used for receiving characters
int scratchByte;

void setup ()
{

```
//Initialize Hardware serial port
Serial.begin(9600);
//Initialize Software serial port
LaserSerial.begin(4800);
//Attaches the interrupt routine below to
Interrupt 0, on pin 2
//There is now no need to poll for button
activity. If the switch is pressed (voltage
goes to zero)
//And then released, the interrupt routine is
invoked with no further programming on
your part.
attachInterrupt(0, Align, CHANGE);
// this is pin 2; use 4.7k pullup resistor
}

void loop ()
{
// if data from computer available, pass to
laser
if (Serial.available() > 0)
{
scratchByte = Serial.read();
LaserSerial.print(char(scratchByte));
// if data from LED available, pass to
```

```
computer
if (LaserSerial.available() > 0){
scratchByte = LaserSerial.read();
Serial.print(char(scratchByte));
}

void Align(){

pinMode(2,INPUT);
while (true){
LaserSerial.println("ABCDE");
LaserSerial.println("FGHIJ");
LaserSerial.println("KLMNO");
LaserSerial.println("PQRST");
LaserSerial.println("UVWXY");
LaserSerial.println("01234");
LaserSerial.println("56789");
if (digitalRead(2) == HIGH)
break;
}
```

Complete Fabrication Center





Quality prototype parts within 24 hours!!

**Precision Laser, Waterjet, Plasma, Machining,
Micro-Machining, Forming, and Welding Capabilities**



**Parts from practically any material and
from 0.001" to 6.000" in thickness.**

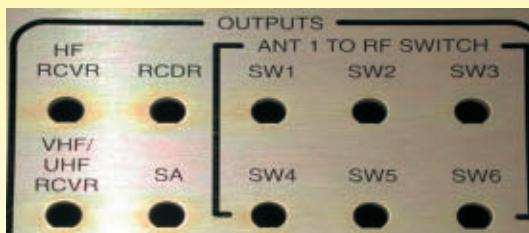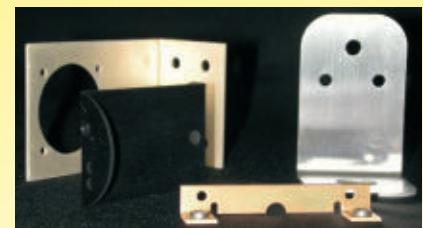**Finishes such as powder coat, paint,
plating, anodizing, silk screen, and
more!**



**Fabricated, silkscreened and
shipped in 2 business days
with no expedite charges!**

- * **Quick**
- * **Affordable**
- * **Precise**
- * **No Minimums**

24 hour turn time based on quantity and finish requirements



Integrated Ideas & Technologies, Inc.
6164 W. Seltice Way • Post Falls, ID • 83854 • USA
Ph (208) 262-7200 • Fax (208) 262-7177 •
www.iitmefab.com

can include misalignment of the laser (shine the laser on the other unit's receiver at close range at least once so you can see what the phototransistor looks like when it is getting properly excited by the laser), electronic malfunction, or distance is too great. Most likely, a back and forth between alignment and comparator adjustment will give you a signal if the two units are less than 100 meters apart. Once aligned, the unit is simply ready to accept serial input data. The default speed of the lasers is set in the code is 4800 baud. Remember that Arduinos do not detect communications settings and both units have to have the laser ports set at the same speed. I have no idea how far apart these things will work.

Code

Code is very, very simple. I used the interrupt feature of the Arduino to detect the button press. This is appropriate for a situation where button presses will be infrequent. For efficiency, I did not want the main loop looking for a state change on the button's pin upon every iteration when activation would be so infrequent. As indicated previously, there are two versions of code: one for the Arduino Mega with multiple hardware ports; and one for the Duemilanove which uses a hardware UART and a software serial port created by the NewSoftSerial library (available by download from the Arduino site).

Areas of Further Investigation

One early experiment was to use an LED as the sensor. Excitation of a conventional (i.e., low) brightness red LED with a red laser beam created a ~1.3 volt potential. From the standpoint of electronics, it worked quite well, requiring a high impedance amplifier to buffer the voltage generated (current generated was tiny). The signal — when present — was quite robust, and once buffered was easy to pass to the comparator (Figure 6). However, from a use/construction standpoint, the LED required a "direct hit" from the laser to generate a voltage. Revisiting this design may be of interest to some builders.

Other ideas to expand on include:

- What is the maximum distance

over which this system can be used?

- Can the electronics be refined to increase sensitivity?
- Can the mechanics be improved to ease alignment procedures?
- What is the maximum data transfer speed?
- Would an array of phototransistors work better (increase target area)?
- Is analog signal modulation possible?

Just remember the whole "point" of this project is to have fun!! **NV**

\$51 For 3 PCBs

FREE Layout Software!

FREE Schematic Software!

01 DOWNLOAD our free CAD software

02 DESIGN your two or four layer PC board

03 SEND us your design with just a click

04 RECEIVE top quality boards in just days

expresspcb.com



PHONE RING-A-THING CONTROL

Several years ago, a friend asked me about the possibility of having a light turn on at his dock site when coming in from night fishing on Lake Ontario. He mentioned using a preset 'timer' but ideally preferred a remote-controlled device and, since he always carried a cell phone, the idea of using that medium for infinite transmission and range was certainly ideal. The question now was providing an appropriate receiver/decoder.

Having a phone installed at his site allowed for the installation of a touch-tone decoder, but this would be over-kill since it was only necessary to turn a light on and/or off. The method I chose was to provide a ring detection device that simply counts the number of rings to perform the on and off functions. The project discussed here has really worked quite well. It simply dials the phone number at the dock site and immediately hangs up as per the ring numbers selected (with "#N: on" and "#F: off").

Take a look at the schematic in **Figure 1**. It indicates the jumpered selected numbers as 'one ring on' and 'four rings off.' Basically, you let the phone ring once for the "#N" time, hang up immediately, then approximately 12 seconds later, the light turns on. To turn the light off, let the phone ring for the "#F" number selected (four, then in this case), immediately hang up. Again, approximately 12 seconds later, the light will turn off. All other ring input counts are

ignored and will not change the pre-existing condition.

A neon bulb (NE1) provides excellent isolation between the circuitry and the phone line because of its high impedance across the ring and tip (red and green) wires within the phone wall socket. However, it makes no difference which wire is connected to either side of the neon bulb for it to light when the pulsating higher voltage ring signal is present.

The neon bulb is soldered to the circuit board, directly connected to the phone line jack via a phone cord having an RJ-11 phone plug on one end and two stripped wire ends soldered to the board on the other end.

Since this project only needs to monitor ring signals (not requiring any data or audio transmissions for it to function), it presents no problem with line loading, which would otherwise be necessary to contend with by using properly designed impedance-matching transformers or opto input circuit configurations.

The photocell (PC1) is placed close to the neon bulb on the circuit board. Each one is soldered in place and formed to face each other so that the photocell receives proper light reception from the neon bulb when the phone rings. Black tape can be used to wrap the two elements together to ensure the best reception.

How It Works

When the phone rings, a pulsating voltage of approximately 60 to 80 volts is present which is sufficient enough to light the neon bulb. The photocell will respond directly to the bulb output, causing a positive pulsating voltage to pass through the anodes of diodes D1 and D2 into their associated timing circuit networks, which are configured with a resistor,

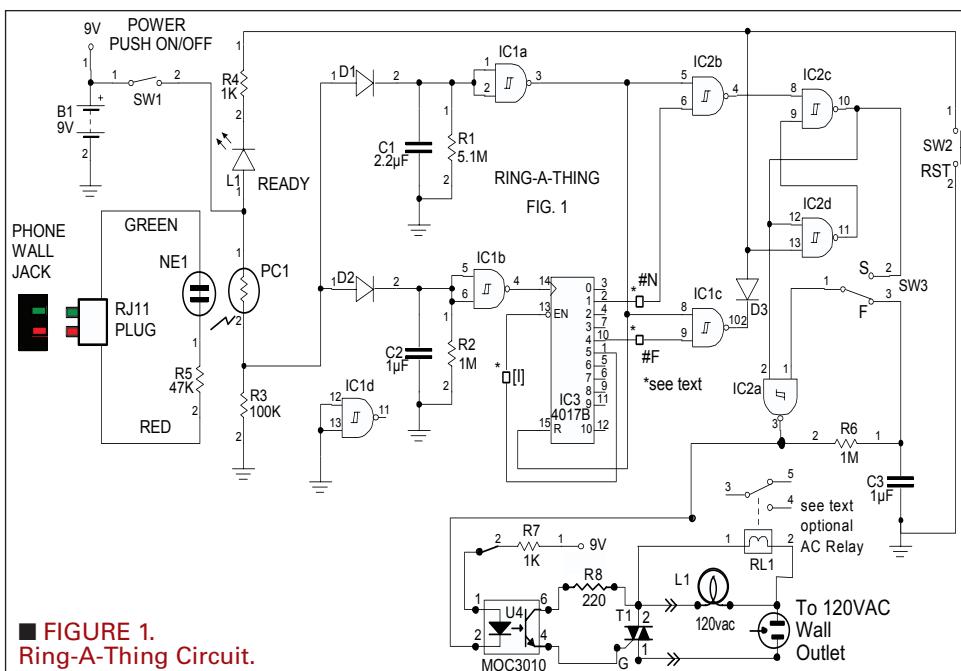


FIGURE 1.
Ring-A-Thing Circuit.

BY JOHN MASTROMORO



capacitor, and NAND gate segment.

Each network is wired to provide a time delay as per the values of the resistors and capacitors. As the positive voltage pulses pass through the anodes of D1 and D2, they are damped and a positive voltage is stored by the capacitors. The diodes now prevent the positive voltage charge from discharging back through their cathodes. The input impedance of each NAND gate is so high that voltage leaks in this manner are not considered. The only convenient discharge path for the stored positive voltage in the capacitors is through the resistors to ground. The amount of charge that the capacitors can hold – combined with the resistance values – determines the discharge rate of the positive voltage to ground. Use the formula $R \times C \times .67 = T$ for your timing requirements.

The component values of $R1/C1$ will provide approximately 12 seconds and 1.5 seconds for $R2/C2$ but – depending on the 4093 IC manufacturer and tolerance values of the components used – it could be slightly different. Since there are no critical timing considerations for circuit operation to be concerned with, the values indicated should be sufficient with any phone service provider as long as the timing cycle of IC1a is longer than one ring cycle to the next, or at least eight seconds.

With a positive voltage applied to each NAND gate timing network (IC1a and IC1b), their normal high-state output pins go low, and remain so during the entire input charging time. Immediately following the absence of an input ring pulse, the capacitors will start to discharge and, when sufficiently discharged through their respective resistors to a ground potential, their output pins go high, indicating the completion of their intended time delay cycle.

Timing circuit IC1b has output pin 4 connected directly



to clock input pin 14 of IC3 – a 4017 1-of-10 output decoder. With the values shown (approximately 1.5 seconds in duration), ample time is provided to allow one input pulse to IC3 per each complete ring cycle; in this instance, causing #1 output pin 2 to go high and remain high. At this exact instance, the timing network of IC1a is being charged and configured to discharge approximately 12 seconds later if no more ring signals were input while discharging.

The IC1a time cycle provides two functions: output pin 3 is directly wired to input pin 5 of IC2b and IC3 output pin 2 (#1) is wired to input pin 6. When both input pins to IC2b are high, then output pin 4 goes low and immediately sets the IC2c/IC2d NAND gate flip-flop at input pin 8. This causes IC2c output pin 10 and input pin 12 of IC2d to go high. Output pin 3 is also wired to input pin 15 of IC3, resetting IC3 to a normal off state immediately after the IC2c/IC2d flip-flop has been set. This turns the light on.

With input pin 2 of IC2a high and switch SW3 in the S position, the light will have a steady glow. If SW3 is in the F position, then the bulb will continually flash since IC2a is wired as a feedback oscillator in this position. Oscillation is determined as per the $R6/C3$ values. Once the flip-flop is set, the light will remain on until reset. This action can be done in one of two ways. Pressing reset switch SW2 places a low voltage on input pin 13 of IC2d, resetting the flip-flop. Diode D3 prevents the low voltage from appearing at IC1c output pin 10 while lighting the ready indicator, LED L1. Switch SW2 provides another function of indicating if the device is powered on. If power switch SW1 is in the on position, it can be verified by simply pressing switch SW2, which will light LED L1 while pressed. Otherwise, LED L1 does not light with the power off.


The other option of resetting the flip-flop is to allow exactly four rings to be entered into IC3, in which case output pin 10 of IC3 (#4) goes high, is inverted to low by IC1c, is passed through the cathode of D3 to pin 13 of IC2d, which resets the flip-flop and lights the ready indicator LED L1 during the reset time period. (Whew!)

That's about it. The ring input counts used here have worked out pretty well. You can select any number of rings you like (from one to nine for either on/off activation), but using a lower number for on and a higher number for off seems to be more practical. Pin 13 (I) of IC3 should be

IC1-IC2	CMOS 4093 Quad two-input NAND Schmitt-Trigger	[13400]
IC3	CMOS 4017 1-of-10 Output Counter	[12749]
IC4	MOC3010 Triac Driver	[26278]
T1	TriacTO-220 400V/2.5A	[1165690]
D1-D2-D3	1N4148	[36038]
L1	Yellow LED Indicator	[34825]
R1	8.2M	[691796]
R2-R	1M	[691585]
R	100K	[691340]
R4-R	1K	[690865]
R	47K	[691260]
R8	220	[661343]
C1-C2	2.2 μ f	[93731]
C3	1 μ f	[29831]
Battery Snap		[109154]
NE1	Neon Bulb	[210315]
PC1	Cadmium Sulfide Photocell	[202403]
RJ11	Phone Line Plug on Wire Lead; Strip Wire Ends	[196227]
SW1	Push On/Push Off Power Switch	[315492]
SW2	SPST PushButton Switch	[174414]
SW3	SPDT two-position Switch	[75969]

All items show Jameco part numbers; www.jameco.com.

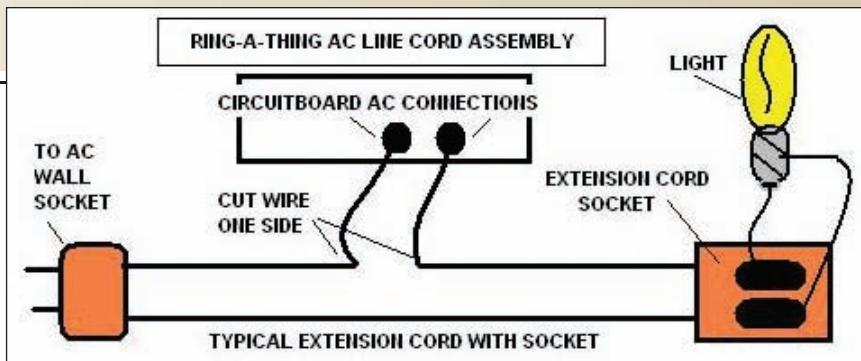Misc: Nine-volt Duracell or Lithium battery; circuit board; IC sockets and terminal strip (optional); 120 VAC light bulb/socket; AC cord/plug; AC relay [see text]; wire; assembling hardware; soldering equipment; appropriate sized enclosure. I do have a number of pre-drilled circuit boards on hand for those interested. Email me at jfmcircuits@frontiernet.net for info.



■ AC Cord Assembly.

the outside world phone line and AC cords to the circuit board. I joined the neon bulb and photocell together with black tape (as mentioned previously), and used a glue gun to seal them and to cover the terminal connections. Wiring is straightforward; and 20 gauge stranded wire throughout will work fine, but solid wire for the three jumper wires is recommended. Recheck

all soldering connections — especially to the IC pins — because any cold solder joints can cause erratic circuit behavior.

Follow the **diagram** included here for AC cord assembly and installation. This project is not recommended for use in a busy phone environment. It's better for remote environments, such as camp sites. Using a land-line cordless phone will let you use your Ring-A-Thing locally and remotely. If your phone service allows you to dial your own phone number, hang up immediately and you can receive call back ringing.

By replacing the light bulb with an AC relay, the Ring-A-Thing can be used in higher-wattage devices such as air conditioners, heaters, or even swimming pool equipment, as well as smaller appliances such as a window fan, coffee pot, radio, TV, garage door, etc. Using a nine-volt Duracell or Lithium battery has provided long, dependable operation but a regulated nine-volt DC power supply can also be substituted for permanent installation. **NV**

jumpered to the next highest unused output pin number to prevent excessive and unwanted ring input counts to IC3. If you have a fax or phone answering machine connected to the phone line, make sure the highest ring number you select is lower than the turn-on ring number for either of the latter devices. Please note that the Ring-A-Thing project shown in the **photo** was assembled with an earlier circuit board layout but the circuit and circuit board design described here are identical in operation and dimension, respectfully. It is assumed that the reader has knowledge of working with AC power.

Construction

The enclosure used is 6" x 4" x 2" which provides ample room to house all the components and battery. Although wires to the switches and LED can be soldered directly to the circuit board, I chose to use a terminal strip between

3pi Robot

Item #975
\$99.95

The Pololu 3pi robot is a high-performance, compact mobile platform featuring:

- * Two metal gearmotors
- * Five reflectance sensors
- * 8x2 character LCD
- * Three user pushbuttons
- * Buzzer and LEDs
- * High-traction silicone tires
- * Speeds exceeding 3 ft/sec using innovative constant-voltage motor supply

All peripherals are connected to an ATmega328P microcontroller running at 20 MHz, with free C-programming tools, libraries, and support for the Arduino environment.

5 reflectance sensors on underside

battery charger connector

4 AAA batteries (not included)

optional power LED

push-on/push-off power button

reset button

user pushbuttons

Pololu 3pi Robot

ISP programming connector

removable 8x2 character LCD

30:1 micro metal gearmotors

robot diameter is 3π cm (~3.7 inches)

**Save 10%
With coupon code
NV3PI44**

Find out more at www.pololu.com/3pi or by calling 1-877-7-POLOLU.


NEW & IMPROVED KITS FOR ELECTRONIC ENTHUSIASTS

UHF ROLLING CODE REMOTE SWITCH

KC-5483 \$58.00 plus postage & packing

High-security rolling code 3-channel remote control that can be used for keyless entry and control of garage doors and lights. Up to 16 transmitters may be used with the one receiver so it's suitable for small-scale commercial applications. The transmitter kit includes a three button key fob case and runs on a 12V remote control battery.

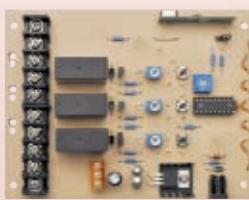Additional UHF Rolling Code Transmitter Kit
KC-5484 \$23.25



SD CARD SPEECH RECORDER & PLAYER

KC-5481 \$43.50 plus postage & packing

Use this kit to store your WAV files on MMC/SD/SDHC cards. It can be used as a jukebox, a sound effects player or an expandable digital voice recorder. You can use it as a free-standing recorder or in conjunction with any Windows, Mac or Linux PC. Short form kit includes overlay PCB, SD card socket and electronic components.



MULTIFUNCTION ACTIVE FILTER MODULE

KC-5480 \$14.50 plus postage & packing

A versatile active filter module that can be used either as an active crossover, a low pass filter, or a high or band pass filter in a speaker project simply by changing a couple of jumper links. Short form kit only with PCB, overlay and all common components. Requires power supply (see specs), amplifiers, and additional components for configuration to PSU and operation frequency.

Input impedance: 47kΩ
Power supply: dual rail \pm 15-60VDC; single rail 12-30VDC or 11-43VAC
Current: 40mA max
S/N ratio: >100dB @ 1V
22Hz-22kHz filter



POST & PACKING CHARGES

Order Value	Cost
\$25 - \$49.99	\$7.50
\$50 - \$99.99	\$20
\$100 - \$199.99	\$40
\$200 - \$499.99	\$60
\$500+	\$75

Max weight 12lb (5kg).
Heavier parcels POA.
Minimum order \$25.

Note: Products are despatched from Australia, so local customs duty & taxes may apply.
Prices valid till 31/12/09



HOW TO ORDER

- ORDER ON-LINE: www.jaycar.com
- PHONE: 1-800-784-0263
- FAX: +61 2 8832 3118*
- EMAIL: techstore@jaycar.com
- POST: P.O. Box 107, Rydalmere NSW 2116 Australia
- ALL PRICING IN US DOLLARS
- MINIMUM ORDER ONLY \$25

*Australian Eastern Standard Time (Monday - Friday 09.00 to 17.30 GMT + 10 hours only)
Expect 10-14 days for air parcel delivery

1-800-784-0263



www.jaycar.com

BATTERY ZAPPER MKIII

KC-5479 \$46.50 plus postage & packing

Prolongs the life of your lead acid batteries. Like the original 2005 project, this circuit produces short high level bursts of energy to reverse the sulfation effect. The battery condition checker is no longer included and the circuit has been updated and revamped to provide more reliable, long-term operation. It still includes test points for a DMM and binding posts for a battery charger. Not recommended for use with gel batteries.

- PCB with soldermask, overlay components included
- Screen printed machined case
- 6, 12 & 24VDC



SLA BATTERY HEALTH CHECKER

KC-5482 \$46.50 plus postage & packing

Checks the health of your SLA batteries prior to charging or zapping with a simple LED condition indication of fair, poor, good etc. An ideal companion to our Battery Zapper MKIII.

- Overlay PCB and electronic components
- Silk-screened front panel and machined case included



FUEL/AIR MIXTURE DISPLAY

KC-5485 \$35.00 plus postage & packing

Displays your car's air-fuel ratio as you drive. Designed to monitor a wideband oxygen sensor and its associated wideband controller. Alternatively it can be used to monitor a narrowband oxygen sensor or for monitoring other types of engine sensors.

- 12VDC
- Double-sided plated PCB
- Programmed PIC
- Electronic components
- Case with machined and screen printed lid



STEREO DIGITAL TO ANALOG CONVERTER

KC-5487 \$80.75 plus postage & packing

Listen to CDs through a DVD player with this DAC kit to get sound quality equal to the best high-end CD players. With stereo RCA outputs, it has one coaxial S/PDIF input and two Toslink inputs. Requires SMD soldering.

- Short form kit with I/O, DAC and switch
- PCB and on-board components only
- Requires PSU
KC-5418 \$11.75
- Requires toroidal transformer




433MHZ REMOTE SWITCH

KC-5473 \$26.25 plus postage & packing

Suitable for remote control of practically anything up to a range of 200m. The receiver has momentary or toggle output with adjustable momentary period. Up to five receivers can be used in the same vicinity. Short-form kit contains two PCBs and all specified components.

Extra transmitter kit: KC-5474
\$13.50

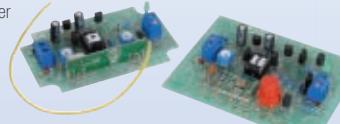

THEREMIN SYNTHESIZER KIT MKII

KC-5475 \$43.50 plus postage & packing

Create your own eerie science fiction sound effects! Updated features to one of our most popular kits include extra test points, change to AC to avoid switchmode plugpack interference, and a new skew control to vary audio tone. Contains PCB with overlay, pre-machined case and all specified components.



FREE CATALOG

Checkout Jaycar's extensive range

We have kits & electronic projects for use in:

- Audio & Video
- Car & Automotive
- Computer
- Power
- Learning & Educational
- General Electronics Projects
- Gifts, Gadgets & Just for fun!
- Lighting
- Test & Meters



For your FREE catalog logon to www.jaycar.com/catalog or check out the range at www.jaycar.com

Jaycar
Electronics

Experiments with Alternative Energy

Part 4 - Build a “Double Wide” Sun Tracker

By John Gavlik, WA6ZOK

This time, the subject of alternative energy is on Sun Trackers: the mechanical devices that keep solar panels pointed at the sun all day. I'll show you how to build one with one or two solar panels along with a low voltage DC geared motor that is controlled by either the Parallax BS2 or PICAXE 28X2 microcontrollers. You already know from our past articles — and from common sense — that maximum power can only be obtained if the solar panels are constantly pointed at the sun from sunrise to sunset; thus the need for a Sun Tracker. While the concept of mechanical sun tracking is fundamentally simple, there are many factors to be considered in achieving it. This article and the one that follows next month describe how it's done and how you can do some very interesting experiments.

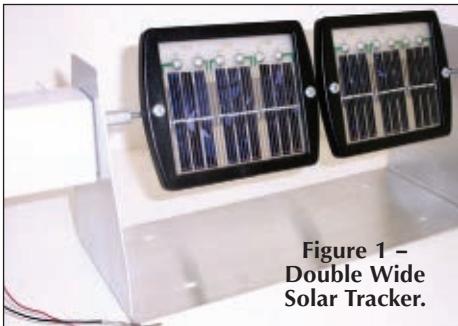


Figure 1 – Double Wide Solar Tracker.

Sun Tracker Design

Our Sun Tracker design can be expressed in the following general categories:

- Mechanical
- Electronics
- Firmware

Mechanical

Mechanically, the Sun Tracker consists of one or two solar panels (your choice) coupled to a 12 inch threaded rod attached to a geared DC motor that's all mounted on a custom mounting bracket (Figure 1). The solar panels are attached to the threaded rod using two small angle brackets that are, in turn, secured by #8 screws, washers, and nuts (Figure 2). The threaded rod is then coupled to the shaft of a geared DC motor with a standard shaft coupler (Figure 3).

To help balance the weight of the cantilevered solar panels, a counter-balance consisting of a straight bracket and some washers is attached to the threaded rod in the center of the back of the solar panel (Figure 4). The counter-balance makes it much easier for the small geared motor to rotate the solar panels. The motor and solar panel wires are routed to the BS2 or PICAXE “test bed” boards where they connect into the proper holes on the solderless breadboard.

The mechanical assembly of the Sun Tracker is straightforward. However, there are many detailed

steps involved. Due to the limited space for everything else I want to cover here, you can find complete details for assembling everything on my website at www.learnonline.com → Experimenter Kits → BS2 or 28X2 → Build a “Double Wide” Sun Tracker. A **Parts List** is included here.

Electronics

Our Sun Tracker is controlled by either a Parallax BS2 or PICAXE 28X2 microcontroller (your choice) mounted on its solderless breadboard alongside the Sun Tracker mounting bracket (Figure 5). Also included are the NiMH battery and battery charger circuit from Part 3 and a new H-bridge circuit to control the DC motor which is powered by the rechargeable battery. The H-bridge circuit is the interface between the micro and the motor. It uses a PWM (Pulse Width Modulated) technique created in the firmware to control the motor's rotational travel and, thus, the solar panel's degree of movement. We want to keep the motor's travel fairly short in order to track the [relatively] slow movement of the sun, hence the PWM technique that pulses the motor in short east-west movements. By using the rechargeable battery, we take the load off the solar panel to power the motor directly. You may configure the solar panels in any series-parallel arrangement you desire. Our versatile solar panels are really three solar modules in one housing,

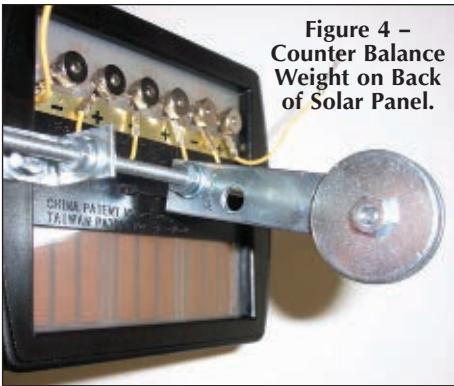


Figure 4 – Counter Balance Weight on Back of Solar Panel.

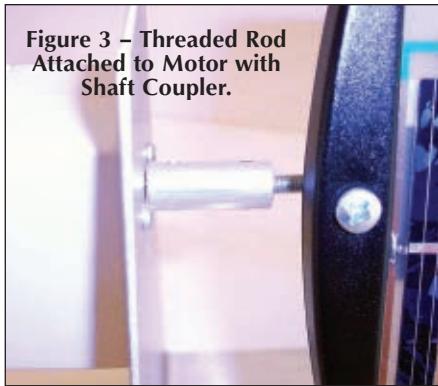


Figure 3 – Threaded Rod Attached to Motor with Shaft Coupler.

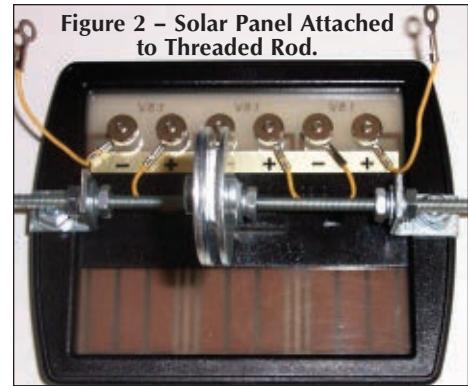


Figure 2 – Solar Panel Attached to Threaded Rod.

so with two panels you have six solar modules that you can arrange in a variety of voltage-current output configurations. Just make sure that the total “open circuit” voltage does not exceed five volts as it will swamp the A/D converter inputs.

Hook up the solar panels, motor wires, battery, and other jumpers as described in the detailed instructions. This includes the H-bridge circuit on the solderless breadboard, as well as the NiMH battery. Refer to **Figure 6** for a combination Block Diagram/Schematic of the hookup. As you can see, there is a lot going on here, and I'll go into how the firmware handles all of this hardware next.

Firmware

The firmware is subdivided into four basic functions:

- Sun Tracking
- Battery Charging
- Data Logging
- Data Output to Computer

Each major function is serviced by the micro in a round-robin manner that repeats from top to bottom, over and over again. A flow diagram of the firmware functions can be seen in **Figure 7**. Refer to it in order to better understand the following discussion.

Sun Tracking

When first powered up or after you push the reset button (on the Parallax BOE or Homework board), the firmware doesn't know where the sun is yet so it goes into *Search Mode*. In *Search Mode*, a sample of the solar panel's voltage is taken then the

firmware causes the motor to move slightly to the east and a new voltage sample is taken. If the new voltage sample is more than the last sample (called *lastVolts* in the code), the firmware moves the solar panels east again. However, if the new voltage sample is less than the last sample, it means that we have overshot the sun's position. When this happens, the firmware enters the Track Mode. **Figure 8** illustrates these actions.

The *Track Mode* is designed to ensure that the solar panels are always facing the sun as it travels in a westerly direction during the day. Each time through the *Track Mode* loop, the firmware takes a sample of the solar panel's voltage and compares that sample to *lastVolts*. If the sample and *lastVolts* are the same, nothing happens and the solar panels are not moved. Otherwise, the solar panels are moved slightly west, then another voltage sample is taken. If the new voltage sample is less than the last voltage sample, that means that we've overshot the sun's position again, so the firmware activates the H-bridge circuit and causes the panels to move back east again. **Figure 9** shows how this works.

After the *Search Mode* has located the sun's position, the *Track Mode* is invoked each time through the Main firmware loop, so the solar panels are constantly moving slightly west to follow the sun if the voltage samples warrant

such movement. Most commercial sun trackers do essentially the same thing because the sun is quite predictable.

Battery Charging

As I said earlier, the NiMH battery is used to power the geared motor through the H-bridge circuit, so it stands to reason that since we have solar panels at our disposal we should use them to charge the battery. I've

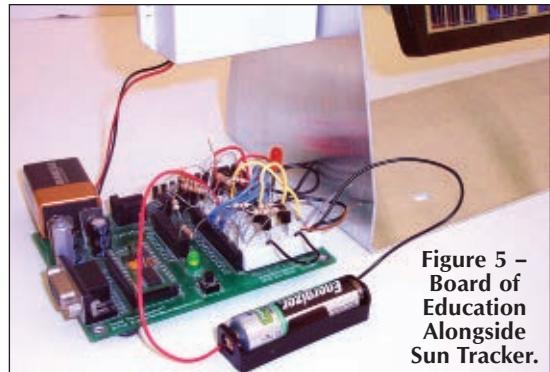


Figure 5 – Board of Education Alongside Sun Tracker.

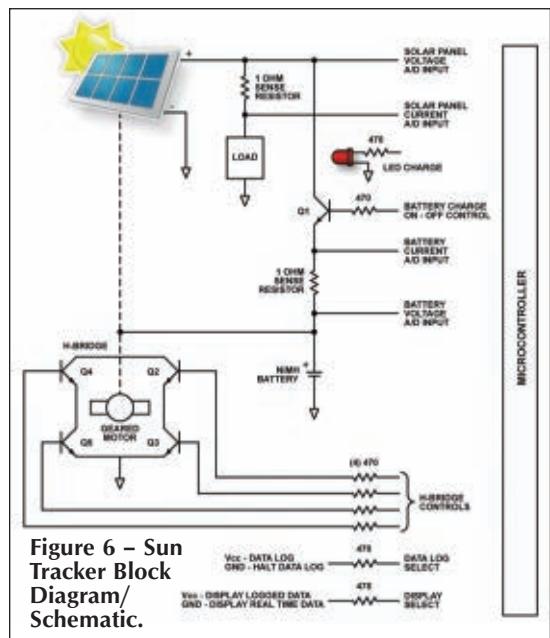


Figure 6 – Sun Tracker Block Diagram/Schematic.

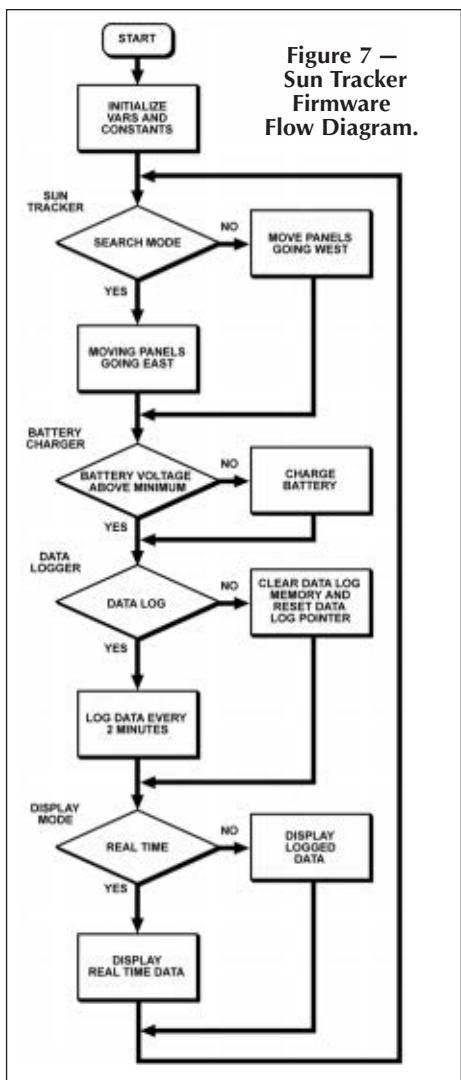


Figure 7 – Sun Tracker Firmware Flow Diagram.

NiMH battery voltage is sampled. If it is at an acceptable voltage level, the firmware returns to the Main loop. However, if the battery voltage falls below a minimum voltage level which you set as a firmware constant called *fullDischargeVolts*, the battery begins its “energy loop” charging cycle.

In the *Charge_Battery* routine, the energy loop turns transistor Q1 ON which delivers the solar panel’s voltage and current into the battery. The LED is also solidly illuminated at this point. The firmware monitors the battery’s voltage and current, and keeps Q1 and the LED ON until the accumulated current level called *minEnergy* in the code is achieved. This puts about 1/20 C of charge into the NiMH battery. That should keep it turning the motor for quite a while. Of course, the battery still powers the geared motor even when it is being charged. Again, if you want to know more about the details of how the battery charging algorithm works, refer to Part 3 and/or go to www.learnonline.com → Experimenter Kits → BS2 or 28X2 → Build an On Demand Solar Powered Battery Charger.

Data Logging

Most sun trackers do not do data logging of the solar panel voltage, current, and power. However, since our theme is on experimentation, I felt that it would be important to actually measure and save the electrical output of the solar panels as they gathered sunlight during the day. With this

data, you can compare the added performance of the Sun Tracker’s ability to gather solar energy against a fixed solar panel’s output. Data logging of the solar panel’s voltage, current, power, and load resistance values are done as follows:

Approximately once every two minutes, the firmware takes a snapshot of the solar panel’s voltage and current readings. This consists of two bytes each for voltage and current making the total “data record” four bytes. With this process, we are essentially taking a snapshot of the sun’s condition every two minutes as it appears to travel across the sky – including all the voltage and current dips created by interference from clouds, haze, and other natural obstructions. Since a normal day consists of about eight useful hours of sunlight and our sample rate is once every two minutes, this translates to 240 samples per day (8 hrs x 30 samples / hr = 240 samples). Multiplying 240 samples times four bytes per sample gives us 960 bytes required for one day of storage. Both the BS2 and 28X2 have at least this much storage available where the program actually uses 1024 bytes for slightly more data logging time.

Data Logging Pointers

To handle reading, writing, and displaying the logged data the firmware maintains two pointers to the data logged memory area: a Data Log Pointer and a Display Pointer. Refer to Figure 10 to follow along.

The following description involves the EEPROM memory of the Parallax BS2. The PICAXE 28X2 operates the same way with scratchpad RAM, but the actual memory address locations are different. At the beginning of the data log cycle and when the data log memory is cleared (we’ll get to this in a moment), the data log pointer is set to the bottom address of the data log memory area. Each time a data log event takes place, the solar panel’s voltage and current – both two byte variables – are written into memory. The Data Log Pointer is then incremented by four bytes to the next

used the same circuitry and basically the same firmware as described in Part 3 with some firmware modifications that allow it to fit into the Main round-robin loop. In the *Test_Battery_Voltage* routine, the rechargeable

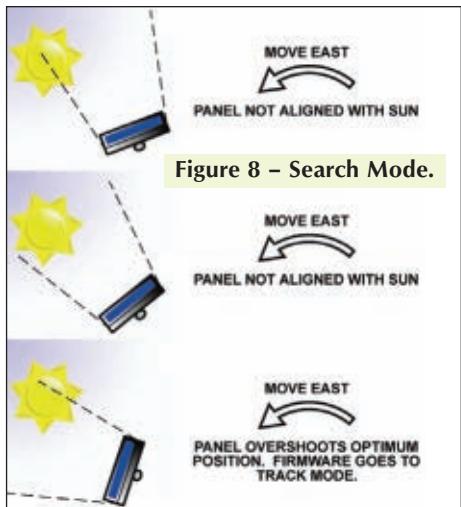


Figure 8 – Search Mode.

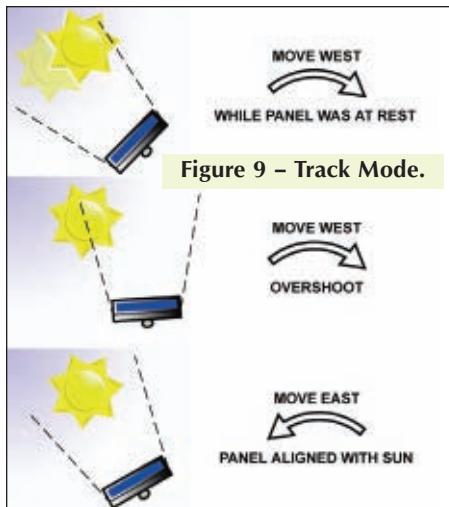


Figure 9 – Track Mode.

“data record” memory location. The process continues until all 256 data records (1024 bytes of data) have been written. At this point, the firmware detects the fact that the Data Log Pointer is at its maximum value and data logging is discontinued. The Data Log Pointer remains fixed at address \$0400 until the data log memory is cleared. While this is happening, the Display Pointer is incremented on every pass through the Main loop (about once a second), then cycles back and restarts at the first data logged event again. This permits you to view the logged data as it is being accumulated or after the data log memory is full. The Display Pointer cycles from address \$0000 to address \$03FC in four-byte increments, and then back to address \$0000 on a continuous, once per second round-robin basis. You can reset it to \$0000 at power on or when the reset button is pressed to restart the display of logged data.

Data Logging Activity

To help you know what’s happening during the data logging sequence, the LED briefly flashes every time through the Main loop to indicate that data logging is taking place. This is like a one-second “heartbeat” that lets you know that all is well with the data logging activity. Approximately once every two minutes, when a data log sample is taken the LED will flash with a longer duration (about one second) to let you know that a snapshot was taken and stored in the data log memory. When the data log memory becomes full, i.e., when all 1024 bytes

(256 data records) are stored, the LED flashes four times for each pass through the Main loop. This flashing will let you know that the data log memory is full and that further data logging has ceased.

You are able to enable and disable the data logging feature with the Data Log Select signal – a resistor-jumper on the test bed (**Figure 6**). Based on this jumper setting, the Main routine directs the firmware to either clear the data log memory and cease data logging, or continue with data logging until the data log memory becomes full. For example, if you previously recorded a set of data and now want to record another set, simply move the jumper from Vcc to ground and the logged memory will be erased the next time through the Main loop. The LED ceases to flash when data logging is disabled, which is another state that lets you know what’s happening. Move the resistor-jumper back to Vcc when you want to resume data logging. I use a 470 ohm resistor instead of just a wire jumper to limit the current into the micro’s input port when it’s connected to Vcc. The LED flash sequences for data logging are listed next including those for the battery charging cycle, as well:

LED Flash Sequences

Data Logging

- Once a second – data logging in progress – short flash.
- Once every two minutes – log event – longer one second flash.
- Four rapid flashes – data log memory full.
- No flashing – data logging disabled – data log memory erased.

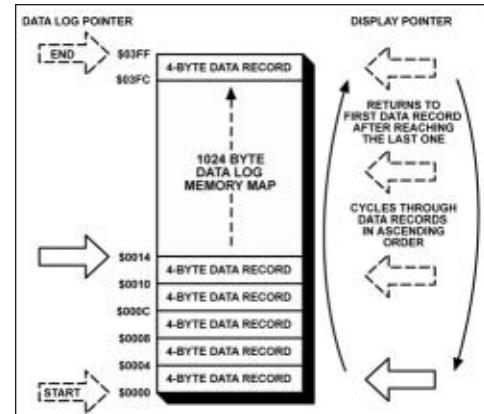


Figure 10 – Data Logging Pointers.

Battery Charging

- Solid on – battery is charging.
- Slow flashing – battery voltage is below minimum while charging.

Data Output

There are two ways to view the solar panel data on the computer: in real time and while data logging is taking place; or when the data log memory is full. This is also handled by a resistor – jumper. Real time data is displayed on the computer when the Display Select jumper (another 470 ohm resistor) is applied to ground. Logged data is displayed when it’s attached to Vcc (refer to **Figure 6** again). The ability to switch between real time and logged data display is quite powerful in terms of experimenting with the Sun Tracker.

For example, you can study the effects of the sun’s activities in real time while data logging continues in the background. Or, you can witness the display of the logged data as it occurs. Just configure the Display

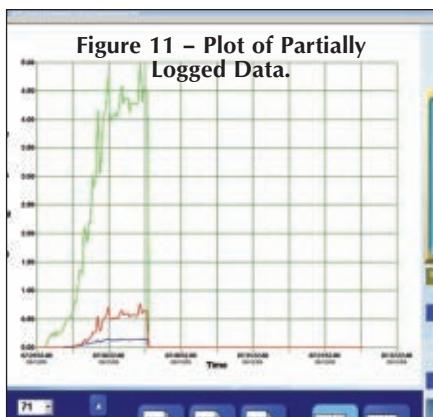


Figure 11 – Plot of Partially Logged Data.

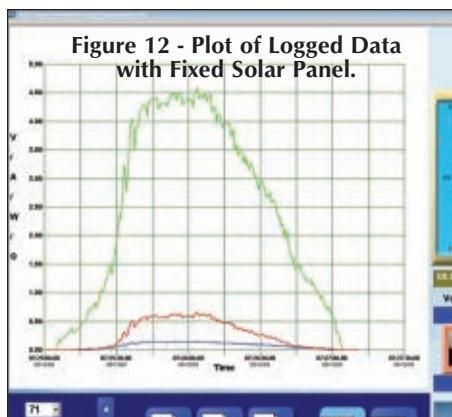


Figure 12 - Plot of Logged Data with Fixed Solar Panel.

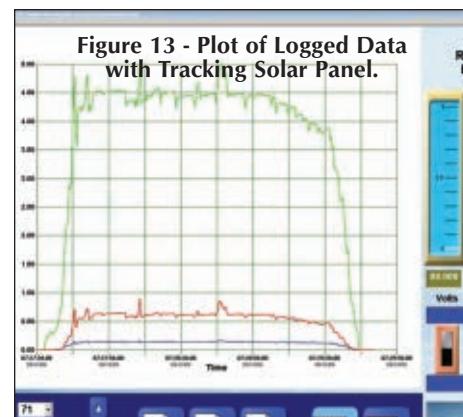


Figure 13 - Plot of Logged Data with Tracking Solar Panel.

Select jumper accordingly. When viewing logged data, the firmware increments the Display Pointer every time through the Main loop. Therefore, the firmware steps through the logged data one data record at a time. If the data logging sequence is in progress and the data log memory is not full, the computer will display all the recorded logged data up to that point followed by "all zero" data for the data log memory that is yet to be recorded (**Figure 11**). Since there is no real indication of where the logged events are relative to the displayed data, you can restart the display process from memory address \$0000 by pressing the reset button or cycling power to the micro. This action resets the Display Pointer to address \$0000.

Orienting the Tracker for Best Results

The Sun Tracker's east-west motor movements are designed with the geared motor facing due south. This will allow the solar panels to acquire and track the sun as it travels from east to west. Another consideration is ensuring that the solar panels have an unobstructed view of the sun all day long without the possibility of shadows from trees, buildings, or other fixed obstructions. This may not be possible if you're inside and trying to track the sun through a window as would normally be the case in very cold or inclement weather. Nevertheless, proper orientation is key to acquiring the optimum amount of sunlight during the day.

Besides the standard south orientation, you may want to also consider angling the entire mounting mechanism from horizontal to align with the sun's height above the horizon. You learned in Part 2 that the sun's apparent angle is dependent on the time of year and your latitude, so it's best to angle the entire mounting bracket mechanism in a "Polar Mount" fashion for best results (refer to the sidebar on Single Axis Sun Trackers).

Data Log Example

Here's what you can expect from

the actions of the Sun Tracker. For **Figure 12**, I used a stationary solar panel without any tracking. I placed it facing due south and recorded its output for one day. Right beside it, I used another panel attached to the Sun Tracker and recorded the same sun data as shown in **Figure 13**. As you can see, the plot of the sun's voltage is much narrower for the stationary panel as compared with the panel on the tracker. The wider plot indicates the increased power and energy captured with the Sun Tracker in operation. This is the real function of the Sun Tracker; that is, to capture the maximum amount of sunlight and resultant electrical power and energy possible. Refer to **Figure 6** in order to set the Data Log Select and Display Select jumpers for data logging.

Summary

As you can see, our Sun Tracker is quite a versatile experimental tool. I felt that just doing a mechanical sun tracker function wasn't enough given the power of our microcontrollers; they should be used to their fullest capability in every way possible to make the project and experiments more interesting. It's always nice to add more firmware functions — mainly because they're free and don't cost any more than the microcontroller hardware that supports them. Always be aware, though, of "feature creep" that can overcomplicate things and destroy the best of designs.

Single Axis Sun Trackers: Horizontal, Vertical, and Polar Mountings

A horizontal sun tracker is like the one we built here. As its name implies, the main axis is aligned parallel to the ground. When the rod that holds the panels is faced due south, the panels will track the sun from east to west. A vertical tracker is like vertical window blinds where the axis is aligned perpendicular to the ground. Here the panels rotate in a vertical plane to follow the sun. A polar tracker is like a vertical tracker that is tilted, generally at the angle the earth turns on its axis. In so doing, it is able to capture more of the sun's energy. If the tilt angle is further "manually" adjusted to account for the additional tilt due to the latitude and seasons of the year, then even more of the sun's energy can be captured. Photos courtesy of Wikipedia.




Horizontal Mount Solar Panels

An important point to note about the Sun Tracker is that all of the energy to move the motor comes from the NiMH rechargeable battery, which is trickle-charged during the day as necessary. This frees up the solar panel to power a load without the periodic heavy current drain of turning the motor every second or so. Another equally important design element is the ability to data log and display the sunlight data in real time or logged mode. I didn't have enough space left to go into the details of the H-bridge circuit, more firmware programming details, single axis versus dual axis sun trackers, or more of the data logging experiments that you can do with the double wide Sun Tracker, so that's what we'll do in the next installment. In the meantime, conserve energy and stay green. **NV**

Qty	Description
1	Mounting Bracket
1	Geared Motor
1	12" Threaded Rod (#8)
1	Shaft Coupler
2	Solar Panels
4	3/4" Machine Screw (#8)
2	1/2 Machine Screw (#8)
18	Hex Nut (#8)
18	Flat Washer (#8)
18	Lock Washer (#8)
1	Acorn Nut (#8)
4	Small Angle Bracket
2	Straight Bracket
8	Flat Washer (1")

Parts List

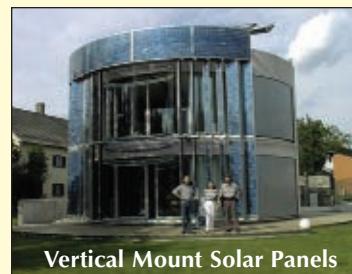The Double Wide Sun Tracker is available as a Nuts & Volts exclusive kit. For kit details, go to <http://store.nutsvolts.com> or page 74 in this issue.



Vertical Mount Solar Panels



Polar Mount Solar Panels



■ BY FRED EADY


TAKE AN IO-WARRIOR INTO YOUR NEXT EMBEDDED BATTLE

We are all used to stuffing code into a microcontroller to enable our embedded applications. This month, the tables are turned. The microcontroller work has been done for us and we must perform some Bill Gates C++ coding to force bits back and forth across the USB pipe. The folks at Code Mercenaries have assembled a microcontroller package that embeds a fully compliant, low speed USB HID device. All we have to do to access the IO-Warrior's I/O subsystem is plug the IO-Warrior into a USB port and perform the IO-Warrior API calls required to implement our application.

CODE MERCENARIES' IO-WARRIOR

The IO-Warrior family (available through Saelig; see **Resources**) consists of the IO-Warrior 24, the IO-Warrior 40, the IO-Warrior 56, and the IO-Warrior 24 Power Vampire. The numbers in the IO-Warrior monikers represent the number of actual pins that make up the host microcontroller package. The 24-pin IO-Warrior 24 exposes 16 I/O pins to the programmer while the IO-Warrior 40 provides the programmer with 32 I/O pins. Fifty of the IO-Warrior 56's pins are available to the user. The IO-Warrior 24 Power Vampire is a specialized variant that is designed to power source from the USB portal. All of the IO-Warriors are low speed USB devices with the exception of the IO-Warrior 56, which is a full speed device. The IO-Warrior 24 you see in **Photo 1** is the one we'll be working with. The IO-Warrior 24 is coded to include limited I²C master support, an HD44780 LCD driver, incoming RC5 IR command support, and SPI master mode support. There is also a special function mode that allows the IO-Warrior 24 to drive an 8 x 32 LED matrix with a little help from some external shift registers.

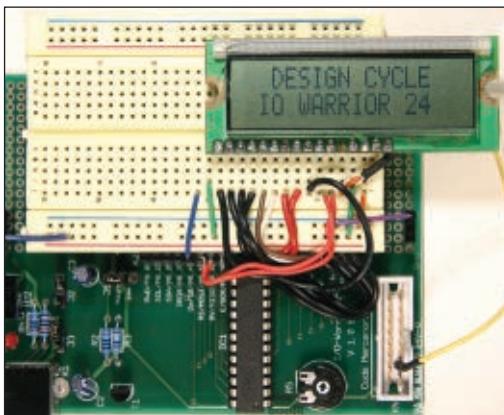■ **PHOTO 1.** The IO-Warrior 24 comes as a kit. The Design Cycle version is shown here. I added the solderless breadboard and the 2 x 16 Lumex LCD.




The basis of the IO-Warrior 24 is an OTP (One Time Programmable) Cypress CY7C63743C-PXC enCoRe USB combination low speed USB and PS/2 peripheral controller which you can see sans the IO-Warrior version label in **Photo 2**. The CY7C63743C-PXC's claim to fame is its ability to automatically operate in USB or PS/2 mode with a minimum of external supporting components.

For you young'uns, a PS/2 is (was) an IBM personal computer that replaced the venerable IBM XT and AT personal computers. The PS is short for "Personal System." USB overtook the clocked PC PS/2 interfaces in the 1990s.

To eliminate the more commonly used microcontroller support components, the CY7C63743C-PXC's internal oscillator can be used in lieu of an external ceramic resonator, while a 3.3 volt internal regulator provides voltage for the USB pull-up resistor. The CY7C63743C-PXC isn't very good at sourcing current on its I/O pins (2 mA max). However, it makes up for the weakness by being able to sink up to 50 mA on a single GPIO pin. Otherwise, as you can see in **Figure 1**, the PXC is a typical USB-enabled microcontroller. A pinout diagram of it and

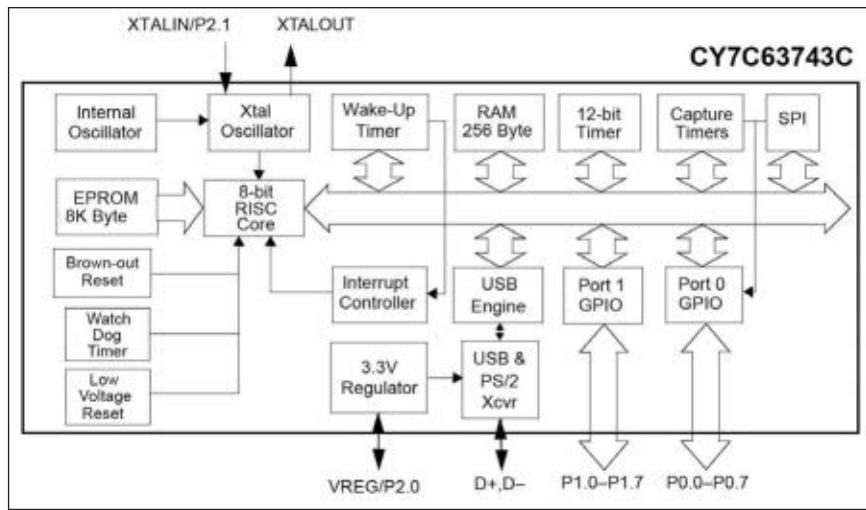■ **PHOTO 2.** The veteran Cypress CY7C63743C-PXC enCoRe USB combination low speed USB and PS/2 peripheral controller take on the IO-Warrior 24 USB mission.





its associated IO-Warrior 24 pinout are given to you in **Figure 2**.

Note that the IO-Warrior 24 configuration does not allow the use of an external clock source of any kind. Instead, the XTALIN pin is used as an input to select the power mode. The IO-Warrior 24 power pin is checked at power-up and bus reset only. When the power pin is pulled logically high, the USB power mode is set to high. In high power mode, the IO-Warrior 24 will request 500 mA from the USB power bus. A low on the Power pin will result in the IO-Warrior 24 settling for 100 mA max from the USB portal. The V_{reg} output is intended to power the USB D pull-up resistor and that is all.

The special SPI, I²C, and LCD functions take precedence over the normal GPIO pin logic. The PXC GPIO speeds are too slow to physically implement the I²C clocking via the I/O pins. So, the I²C protocol is handled internally to the IO-Warrior 24 to improve the data throughput. The IO-Warrior 24 can only participate in an I²C network as the one and only master node. Due to the IO-Warrior's lack of a stable hardware I²C clock, it may not be the best I²C master for some I²C slave devices.

SPI and LCD support on the IO-Warrior are mutually exclusive. This is due to the fact that the LCD E signal is multiplexed with the SPI SCK signal and the SPI data I/O pins (MOSI and MISO) are shared with the remaining LCD control signals RS and R/W. The IO-Warrior 24 SPI portal is capable of clocking at 2 MHz. However, the USB interface bandwidth is limited and the full bandwidth of the SPI channel cannot be utilized. LCD and LED matrix support are also

FIGURE 1. The CY7C63743C-PXC hangs its hat on the reduced component count hook. No external clock source or voltage regulator is needed for this part to operate in USB mode.

nonconcurrent as some of the LCD data pins are used to drive the LEDs. A separate IO-Warrior 24 application note describes the implementation of an LED matrix.

THE IO-WARRIOR 24 STARTER KIT

The IO-Warrior 24 Starter Kit comes out of the box in kit form. My assembled IO-Warrior is shown in **Photo 1**. As you can see, putting one of these together

is a snap. I took the liberty of adding the solderless breadboard and the LCM-S01602DTR/M LCD. You can get an idea of how the starter kit is laid out by matching up the components you see in **Photo 1** with their graphical counterparts in **Schematic 1**.

The LCM-S01602DTR/M LCD's I/O pinout is compatible with the layout you see in **Schematic 1** with the exception of pins 15 and 16 which do nothing on the LCD as it has no backlight. Note the use of a PNP transistor backlight switch. Recall that the CY7C63743C-PXC doesn't like to source current and grounding (sinking) the BC307's base is right down the PXC's alley.

ARMING THE IO-WARRIOR 24

All of the major PC operating systems support USB. In addition, those operating systems natively support HID (Human Interface Device) class devices such as keyboards, joysticks, and mice. A major advantage to HID class devices is that they can be accessed from the application level. The IO-Warrior 24 is internally coded to act as a USB HID class device.

The CY7C63743C-PXC USB subsystem consists of three USB endpoints. Thus, the IO-Warrior 24 inherits that trio of endpoints. To get data to and from device resources, USB endpoints can be assigned to interfaces which provide a path to the device's functions. In the case of the IO-Warrior 24, interface 0 is the direct path to the GPIO pins. The special mode functions available via the IO-Warrior 24 firmware are spoken to via interface 1. If you recall your USB 101 training, endpoint 0 is common to all USB devices.

FIGURE 2. You can clearly see the native CY7C63743C-PXC multiplexed GPIO pin functions in this figure. The XTALIN and XTALOUT expect to see a 6 MHz ceramic resonator when the external clock option is selected. P2.0 and P2.1 are alternate inputs. Firmware forces the CY7C63743C-PXC to suit up with the IO-Warrior 24 armor.

CY7C63743C
24-pin SOIC/PDIP/QSOP

P0.0	1	24	P0.4
P0.1	2	23	P0.5
P0.2	3	22	P0.6
P0.3	4	21	P0.7
P1.0	5	20	P1.1
P1.2	6	19	P1.3
P1.4	7	18	P1.5
P1.6	8	17	P1.7
VSS	9	16	D+/SCLK
VPP	10	15	D-/SDATA
VREG/P2.0	11	14	VCC
XTALIN/P2.1	12	13	XTALOUT



IO-Warrior 24	
DIL24 / SOIC24	
P0.0/RxD	1
IIC-SCL/P0.1	2
IIC-SDA/P0.2	3
SPI-DRDY/P0.3	4
LCD-DB0/P1.0	5
LCD-DB2/P1.2	6
LCD-DB4/P1.4	7
LCD-DB6/P1.6	8
GND	9
PullToGND	10
Vreg	11
Power	12
P0.4/SPI-SS/LCD-/On	1
P0.5/SPI-MOSI/LCD-RS	2
P0.6/SPI-MISO/LCD-R/E	2
P0.7/SPI-SCK/LCD-E	2
P1.1/LCD-DB1	20
P1.3/LCD-DB3	19
P1.5/LCD-DB5	18
P1.7/LCD-DB7	17
D+	16
D-	15
Vcc	14
NC	13

Endpoint 0 is used to interrogate and configure a downstream USB device. Also, endpoint 0 can be used to send data to a downstream USB device's functions. The IO-Warrior 24 USB driver firmware employs endpoint 0 for output data (host to IO-Warrior 24) and as a vehicle for the host to send commands to the IO-Warrior's special mode functions. The path used to set the logical state of the IO-Warrior 24 GPIO pins flows through endpoint 0 and interface 0. The commands destined for the special mode functions also enter the IO-Warrior 24 via endpoint 0 but flow through to interface 1.

The IO-Warrior 24 can only report the state of the GPIO pins when it is asked to do so by the host. Endpoint 1 is used for this purpose. When logic states on the IO-Warrior 24's GPIO pins change, the new data is transferred on the next host request.

Thus, when the state of the GPIO pins change, a report is generated and flows from the GPIO function through interface 0 and out to the host via endpoint 1. Replies from the special mode functions pass from interface 1 through endpoint 2 to the host. Endpoints 1 and 2 are called

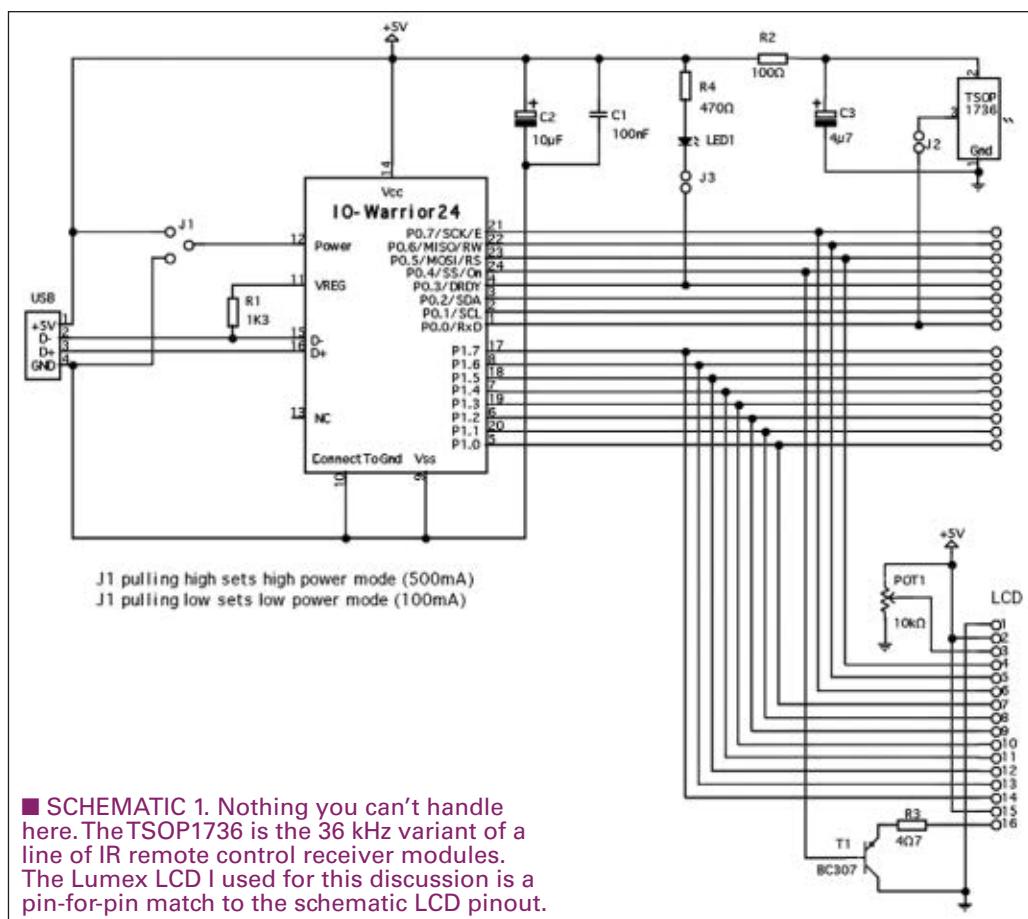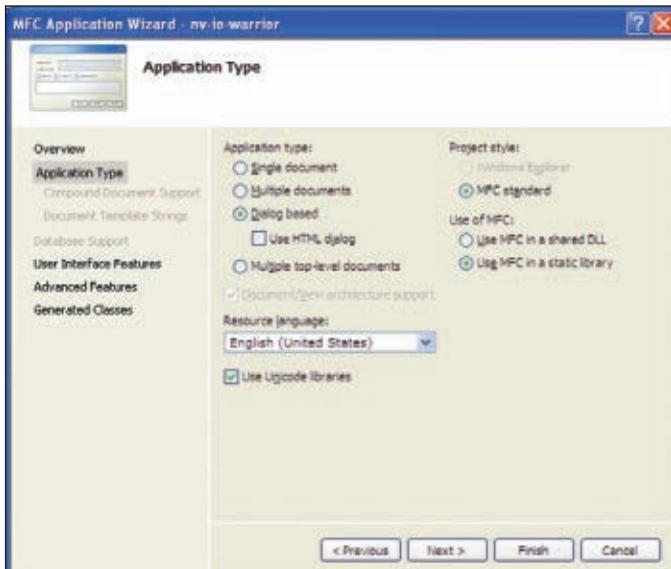■ Screenshot 1. There's no need to get fancy and complicated. All we want to do is display the results of the IO-Warrior API calls. Visual C++ is easy to learn and allows you to associate the IO-Warrior API calls with buttons and controls.




■ SCHEMATIC 1. Nothing you can't handle here. The TSOP1736 is the 36 kHz variant of a line of IR remote control receiver modules. The Lumex LCD I used for this discussion is a pin-for-pin match to the schematic LCD pinout.

interrupt-in endpoints. In this case, interrupt means that data is transferred only when there is new data to pass along. The host determines when the new data is transferred which (due to the USB protocol) is once every 8 to 10 ms.

IO-WARRIOR 24 FIRE CONTROL

We've already discussed more USB concepts than

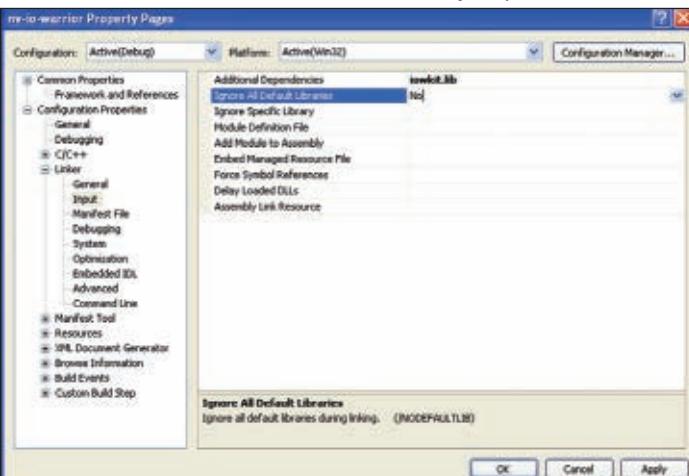■ Screenshot 2. Things just don't work well in the compilation and link processes without including this library into the mix. The library is included with the IO-Warrior Software Development Kit which is part of the IO-Warrior 24 Starter Kit. This window can be found in the Project pull-down menu.





■ **Screenshot 3.** Visual C++ is carrying the work load behind this visual. This message box was generated with a couple of lines of Visual C++ code. If the IO-Warrior 24 is not connected to the host USB portal, this little box will pop up.

you need to know in order to code an IO-Warrior 24 application. The idea behind the IO-Warrior is to allow a programmer with absolutely no USB knowledge to apply USB technology in a microcontroller application. To this end, the Code Mercenaries folks have preloaded a CY7C63743C-PXC with HID firmware and supplied a USB-laden API for the host PC. The Windows API is housed in a DLL called *iowkit* and the Linux library is called *libiowkit.so*. The API encompasses all of the functionality for every IO-Warrior variant and is designed to be used with any Windows or Linux programming language. I've chosen to exercise the IO-Warrior 24 resources using Visual C++ which is one of the Windows programming languages available within Microsoft's Visual Studio 2008. I'll demonstrate the capabilities of the IO-Warrior API with the help of a Visual C++ dialog based MFC application. **Screenshot 1** – which is one of the MFC Application Wizard configuration windows – backs up my previous declaration. The only additional step we need to take outside of the MFC Application Wizard is to include the *iowkit.lib* in the link process. I've done this in **Screenshot 2**.

Like Visual Basic, Visual C++ is an event driven programming language. In a normal Visual C++ application, we would place much of the code we're about to write behind a button or control. For simplicity, we'll code everything we can inside of the Visual C++ initialization function which is defined as follows:

```
BOOL CnviowarriorDlg::OnInitDialog()
```

Our initial goal is to discover an IO-Warrior 24 at the other end of the USB cable. This is done with this API call which returns a unique handle for the first IO-Warrior detected:

```
IOWKIT_HANDLE ioHandle_1;
ioHandle_1 = IowKitOpenDevice();
```

The handle is actually a value that we will use to identify the detected IO-Warrior 24 to other API functions. The Visual C++ debug watch window revealed that a value of 0x00B60014 was assigned to the variable *ioHandle_1*. If the *IowKitOpenDevice* API function returns a NULL value, no IO-Warrior 24 was sensed. So, we will need to code an *if-else*

segment to handle the

■ **Screenshot 4.** So far, so good. Once again, Visual C++ and the IO-Warrior API are doing most of the work here.

possibility of not finding an IO-Warrior waiting in the wings:

```
CString msgCHECKCONN = _T("Check IOWarrior Connection");
CString msgNOTDETECTED = _T("No IOWarrior Detected");

if(ioHandle_1 != NULL)
{
    //Continue on our way..
}
else
{
    IowKitCloseDevice(ioHandle_1);
    MessageBox(msgCHECKCONN,msgNOTDETECTED,0);
}
```

In the previous code snippet, we assume that the IO-Warrior device open failed as there is only code for the *else* (failure) branch of the *if-else* segment. So, upon receiving a NULL *ioHandle* value, we close all IO-Warrior devices and post a device-not-detected message like the one you see in **Screenshot 3**. Let's code a positive response to the *IowKitOpenDevice* API call that will retrieve the detected IO-Warrior 24's serial number and display it on the LCD and in the application dialog box:

```
CString msgCHECKCONN = _T("Check IOWarrior Connection");
CString msgNOTDETECTED = _T("No IOWarrior Detected");

WCHAR SerialNumber[10];
CString SNtext;
UCHAR nextline;
nextline = 0;

if(ioHandle_1 != NULL)
{
    // Get Serialnumber
    IowKitGetSerialNumber(ioHandle_1,
    SerialNumber);
    // Display Serial Number
    SNtext.Format(_T("IOWarrior 24 Attached with Serial Number = %s"),
    SerialNumber);
    m_DisplayWindow.InsertString(nextline++, SNtext);
}
else
{
    IowKitCloseDevice(ioHandle_1);
    MessageBox(msgCHECKCONN,msgNOTDETECTED,0);
}
```

Note the use of the *ioHandle_1* value in the *IowKitGetSerialNumber* API call, which returns the eight word IO-Warrior 24 serial number in the *SerialNumber* array. Once we have the IO-Warrior's serial number, we can format a message and display it as shown in **Screenshot 4**. Just in case you're wondering, the *_T*'s provide Unicode support for the message box strings.

We can also use the IO-Warrior API functionality to send the serial number information to the LCD. However, before we write that bit of code I need to clue you in on the data structure behind the bytes we're about to push towards the LCD's HD44780 controller. I also need to show you the data structure that the IO-Warrior 24 uses to control its GPIO pins. Recall that the IO-Warrior operates in the HID class. That means that the IO-Warrior 24 communicates using reports which are actually data



structures like the one shown here:

```
typedef struct _IOWKIT24_IO_REPORT
{
    UCHAR ReportID;
    union
    {
        WORD Value;
        BYTE Bytes[2];
    };
} IOWKIT24_IO_REPORT, *PIOWKIT24_IO_REPORT;
```

Each report is prefixed by a *ReportID* byte. The report ID is associated with a pipe. A pipe (in this case) is synonymous to an interface. So, Pipe 0 is used to talk to the IO-Warrior 24's GPIO pins just as Pipe 1 is used to communicate with the special mode functions. The IO-Warrior 24 report data structure contains a report ID and three bytes of payload. Pipe 0 is always used to interface to the GPIO pins. So, the ReportID value for GPIO access is always 0. A ReportID value would not be necessary in any case of GPIO access but Windows requires that a report ID byte be present. With that, here's how we write a 0xAA to the IO-Warrior 24's P0 GPIO pin set and 0x55 to its P1 GPIO pin set:

```
IOWKIT24_IO_REPORT report24;
ULONG rc32;
DWORD BitsRead;
CString BITStext;
CString RCtext;

#define IOW_PIPE_IO_PINS 0
#define IOWKIT24_IO_REPORT_SIZE sizeof(IOWKIT24_IO_REPORT)

// Write 0x55AA to GPIO
IowKitSetWriteTimeout(ioHandle_1, 2000);
memset(&report24, 0, IOWKIT24_IO_REPORT_SIZE);
report24.ReportID = 0;
report24.Value = 0x55AA; //0x55 to P1-0xAA to P0
rc32=IowKitWrite(ioHandle_1,IOW_PIPE_IO_PINS,(char*)&report24,IOWKIT24_IO_REPORT_SIZE);
// Display number of bytes written (rc32)
RCtext.Format(_T("%X Bytes Written"), rc32);
m_DisplayWindow.InsertString(nextline++, RCtext);
// Read and display states of all 16 IO-Warrior
24 GPIO pins
IowKitReadImmediate(ioHandle_1,&BitsRead);
BITStext.Format(_T("P0 = 0x%X"), (BitsRead &
0x000000FF));
m_DisplayWindow.InsertString(nextline++, BITStext);
BITStext.Format(_T("P1 = 0x%X"), ((BitsRead &
0x0000FF00)>> 8));
m_DisplayWindow.InsertString(nextline++, BITStext);
```

The pair of `#define` statements can be found in the *iowkit.h* file, which is part of the IO-Warrior SDK. To be safe, I added the *IowKitSetWriteTimeout* API call to force a timeout of two seconds if the *IowKitWrite* function failed. That's not likely, but the insurance is there to keep the program from locking up on a GPIO write failure. The *memset* function simply clears the *report24* data structure to zero. Adding the GPIO read-write-display code to our existing serial number code results in the display shown in **Screenshot 5**. We've got the hang of putting human readable things into the dialog box display window.

Let's get just as good with the LCD. We must use the eight-byte special report ID data structure to

communicate with the LCD's HD44780:

```
typedef struct _IOWKIT_SPECIAL_REPORT
{
    UCHAR ReportID;
    UCHAR Bytes[7];
} IOWKIT_SPECIAL_REPORT,
*PIOWKIT_SPECIAL_REPORT;
```

You already know how to assemble and transmit a report. So, the language within the enable LCD API special function call should not be foreign:

```
IOWKIT_SPECIAL_REPORT reportLCD;
// These are found in the iowkit.h file
#define IOWKIT_SPECIAL_REPORT_SIZE sizeof
(IOWKIT_SPECIAL_REPORT)
#define IOW_PIPE_SPECIAL_MODE 1

// Enable LCD
memset(&reportLCD, 0,
IOWKIT_SPECIAL_REPORT_SIZE);
reportLCD.ReportID = 0x04; //ReportID for
//LCD-Mode
reportLCD.Bytes[0] = 0x01; // enable LCD Special
// Function
IowKitWrite(ioHandle_1, IOW_PIPE_SPECIAL_MODE,
(char *) &reportLCD,
IOWKIT_SPECIAL_REPORT_SIZE);
```


Upon receiving the enable LCD report, the IO-Warrior 24 will initialize the attached LCD and display the cursor at the home position. If the LCD has a backlight, the backlight is illuminated at this time, as well as via the active-low *ON* GPIO pin (P0.4). The LCD is now active and configurable. Notice that we used a *ReportID* value of 0x04 to enable the LCD and we'll use a *ReportID* value of 0x05 to configure the display:

```
// Configure LCD
// Reference page 43 of HD44780 data sheet
memset(&reportLCD, 0,
IOWKIT_SPECIAL_REPORT_SIZE);
reportLCD.ReportID = 0x05; //ReportID for
//LCD-Mode "write"
reportLCD.Bytes[0] = 0x04; //R/S mode=0 / Send
//bytes
reportLCD.Bytes[1] = 0x38; //function "8-Bit
//mode"
reportLCD.Bytes[2] = 0x0E; //function "display
//on-no blink"
reportLCD.Bytes[3] = 0x06; //function "entry
//mode set"
reportLCD.Bytes[4] = 0x01; // function "CLEAR
//DISPLAY"
IowKitWrite(ioHandle_1, IOW_PIPE_SPECIAL_MODE,
(char *) &reportLCD,
IOWKIT_SPECIAL_REPORT_SIZE);
```

If you go to the HD44780 datasheet page I reference in the code's comments, you'll be able to easily pick out and identify the bit patterns used in the *reportLCD* bytes. With the LCD initialized and configured, we're ready to send it a message to display:

```
WCHAR SerialNumber[10];

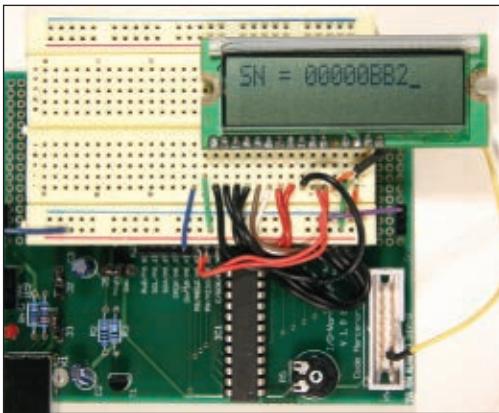// Send Serial Number to LCD
memset(&reportLCD, 0,
IOWKIT_SPECIAL_REPORT_SIZE);
reportLCD.ReportID = 0x05; //ReportID for
//LCD-Mode
```




■ PHOTO 3. What we have here is a single-IC USB interface for any HD44780-compatible LCD.

```

reportLCD.Bytes[0] = 0x85; //write 5 bytes to
                           //LCD command register
reportLCD.Bytes[1] = 'S'; //send character to
                           //LCD
reportLCD.Bytes[2] = 'N'; //send character to
                           //LCD
reportLCD.Bytes[3] = ' ';//send character to
                           //LCD
reportLCD.Bytes[4] = '=';//send character to
                           //LCD
reportLCD.Bytes[5] = ' ';//send character to
                           //LCD
IowKitWrite(ioHandle_1, IOW_PIPE_SPECIAL_MODE,
(char *) &reportLCD,
IOWKIT_SPECIAL_REPORT_SIZE);
memset(&reportLCD, 0,
IOWKIT_SPECIAL_REPORT_SIZE);
for(i=0;i<8;+i)
{
  reportLCD.ReportID = 0x05; //ReportID for
                           //LCD-Mode
  reportLCD.Bytes[0] = 0x81; //write 1 byte to
                           //LCD command register
  reportLCD.Bytes[1] = (char) SerialNumber[i];
                           //send character to
                           //LCD
  IowKitWrite(ioHandle_1, IOW_PIPE_SPECIAL_MODE,
(char *) &reportLCD,
IOWKIT_SPECIAL_REPORT_SIZE);
}

```

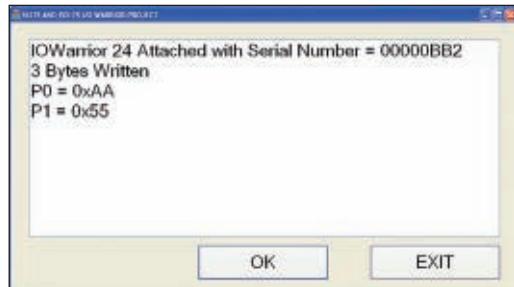

■ Screenshot 5. Note that I changed the CANCEL button to an EXIT button. You can see what I did to support that in the Visual C++ source code. The neat thing about Visual C++ is that in Debug mode you can see the strings and values before they are officially displayed in the dialog box. As you can see here, things worked as designed.

When addressing an LCD, the report ID and LCD command byte must always be sent. So, the maximum number of data bytes we can send to the LCD in a single report is six. That works out well with the "SN = " character string. However, the IO-Warrior 24 serial number is eight bytes long. No problem. Since we have the IO-Warrior 24 serial number coralled in an array, we can send the LCD data one byte at a time. Just as we did in Photo 3.

SOLDIER ON

I've supplied the Visual C++ source code you need to duplicate the IO-Warrior 24 efforts you've just read about in the download package available at www.nutsvolts.com. If Visual C++ is not your strength, the IO-Warrior SDK also includes sample code for Java, Delphi, Visual Basic, and C. There's also IO-Warrior support for Linux and MAC. No matter which programming language or operating system platform you choose to use, you can add the IO-Warrior to your Design Cycle. NV

SOURCES

IO-Warrior 24 Starter Kit
Saelig
www.saelig.com

Visual Studio 2008
Microsoft
www.microsoft.com

■ Fred Eady can be contacted via email at fred@edtp.com.

Order online at:
www.melabs.com

Development Tools for PIC® MCUs
*micro*Engineering Labs, Inc.

Phone: (719) 520-5323
Fax: (719) 520-1867
Box 60039
Colorado Springs, CO 80960

USB Programmer for PIC® MCUs
\$89.95 (as shown)

RoHS
Compliant

Programs PIC
MCUs including
low-voltage (3.3V)
devices



With Accessories for \$119.95:
Includes Programmer, Software, USB Cable,
and Programming Adapter for 8 to 40-pin DIP.



**EPIC™ Parallel
Port Programmer**
starting at \$59.95

LAB-X Experimenter Boards

Pre-Assembled Board
Available for 8, 14, 18, 28,
and 40-pin PIC® MCUs
2-line, 20-char LCD Module
9-pin Serial Port
Sample Programs
Full Schematic Diagram

Pricing from \$79.95 to \$349.95

PICPROTO™ Prototyping Boards

Double-Sided with Plate-Thru Holes
Circuitry for Power Supply and Clock
Large Prototype Area
Boards Available for Most PIC® MCUs
Documentation and Schematic

Pricing from \$8.95 to \$19.95

BASIC Compilers for PICmicro®

Easy-To-Use BASIC Commands
Windows 98/Me/2KXP/Vista

PICBASIC™ Compiler \$99.95
BASIC Stamp 1 Compatible
Supports most 14-bit Core PICs
Built-In Serial Comm Commands

PICBASIC PRO™ Compiler \$249.95
Supports most PICmicro® MCU Families
Direct Access to Internal Registers

Supports In-Line Assembly Language
Interrupts in PICBASIC and Assembly
Built-In USB, I2C, RS-232 and More
Source Level Debugging

See our full range of products, including
books, accessories, and components at:
www.melabs.com

ALL ELECTRONICS

C O R P O R A T I O N

QUALITY Parts
FAST Shipping
DISCOUNT Pricing

CALL, WRITE, FAX or E-MAIL
for a FREE 96 page catalog.
Outside the U.S.A. send \$3.00 postage.

RECHARGEABLE LITHIUM-ION BATTERY



iomega P/N 31021100. Lithium-Ion prismatic battery. 4.2 Vdc max. 900 mAh min. 54mm x 34mm x 7mm. 23mm leads with 2-contact female connector (2mm centers).
CAT# LBAT-60

\$2.50
each

LARGE, SURFACE-MOUNT PUSHBUTTON



S.P.S.T., normally-open, momentary pushbutton switch. 1.6" diameter metal body with mounting flanges, holes on 2.3" centers. Originally for automotive horn application. 0.84" diameter black push-button, 0.95" overall height. Packaged with 2 mounting screws.
CAT# PB-156

\$1.75
each

LOW VOLTAGE TESTER



NuTone # RCDT900. Convenient test light for 5-30 Volts AC or DC. Marketed as a Door Chime Diagnostic Tool, consists of an enclosed light bulb with two test leads. Light glows, brightness varying with voltage, when power is present. Leads snap into back of unit for compact storage.
CAT# LVT-2

\$2.50
each

12 VDC 1.5 A SWITCHING POWER SUPPLY



Input: 100-120Vac, 50/60Hz.
Output: 12Vdc 1.5A. 6' cord. 2.1mm coax power plug. Center positive. UL.
CAT# PS-12151

\$11.50
each

12V LIGHTED ROCKER SWITCH, 4-LENSES



S.P.S.T., on-off, 12V lighted rocker switch four interchangeable lenses, red, yellow, blue and green. Illuminated when switch is on. For accessories up to 25 Amps (300W). Snap-mounts in 0.94" diameter hole. 0.25"qc / solder terminals.
CAT# LRS-143

\$1.95
each

24" DUAL-SHIELDED CABLE W/ 3.5MM PHONE PLUGS



3.5mm stereo phone plugs on each end. Cable consists of two shielded single conductor cables. Great for ipods and other mini-audio players.
CAT# CB-461

\$1.25
each

10 for \$1.00 each

SAW III DIGITAL VOICE RECORDER



30 second voice recorder. 5.50" high. Operates on 2 AAA batteries (included).
CAT# SAW-3

\$2.00
each

10 for \$1.85 each

SOLAR CELL



Output: approximately 3 Volts @ 40 mA. 60mm square x 2.5mm thick epoxy-encapsulated silicon photovoltaic cell. Solid, almost-unbreakable module with solderable foil strips on backside. Ideal for solar-powered battery chargers and other projects.
CAT# SPL-61

100 for \$3.25 each

\$3.75
each

5 VDC DPDT MINI SIGNAL RELAY, 2A



NEC# EC2-5NJ. D.P.D.T. sub-miniature pc mount relay. Contacts rated 2A @ 30Vdc, 178 Ohm coil. 15 x 7.5 x 8.5mm high. Sealed. PC leads. UL, CSA.
CAT# RLY-532

\$1.40
each

PADDED MINI-POUCH



Ballistic nylon mini-pouch with keyring. Zipper closure. Interior elastic strap. Carry and store small items like removable memory cards, thumb-drives, stereo in-ear earphones, plug and jack adapters. A tough, well-crafted mini-carrying case. 3" x 2.5" x 0.9" Large quantity available.
CAT# CSE-83

50¢
each

50 for 40¢ each • 100 for 35¢ each

N-CHANNEL MOSFET, 55V 22A 0.06 OHM



N-channel SIPMOS Power Transistor Vds. 55V, 22A, 0.06 Ohms
CAT# BUZ101S

55¢
each

10 for 50¢ each
100 for 35¢ each

24VDC 6.5A POWER SUPPLY



Potrans #FS-15024-1M
ITE Power Supply
Input: 100-120V 4A
200-240V 2.3A
Output: 24Vdc 6.5A
150W switching power supply. Enclosed metal vented case. 7.875" x 4.35" x 1.96". Over voltage, over current and temperature protected. LED output indicator. Adjustable voltage output.
UL, CE, TUV.
CAT# PS-6524

\$24.95
each

Shop ON-LINE www.allelectronics.com
ORDER TOLL FREE 1-800-826-5432

MAIL ORDERS TO:

ALL ELECTRONICS CORP.
14928 OXNARD ST., VAN NUYS, CA 91411-2610

FAX (818) 781-2653 • INFO (818) 904-0524

E-MAIL allcorp@allcorp.com

NO MINIMUM ORDER • All Orders Can Be Charged to Visa, Mastercard, American Express or Discover • Checks and Money Orders Accepted by Mail • Orders Delivered in the State of California must include California State Sales Tax • NO C.O.D. • Shipping and Handling \$7.00 for the 48 Continental United States - ALL OTHERS including Alaska, Hawaii, P.R. and Canada Must Pay Full Shipping • Quantities Limited • Prices Subject to change without notice.

MANUFACTURERS - We Purchase EXCESS INVENTORIES... Call, Write, E-MAIL or Fax YOUR LIST.





GETTING STARTED WITH PICs

THE LATEST IN PROGRAMMING MICROCONTROLLERS

■ BY CHUCK HELLEBUYCK

EIGHT-PIN PROJECTS


I often receive great article suggestions and sometimes I receive pre-released products for review. I recently received a development setup that I found quite interesting, as it's targeted at my favorite audience—the beginner market. It is called the CHIPAXE system (see Figure 1) and it is designed to be an open source-style development tool initially based on the PICBASIC PRO™ compiler from microEngineering Labs. However, it can also be used with Assembly or C programming languages. Because the system is open source, you don't need to purchase a pre-programmed chip. It comes with a blank, eight-pin PIC12F683 eight-bit microcontroller from Microchip Technology. You can purchase this part just about anywhere, including from many of the advertisers in this magazine.

The board is not dependent upon a custom bootloader, as some open source systems require. The package relies on an interesting programmer/cable which is actually a clone of the Microchip PICkit™ 2 programmer; however, this isn't the only option. The board can also be used with an actual PICkit 2 or the latest PICkit 3 programmer, if you prefer. I'll update you on those programmers a little later. A breadboard version of the CHIPAXE development board is also available, and it gave me a great setup to revisit how to program an eight-pin microcontroller. Many beginners find it more comfortable to start with a smaller-sized and less intimidating microcontroller.


The CHIPAXE system uses In-Circuit Serial

Programming™ technology to program the chip and the board is powered from the programmer connection, so you don't need an external power connection. Figure 2 shows the breadboard module wired up to LEDs. I wanted to create a few simple projects for anyone just starting out with the PIC12F683. I initially created a traffic light project using the CHIPAXE board and the sample version of PICBASIC PRO. This is a great project to show a kid since a traffic light is something they immediately understand and it may get them interested in what you can do with a microcontroller. I will show you the traffic light project and then a few other sample projects for this small eight-pin chip.

■ FIGURE 1. CHIPAXE Starter Package.

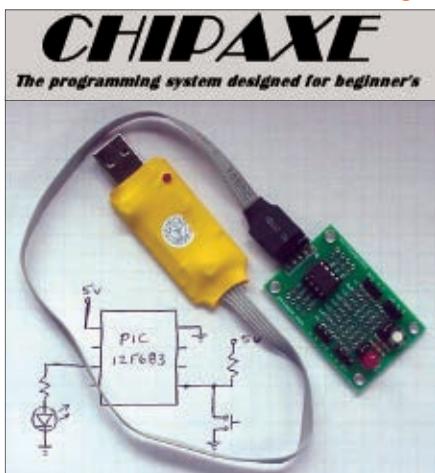

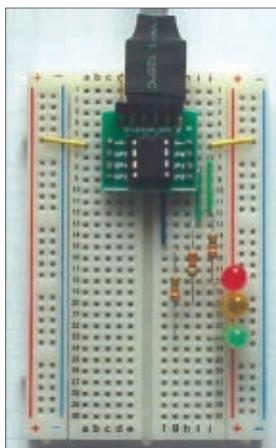■ FIGURE 2. Final LED Traffic Light Project.



LED TRAFFIC LIGHT

This project reproduces a traffic light with red, yellow, and green LEDs. The timing of each LED is separately controlled which allows you to control how long each color is lit. The project also shows how to control multiple LEDs from one microcontroller. The completed project is shown in Figure 2.

HARDWARE

This breadboard is available from All Electronics (www.allelectronics.com). It has letters designating columns and numbers indicating rows. This helps me in explaining the connections for those just getting started with building electronics. The connection table for this project is shown next and the schematic is shown in Figure 3.

Connection Table

Micro	- Pin 1 at C6
Vdd Jumper	- a6 to +rail
Vss Jumper	- j6 to -rail
Green Jumper	- j7 to j12
330 ohm	- i12 to i18
Red LED	- Anode j18, Cathode -rail
Green Jumper	- i8 to i13
330 ohm	- i13 to i20
Yellow LED	- Anode j20, Cathode -rail
Blue Jumper	- f9 to f15
330 ohm	- g15 to g23
Green LED	- Anode j23, Cathode -rail

SOFTWARE

The software is quite simple because it uses some of the commands that make PICBASIC PRO easier to use than many other compilers. The first steps involve making the I/O digital. When the PIC12F683 is first powered up, the I/O defaults to analog mode. The I/O pins share a connection to both analog and digital features. The ANSEL = 0 command line sets all the I/O pins to digital mode.

```
ANSEL = 0 ' Set I/O to digital
```

The PIC12F683 also has an internal comparator which can be shut down with the CMCON0 = 7 line.

```
CMCON0 = 7 ' Comparator off
```

The main program loop begins with the label "main" followed by a colon. We will use this as a marker in a future GOTO command line.

```
main:
```

The I/O pins on the PIC12F683 are referred to as general-purpose I/O pins, or GPIO. The internal register that controls these pins individually is also called the GPIO register. These can be controlled by writing to the GPIO register directly, but we would also need to set up the TRISIO register inside the PIC12F683. The TRISIO determines whether the pins are digital-input or digital-output pins. Both of these are automatically controlled with the HIGH or LOW command.

The GPIO.0 is the nickname for the GP0 pin. The software uses the HIGH command to place a high signal on that pin. This will light the LED. The PICBASIC PRO compiler doesn't care if you use capitals or lower case letters for the commands. The red LED is lit first for two seconds and then shut off to create the stoplight portion of the traffic light. All actions are on the GP0 pin which is connected to the red LED.

```
HIGH GPIO.0      'Light Red LED
PAUSE 2000      'Delay 2 second
LOW GPIO.0       'Red LED off
```

The green LED is next and it is lit for the same amount of time as the red LED. The green LED is connected to the GP2 pin.

```
HIGH GPIO.2      'Green LED on
PAUSE 2000      'Delay 2 second
LOW GPIO.2       'Green LED off
```

Finally, the yellow LED is lit for a short time and then

it turns off. The yellow is connected to the GP1 pin.

```
HIGH GPIO.1      'Yellow LED on
PAUSE 1000      'Delay 1 second
LOW GPIO.1       'Yellow LED off
```

The final step is to loop back to the main label to light the red LED and repeat the process.

```
GOTO main        'Loop Back to Red LED
```

NEXT STEPS

The logical next step is to change the delays to make the traffic light fit your application. If you wanted to make a real traffic light from a project like this, then the delays need to be a lot longer. There are three unused I/O pins, so adding three more LEDs for another crossing lane of traffic would be an option. Unfortunately, the GP3 pin is an input-only pin and cannot drive an LED. This is an example of where a larger-pin microcontroller might be a better choice.

SENSING A SWITCH


Many projects require some kind of human interface to control the operation. A momentary pushbutton switch is a very common way to do this. It can start and stop the operation, or speed up or slow down what the microcontroller is controlling. In order to do this, however, the software needs to recognize that a switch was pressed. This project shows a simple method of sensing a momentary pushbutton switch.

The software must monitor the switch continuously as part of the main loop of code, and then respond. In this project, the software lights an LED until the switch is pressed, at which point the LED shuts off. As long as the switch is pressed, the LED will stay off. As soon as the switch is released, the LED will once again light up. The completed project is shown in **Figure 4**.

HARDWARE

The hardware uses the same red LED connections as the traffic light project. The addition of the switch is shown in the schematic in **Figure 5**. The switch is wired as a low-side switch which means the circuit has a pull-up

FIGURE 3. LED Traffic Light Schematic.

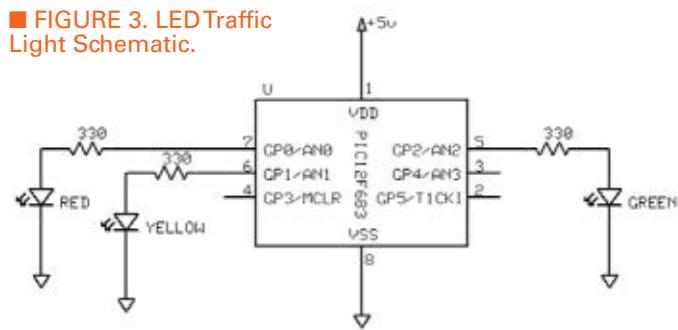



resistor to five volts so the input to the micro is high when the switch is not pressed and low when the switch is pressed. If the parts were reversed where the switch was connected to five volts and the resistor to ground, then it would be a high-side switch.

The software will test the input pin GP4 to see if it changes to low, indicating the switch has been pressed. The GP4 pin will be configured as an input pin in the software, so all we need from the hardware is a known idle state which is determined by the pull-up resistor. The connection table for the breadboard is as follows:

Connection Table

Micro	- Pin 1 at C6
Yellow Jumper	- a6 to +rail
Yellow Jumper	- j6 to -rail
Green Jumper	- j7 to j12
330 ohm	- i12 to i18
Red LED	- Anode j18, Cathode -rail
Yellow Jumper	- j22 to -rail
Orange Jumper	- f22 to e22
Orange Jumper	- b22 to b19
White Jumper	- b8 to b17
10k ohm	- a17 to +rail
Switch	- d17 to d19


SOFTWARE

The software starts with the same I/O setup, but now adds a new line to make the GP4 pin an input for the switch. This command acts on the internal TRISIO register of the PIC12F683. That register determines whether the I/O pin is an input or output. Each bit of that eight-bit register represents a pin. A 1 in the GP4 slot makes it an input and a 0 makes it an output. The INPUT GPIO 4 command line sets the GP4 pin to a 1 for input mode.

```
ANSEL = 0 ' Set I/O to digital
CMCON0 = 7 ' Comparator off
INPUT GPIO.4
```


The main label starts us off again, followed by an IF-THEN-ELSE command from the PICBASIC PRO compiler. This command will test the equation after the IF, to determine whether it is true or false. If the equation is

FIGURE 4. Final Switch Sensing Project.

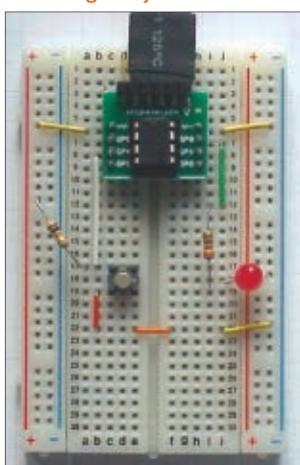

true, then the command following the IF command line will be executed. If it is not true, then the command

FIGURE 5. Switch Sensing Schematic.

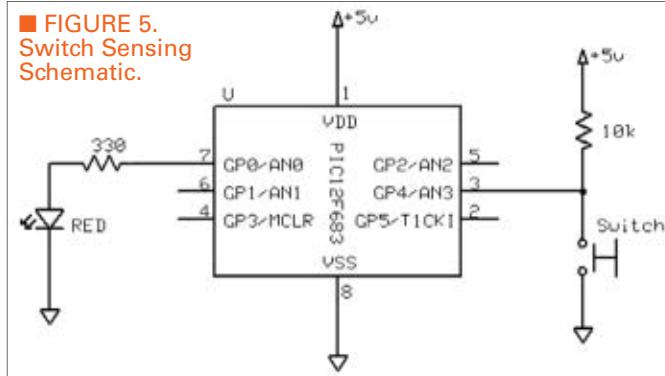

following the ELSE line will be executed. In this case, if the GP4 pin is high — meaning the switch is not pressed — then the red LED is lit. If instead the GP4 pin is low — meaning the switch is pressed — then the LED is shut off.

```
main:
If GPIO.4 = 1 then
HIGH GPIO.0      'Light Red LED
Else
LOW GPIO.0       'Red LED off
ENDIF
```

A GOTO statement completes the loop and sends control back to the main label, so the switch can be tested again.

```
GOTO main      'Loop Back to Red LED
```

NEXT STEPS

You could add the extra LEDs from the traffic light project and change to red, yellow, or green with the push of a button. You could also create a speech timer where the green indicates time is okay, yellow means time is running out, and red means time is up. The switch starts the process. You could also just reverse the logic and have the LED light when the switch is pressed. This is a very simple change that I'll let you figure out.

The thing to remember is that the switch represents several different options. A Sharp GP2D15 obstacle-detection sensor can easily replace the switch for robotic applications. A magnetic reed switch could replace the switch to create a simple alarm system. Any device that has a simple open-collector output and a digital on/off output state can replace the switch.

SENSING LIGHT

The PIC12F683 has a built-in analog-to-digital converter (ADC), so I'll use that to read a cadmium sulfide (CdS) cell. A CdS cell or photoresistor is a resistor whose resistance decreases with increased light exposure. It can also be referred to as a light-dependent resistor or photoconductor. You can get a pack of them from RadioShack under part number 276-1657.

The PICBASIC PRO compiler has an ADCIN command to make this another easy task to complete. I used an eight-bit resolution result that worked perfectly. As the light

changes, I have the ADC value tested. If the result is a high value (high resistance), then it is dark out and the LED lights up. **Figure 6** shows the final setup.

HARDWARE

The schematic is very similar to the switch schematic, except the switch is replaced by the CdS cell. The pull-up resistor is also lower, but it could easily

be replaced by a potentiometer so you have some sensitivity adjustment. The connection table is shown below, along with the schematic.

Connection Table

Micro	Pin 1 at C6
Yellow Jumper	- a6 to +rail
Yellow Jumper	- j6 to -rail
Green Jumper	- j7 to j12
330 ohm	- i12 to i18
Read LED	- Anode j18, Cathode -rail
Yellow Jumper	- j22 to -rail
Orange Jumper	- f22 to e22
Yellow Jumper	- b22 to b18
White Jumper	- b8 to b17
1k ohm	- a17 to +rail
Cds Cell	- d17 to d18

SOFTWARE

The start of the software requires a different setup since we will be using the GP4 pin as an analog input. Using the binary designation in the PICBASIC PRO compiler allows me to easily set the AN4 bit of the ANSEL register making it analog, while the rest of the I/O pins are zero or set to digital mode.

```
ANSEL = %00001000 ' Set I/O to digital except
                     ' AN3/GP4 is Analog
```

Once again, the comparators are shut down.

```
CMCON0 = 7 ' Comparator off
```

The state of GP4 has to be set to input mode using the TRISIO register which can also set the remaining I/O pins to outputs. GP3 is always an input.

```
TRISIO = %00011000 ' GP4 input, GP2 thru GP0
                     outputs
```

The ADCIN command requires some setup parameters to be established such as ADC resolution, ADC clock source, and sampling time. These are easily done with DEFINE statements.

```
' Define ADCIN parameters
Define ADC_BITS     8      ' Set number of bits
                           in result
Define ADC_CLOCK    3      ' Set clock source
                           (3=rc)
Define ADC_SAMPLEUS 50    ' Set sampling time
                           in us
```

A variable is established to store the ADCIN result.

```
adval var byte      ' Create adval variable
                     ' to store result
```

The main label establishes the main loop, followed by the ADCIN command line where the CdS cell is read.

```
main:
ADCIN 3, adval      ' Read channel AN3 to adval
```

After the value of the CdS cell is stored in the adval variable, it is compared to the value 150. If it is less than 150, then the LED is off. If the value is greater than 150,

then it is dark and the LED is lit using the HIGH command.

```
If adval > 150 then 'Light LED if in the dark
High GPIO.0           'Light all LEDs
ELSE
Low GPIO.0
ENDIF
```

Another GOTO statement completes the main loop.

```
goto main           'Loop Back to test
                     'potentiometer
```

NEXT STEPS

Changing the threshold value from 150 to something higher or lower will determine how dark it has to be to light the LED. The limit is 0 to 255 since we used an eight-bit result. As with the switch project, other sensors can replace the light sensor. For example, a thermistor could replace the light sensor to measure temperature. A potentiometer could be used to create a manual interface. If you remove the pull-up resistor, then a Sharp GP2D12 object-detection sensor that produces a variable output voltage can be directly read by the analog pin for more accurate robotic obstacle detection.


I would like to create more projects using this great eight-pin setup, but I'm running out of time and space, as I wanted to cover some news that has happened since my last article. Give this little eight-pin part a try in your own setup and see what you can come up with.

PICBASIC PRO COMPILER

In a previous article, I mentioned that you needed to use Microchip's MPLAB® IDE version 8.15 or earlier with microEngineering Labs PICBASIC PRO compiler. This is no longer the case because microEngineering Labs recently released a new version of the compiler that works with the latest version of the MPLAB IDE. The setup instructions are slightly different from the previous method of getting the PICBASIC PRO compiler to work within the MPLAB IDE. Full details are available at <http://melabs.com/support/mplab.htm>.


Along with this update comes expanded chip support in the sample version of the PICBASIC PRO compiler. What is really great is that microEngineering Labs added the PIC16F88X parts to the supported microcontroller list. This allows you to use eight- to 40-pin parts without the need for external MCLR pull-up or crystals/oscillators in order to test the compiler. After you use this compiler for a while, you'll find the full-priced version of it

■ FIGURE 6. Final Light Sensor Project.

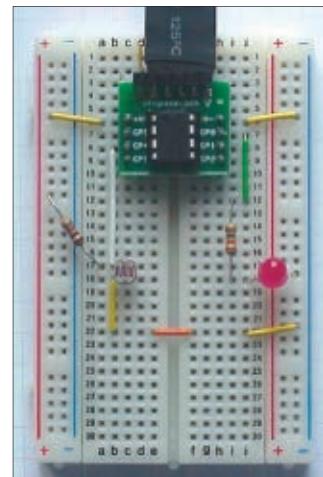



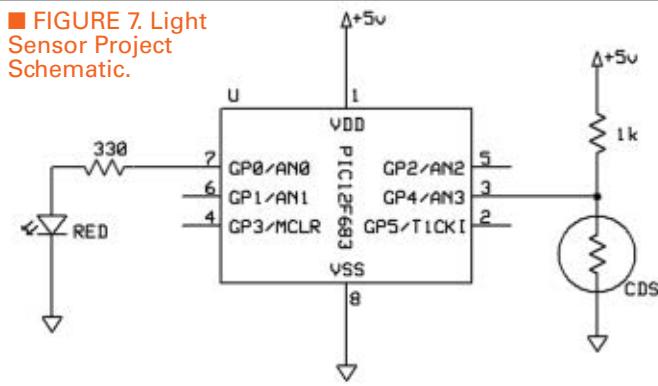■ FIGURE 7. Light Sensor Project Schematic.



to be well worth the investment.

MICROCHIP'S PIC16F1 MICROCONTROLLER FAMILY

Microchip recently released a new series of PIC16F parts called the PIC16F193X family. Featuring the company's enhanced mid-range eight-bit core, these parts offer many more features than the previous PIC16F family such as higher program memory (up to 32K), a faster internal oscillator (16 MHz), and a lot more RAM (up to 4K). This allows these new microcontrollers to offer more peripherals such as additional timers and PWM channels. More communication channels are expected to be

available on future parts. These parts will be easily identified by the four-digit number after the letter F, starting with a 1. More details are available at www.microchip.com/enhanced.

MICROCHIP DEVELOPMENT TOOLS

Microchip recently released the PICkit™ 3 Debug Express and MPLAB ICD 3 tools which offer much higher programming speeds and better debugging capabilities than previous versions. There is also a higher-end MPLAB REAL ICE™ tool. As new products are released, you will need the PICkit 3 or MPLAB ICD 3, as the PICkit 2 and MPLAB ICD 2 will not support PIC16F193X parts.

CONCLUSION

I hope you enjoy the topics I've covered, but feel free to let me know your thoughts either way by emailing me at chuck@elproducts.com. I've also started a free newsletter at www.elproducts.com, so be sure to sign up for it. As this is my last column before the holidays, be safe and I hope you have a happy one. **NV**

Complete code listings are available at www.nutsvolts.com.

NOTE: The Microchip name, logo, MPLAB, and PIC are registered trademarks of Microchip Technology, Inc., in the USA and other countries. In-Circuit Serial Programming, PICkit, and REAL ICE are trademarks of Microchip Technology, Inc., in the USA and other countries. All other trademarks mentioned herein are property of their respective companies.

FRONT PANELS & ENCLOSURES

Customized front panels can be easily designed with our free software
Front Panel Designer

• Cost-effective prototypes and production runs

• Wide range of materials or customization of provided material

• Automatic price calculation

• Fabrication in 1, 3 or 7 days

Sample price:
\$43.78 plus S&H

FRONT PANEL EXPRESS

www.frontpanelexpress.com
(206) 768-0602



AP CIRCUITS
PCB Fabrication Since 1984

As low as...
\$9.95
each!

Two Boards
Two Layers
Two Masks
One Legend


Unmasked boards ship next day!

www.apcircuits.com







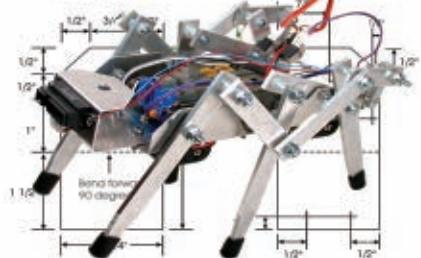

■ BY VERN GRANER

TRY, TRY AGAIN

"I have not failed. I've just found 10,000 ways that won't work."
— Thomas Alva Edison

IF AT FIRST YOU DON'T SUCCEED ... DON'T TAKE UP SKYDIVING! Yes, I know "try again" has to be one of the oldest work-related clichés. However, many times if you turn over a dusty old cliché, you find a kernel of truth nestled under it. In this particular case, that kernel is persistence pays. My direct experience has taught me that nothing is ever as easy as it looks.

Experience has also taught me that when things get complicated, a methodical and consistent approach is typically the best course of action. Problems seem to be a natural part of development, so encountering them should come as no surprise and you certainly shouldn't let possible (or actual) problems stop you from building. If you've started building, it means you have something to work on, something to improve.

YOU MAY ASK YOURSELF HOW DID THIS GET HERE?

Sometimes, when we see a finished project, we can only picture it in its finished form. It seems as if it sprung fully-formed from the mind of the creator directly into being. In my career, this has never been the case. I have to design, then prototype, then test (lather, rinse, repeat!). I evaluate what works in the prototype and what doesn't. I then revisit the design and make changes. Sometimes the creation and testing of a prototype reveals better ways that the idea might be implemented. Other times, things just don't work no matter how the diagrams, datasheets, and experts insist it should!

In this month's article, I'm going to give you a behind the scenes tour of the more notable projects I've been involved with and the hidden problems we encountered along the way. I hope to document how these projects would never have come to fruition if not for many people's tenacity in overcoming problems and improvising solutions. I'll begin with one of the single biggest projects upon which I've worked, The Ponginator.

THE PONGINATOR MK-II

Back in the December '07 issue of *Nuts & Volts*, I introduced The Ponginator MK-I, a 20 foot tall smoke-spewing, light-flashing, music-playing, siren-wailing robot with quad-barrel

pneumatic ping pong ball cannons. It was the centerpiece of The Robot Group's presentation for the very first Maker Faire in Austin, TX. In the days leading up to that event, we had struggled with various issues including multiple prototype ping pong ball propulsion systems, leaky air lines, and a stripped cannon pan motor.

In spite of those challenges, the Ponginator was assembled on-site the day before Maker Faire opened and performed much more smoothly than anyone could have imagined. The Ponginator was an unmitigated success. It operated amazingly well for something that, in only 30 days, went from a pencil sketch to towering over the arena floor. This was just the beginning of the Ponginator's career, and more problems would present themselves as we tried to adapt it to changing requirements.

THE PONGINATOR MK-II

When it came time for the next event, we figured it would be easy to just bring out the Ponginator and set him right back up. Unfortunately, when we visited the proposed site, we discovered that we would be in an outdoor area. In the original design, we hadn't considered the challenges an outdoor venue would pose. For starters, the MK-I used a two-story construction scaffolding as a frame and was wrapped with a tarp. There was concern over how we would keep the whole thing from toppling over if the wind picked up. To be safe, we needed to redesign the frame and find something fairly substantial to use as an anchor. Time to put on the thinking caps!



■ FIGURE 1. The Ponginator MK-II frame test-fit on the van.



■ FIGURE 2. Testing the pneumatic cannons on the new frame.



■ FIGURE 3. Test-fitting the Ponginator MK-III on the new bucket lift.

As we would need transportation to and from the event anyway, we decided my full-sized Ford van could act as both the frame and the anchor. We fabricated a new PVC-pipe frame from scratch that mounted to the top of the van (**Figure 1**). We then mounted the crossbar and hung the pneumatic cannons to make sure they could still move properly (**Figure 2**). Though we still had the original Ponginator "skin," we discovered we would need to make a new one as the old one had both a hole cut for a video display (not practical in the MK-II design) and was also about five feet too big for the new frame.

In spite of having to do a thorough retrofit, on the day of the show we managed to assemble the Ponginator for the first time in downtown Austin without any major issues. The MK-II was a smash hit, thrilling crowds with his siren wail and catchy dance tunes. This event also saw the unveiling of the Ping Pong Printer, which didn't exactly go as planned either (are you seeing a trend here?), but we'll touch on that in a bit.

THE PONGINATOR MK-III

After this last show was done, the Ponginator again went into a storage shed until the next big event: Maker

■ FIGURE 4. The Ponginator MK-III towering 30 feet up in the air.



■ FIGURE 5. The Ping Pong Printer with plastic water jug hopper.



Faire Austin 2008. By the time this event rolled around, I had sold the van so we no longer had our "base." However, as luck would have it, my brother Walt had recently purchased a 30 foot hydraulic bucket-lift for his construction company and was happy to let us use it.

We brought all the parts out of storage and mounted them on the lift bucket (**Figure 3**). After fabricating new brackets, adding shelves for the speakers, and mounting the air compressor, we towed the lift out from under the trees and extended it to its full height of 30 feet (**Figure 4**). It looked AMAZING!

When it was time for the event, we trucked the lift out to the Maker Faire show but on the way, one of the gear motors that positions the cannons stripped due to stresses on the mounts created by the movement of the trailer while being towed. We had to quickly swap motors out on the show floor when we arrived. As before, we put all the new electronics and pneumatics together for the first time right there at the show. Once again, the Ponginator lived up to its reputation, not only earning us another Maker Faire "Editors Choice" Blue Ribbon, but also being immortalized on a MAKE poster, and then to headlining on the GeeksAreSexy.com website, among others.

This is a perfect example of how a project can still enjoy continuous success in spite of changing circumstances if the people involved persist. Which brings us to the Ping Pong Printer — a rather problem-plagued device that grew out of the Ponginator project.

PING PONG PRINTER PROBLEMS

The Ping Pong Printer was featured in my February '08 column and was basically a solution to an economic problem. Turns out the Ponginator uses up lots of ping pong balls when it's in operation. As we wanted the ping pong balls to be souvenirs (and not just trash), we had some custom-printed ping pong balls created for the MK-I. Though these worked fine, they turned out to be very expensive (on the order of about .60 cents each!).

The Ping Pong Printer was designed to allow us to create our own "ordnance" for the Ponginator. It was built by a team of folks from The Robot Group including myself (programming), Rick Abbott (metal/plastic fabrication), and Marvin Niebuhr (carpentry).

THAT JAMMED JUG!

When I first designed the Ping Pong Printer, a five



DER MAGNETFELDER DETEKTOR: DAS BLINKENBOARD!

by Nyssa Hughes and James Delaney

As promised, we continue our series on new uses for Das BlinkenBoard. This month, we feature an amazing and simple mod from the "UnfocusedBrains" of James Delaney and Nyssa Hughes. By adding a Hall-effect sensor and a 2K resistor, they have turned the mild mannered Das BlinkenBoard into a magnetic field detector! It uses the LEDs as a bar-graph to display both relative field strength and magnetic pole polarity of magnets held near the sensor. In their own words, here's how James and Nyssa did it:

Because our home laboratory was without a way to measure relative magnetic field strength, we figured it was time to build a simple Gauss meter. Turns out it was really easy! We started by reading a few datasheets, then settling on a Honeywell SS49 analog position sensor (which is a type of Hall-effect sensor). By connecting the part to a voltmeter, we were able to detect magnetic fields from various magnets and read voltage levels from the SS49 to determine the field's relative strength.

Not wanting to stop there, we decided to build a steam-punk inspired "prop" version of a magnet detector. Fortunately, we had a Das BlinkenBoard on hand, so James built a cable to connect the SS49 to the BlinkenBoard (**FIGURE A**). When it came time to program the microprocessor on the BlinkenBoard, James ran into some challenges when he discovered that

the datasheet for the SS49 sensor was very confusing. Our friend Paul Atkinson came to the rescue (he always seems to be helping us out!). He read the datasheet and told James that a 2K ohm "load" resistor would be needed to make the SS49 work according to specifications. We simply added the resistor and *Der Magnetfelder Detektor* (DMD) was born.

Now that we had the unit working, the final step was to build a snazzy case in which to place the electronics. Since this is a prop version of a magnet detector, we decided to build it as a piece of

foam covered in an ink jet color-printed "skin." Nyssa cut two pieces of foam into a 3" x 5" rectangle to make the case deep enough. She then cut a BlinkenBoard-sized hole in both pieces. As James designed the custom graphics



FIGURE B. The printed cover for "Der Magnetfelder Detektor."

gallon water jug was sitting on a cooler by the kitchen table where I was sketching. I envisioned the jug filled with ping pong balls (like a gumball machine) and a motor "stirring" the balls to make sure they flowed down the bottle neck to the printer. I figured that would make a simple and easy "hopper" to feed blank ping pong balls into the printer. It looked good on paper and once built, it worked fine with a handful of ping pong balls. However, once we

FIGURE C. The Das BlinkenBoard mounted in the foam enclosure.

for the skin, Nyssa glued the two pieces of foam together. The graphic was printed, sprayed with a layer of protective acrylic, and cut out (**FIGURE B**). The SS49 sensor was taped to the back of the paper, with the sensor facing up (**FIGURE C**).

Next, Nyssa stuffed the BlinkenBoard into the foam frame with the circuit. This allowed room to run all the cables for the LEDs in the space beneath the circuit board. She pushed the SS49 sensor cable into a gap between the circuit board and the foam, and plugged it into the circuit board.

Then, it was time to glue the graphic to the foam and drill the holes. The graphic was glued only to the face of the DMD. Using a drill press made quick work of the eight holes. With the holes drilled, Nyssa was about to stuff the LEDs through, but first needed to figure out which LED was "South." The first LED in the series is the one that goes into the South hole. The eighth LED is the one that goes into the North hole.

The LEDs were poked through the holes in sequential order. After some adjustments, the LED cables got organized, plugged in, and taped down. Nyssa poked a hole into the side of the paper-covered foam through



which to run the power. She glued the sides of the DMD and added some foam feet (**FIGURE D**).

Now it was time to play with magnets! By holding a magnet to the DMD's printed button, you can determine the general strength (i.e., one LED versus eight LEDs) and the alignment of the magnet. If the bar graph starts on the North side, you are holding the North pole of the magnet to the sensor and vice-versa.

Please let us know if you configure your Das BlinkenBoard as *Der Magnetfelder Detektor*. Also, please let us know if you do something fun and interesting with your own Das BlinkenBoard. You can send your emails to vern@txis.com.

DER MAGNETFELDER DETEKTOR RESOURCES

Honeywell SS49 Sensor from Mouser
www.mouser.com/ProductDetail/Honeywell/SS49/?qs=sGAEpiMZZMvhQj7WZhFIA%252bM%3d

James Delaney's Blog
www.unfocusedbrain.com/

Nyssa Hughes' Blog
www.nyssa.com/
http://en.wikipedia.org/wiki/Hall_effect

Das BlinkenBoard Web Page
www.DasBlinkenBoard.com

Source Code
www.nutsvolts.com/index.php?/magazine/downloads/

filled up the entire water jug, the first problem appeared.

At the beginning of the print cycle, the stirring rod system would activate as designed but, instead of the balls mixing around, they would "stack up" and stick to each other. This would cause the stirring rods to bind and resulted in the motor attempting to back spin, twisting and eventually tearing up the motor wires.

Upon closer inspection, we discovered that — unlike



the smooth-surfaced gumballs I used for inspiration — ping pong balls are created with an abrasive surface so they can get traction on the ping pong paddle and table. Unfortunately, this extra friction caused the balls to stick together in the jug, jamming the stirring rods. The only way to un-jam the system was to fill the jug to less than 10% of its capacity (**Figure 5**) which really defeated the purpose of the jug itself. This was about the time we noticed a second problem with the design (insert deep sigh here).


It seems that rotating the ping pong balls inside the plastic jug caused them to build up a static electric charge! This would cause the ping pong balls to cling tenaciously to the sides of the jug making the stacking/jamming problem worse and, of course, stopping them from dropping down through the indexer to the print pedestal (insert second deep sigh here).

DOES SIZE REALLY MATTER?


As we were pondering what to do about the sticking, stacking, and static problems, our bulk-order of blank white ping pong balls arrived. We were excited by this good news and dumped a bunch of these new balls right into the jug in the hopes they would be smoother and might alleviate the jamming. No such luck. These new balls jammed the exact same way. We weren't getting off that easy! We then dumped out the jug and put just a handful of these new balls back in for testing. We activated the printer and the first ball dropped right onto the pedestal for printing as expected (**Figure 6**). When the printing was done, the "indexer" (**Figure 7**) started to cycle, then jammed without releasing the second ball. We removed the jammed ball and tried again. Same thing, the indexer was stuck and would not release the second ball. A lot of head scratching later, we discovered the root cause of the indexer jams.

It turns out that there are two "types" of ping pong balls. The first type is "professional" 40 mm balls and the second type are "hobby" ping pong balls that are 38 mm. We had started buying the test balls from local sporting goods stores and they were of the 40 mm variety. Subsequently, when Rick had machined the parts, he had used 40 mm as his reference size. When the indexer would try to cycle, it would bump into the bottom edge of the next ball in line to be printed and stall without completing the cycle. Rick took the

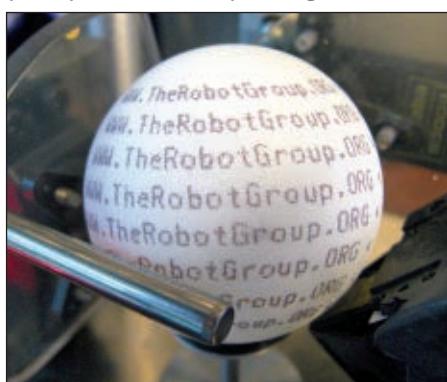■ FIGURE 6. A ping pong ball on the print pedestal after printing.



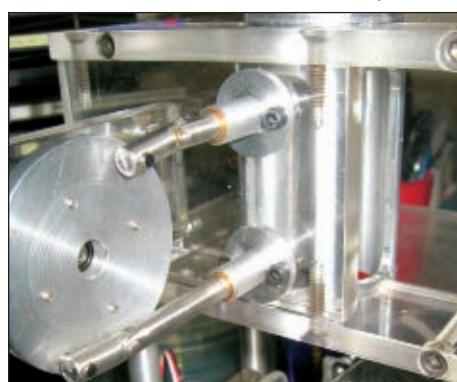■ FIGURE 7. The indexer stage that controls the fall of balls into the printer.



printer back to his shop and reworked the indexer push-bars to accommodate the 38 mm balls. Once this was done, the bulk purchased balls worked fine but we still had the existing multiple water jug issues to contend with.

CHANGE TO CHAIN DRIVE


When Rick had the Ping Pong Printer at his shop to re-engineer it for the 38 mm balls, he also took time to look at the plastic jug and try to come up with a new way to serve ping pong balls to the printer. After a few different designs were tossed around, he settled on an ingenious chain drive belt-scoop feed system which he then fabricated from aluminum, polycarbonate plastic, and steel (**Figure 8**). This new system would ferry the balls up to the top of the Ping Pong Printer, then let them roll down a ramp and drop into the indexer. This new design solved both the static problem as well as the stacking/sticking problem, but at the cost of a bit more software complexity. I had to figure out how to sense when to run the motor and — more importantly — when to stop it. To deal with this, I added an IR beam-break detector to determine when a ball was rolling down the ramp. A bit of coding had the software turning on the belt drive motor, waiting for a ball to occlude the sensor, then switching the motor off. With these modifications, the new and improved Ping Pong Printer was all ready to go.

Since then, we've used the Ping Pong Printer not just to make "ammo" for the Ponginator, but to create souvenirs for many events such as movie premieres (**Figure 9**), South By South West Austin, and multiple Dorkbot events. Around this time, the video of the Ping Pong Printer in action (with its original water jug) was picked up by a number of tech-blogs and ended up with over 30,000 views (and counting)!

NOTHING EVER GOES AS PLANNED

The point I'm trying to make with all this detail on what went wrong and how it was overcome is that we have yet to encounter a problem that could not be bested with the proper amount of perseverance. As the above examples show, given the right motivation and the right people, you can overcome just about any engineering challenge. Just expect that Murphy is alive and well and living in your

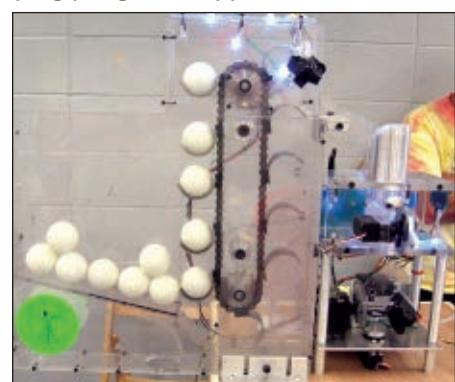■ FIGURE 8. The new chain-drive ping pong ball hopper.





■ FIGURE 9. The Ping Pong Printer at a movie premier in Austin, TX.

projects, but with the right team, and/or the right attitude, he can be evicted. You just have to learn to manage the stress.

HOW DO YOU SPELL "SUCCESS?"

For many of us (me included!), success is spelled "S-T-R-E-S-S." When a deadline is looming, you're staring down the throat of a killer problem, and you have no idea of how to solve it, it's time to try and regain perspective. Take a deep breath and a step back. Look at what you're doing, what you've accomplished, and envision how you would like things to come out. Remember the bottom line: Making things is supposed to be fun! Unfortunately, the price of this type of fun is sometimes a bit of stress (okay, sometimes more than a bit!). Being nervous, feeling pressure, getting headaches, lack of sleep, worrying, and then worrying some more, then worrying about worrying ... The point is to "keep your eye on the prize."

Bear with me as I wax a bit philosophical here; projects like these are supposed to be the events that – when you look back on your life – clearly stand out as landmarks along the twisted path of this mortal coil (hmm ... I wonder how many uH a mortal coil has ... but I digress ...). I don't know about you, but when I turn around and examine my life there are long gray blurs of continuous, monotonous, "work." Swaths of the regular "nine to five" stuff that consumes much of my life. Honestly, I can't tell you what I was doing at this time and date exactly 10 years ago, or even 10 months ago! However, I can tell you all about my first Maker Faire in San Mateo, CA and going out to San Francisco to attend RoboGames. I can tell you about the first First Night Austin, and the second First Night Austin, and I can also tell you all about the first Robot Group meeting I attended. I can tell you all about the first article I had published in this magazine (yes, writing can be a project!).

For me, these projects really stand out when I look back on my life. I can also tell you that each and every one of these memorable events was surrounded by stress. It was the price of admission. The interesting part is that each of us gets to set that ticket price. If we choose to relax, take the long view, and realize this isn't rocket

RESOURCES

Maker Faire Austin
<http://makerfaire.com/pub/e/2097>

Ponginator in *Nuts & Volts*:
<http://nutsvolts.textricity.com/nutsvolts/200712#pg84>

The Robot Group
www.TheRobotGroup.org

The Ping Pong Printer in
Nuts & Volts
<http://nutsvolts.textricity.com/nutsvolts/200802#pg14>

The Original Ponginator Video:
<http://www.youtube.com/watch?v=iPS0>

FYHywJw
 The Ponginator featured on
 GeeksAreSexy.com:
<http://www.geeksaresexy.com/2009/02/10/feature-the-ponginator-a-robotic-combination-of-king-kong-and-ping-pong/>

The Original Ping Pong
 Printer Video:
<http://www.youtube.com/watch?v=8Ep5OC3E021>

The Ping Pong Printer on the net:
<http://tinyurl.com/161>

The Creation of the Therping
<http://nutsvolts.textricity.com/nutsvolts/200604#pg50>

science (well ... maybe in some cases it is), it might help to reduce that price.

Remember: ELECTRONICS IS SUPPOSED TO BE FUN! Treat it accordingly. Build a project, draw a drawing, create a monster, find a team, form a team, do something that challenges you. Take some chances. But for cryin' out loud, HAVE FUN with it! And please, PLEASE take care of yourself so you can be healthy and ready to PLAY! If you have questions, comments, or would like to share your project experiences, feel free to drop me an email. As always, I can be reached at vern@txis.com. **NV**

**Save Up To 60% On
Electronic Components**



10A Dual Battery Solar Regulator

- * Automatically Switches between Batteries depending on the state of Charge
- * Microcontroller Control with Serial Mode
- PWM Control for High Efficiency
- * Suitable for 12V and 24V Systems

Only \$42.90



Huge Range of Solar Cells

- * From 0.5V to 9V Outputs
- * Larger Solar Panels Also Available
- * Ideal for Projects, Experimentation and Battery Charging

Starting From \$1.20



Upgraded ET-avr Stamp Module

- * Utilizes the ATmega128 Microcontroller with 128k Flash Memory
- * A/D, SPI, I2C, PWM All Supported
- * Up to 53 I/O Points
- * Ideal Embedded Controller

Only \$19.90

We are your one-stop shop for Microcontroller Boards, PCB Manufacture and Electronic Components

www.futurlec.com

ELECTRONET

www.canakit.com

- Over 200 Kits & Modules to choose from!
- Easy Worldwide Online Ordering
- Fast Delivery & Same Day Shipping

FM Transmitters • Timers • Audio Amplifiers • Motor Controllers



ramsey
www.ramseykits.com

AM/FM Broadcasters • Hobby Kits
Learning Kits • Test Equipment
...AND LOTS OF NEAT STUFF!



superbrightleds.com

Component LEDs - LED Bulbs - LED Products
Super Bright LEDs Inc. St. Louis, Missouri - USA superbrightleds.com

RobotShop
.com



Serial LCD & LED

www.melabs.com

beta
LAYOUT
TOLL FREE
1877 3908541

PCB-POOL
WWW.PCBPOOL.COM

Adapt9S12C

Just plug it into your solderless breadboard! Perfect for school & hobby projects!

www.technologicalarts.ca

- SPI, SCI
- CAN, RS232
- 10-bit A-to-D
- Hardware PWM
- Input Captures
- Output Compares
- 32K or 128K Flash
- 3V/5V Operation
- Asm, BASIC or C

USB

Add USB to your next project—it's easier than you might think!

DLP
Design

- USB-FIFO • USB-UART • USB/Microcontroller boards
- RFID Reader/Writer • ZigBee Ready Transceivers

www.dlpdesign.com

Absolutely NO driver software development required!

BiPOM Electronics, Inc. Your One Source for µController Systems
ARM, AVR, PIC, 2851, 580X, STAMP and others

µController Boards
Peripherals
Development Tools
Emulators
Programmers
Robotics

GadgetPC ARM9 USB Computer with Linux

www.bipom.com

PAIA
paia.com
Electronic Music Kits and More

Music/Tutorials/Kits
Analog Synthesizers
Guitar Effects
Tube Electronics
Studio Gear


Sheet Metal Fabrication



Complete Fabrication Center
Integrated Ideas & Technologies, Inc.
Precision Laser, Waterjet, Plasma, Machining,
Forming, and Welding Capabilities
www.iitmetalfab.com

Pololu

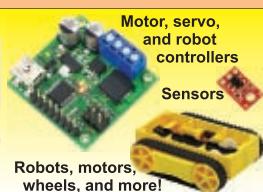Robotics & Electronics
3095 E. Patrick Ln. #12, Las Vegas, NV 89120
www.POLOLU.com 1-877-7-POLOLU



A new era of secure RF

www.CipherLinx.com

NUTS AND VOLTS

EVERYTHING FOR ELECTRONICS

5 years worth of great articles & projects on CD-ROMs. \$24.95 ea.

www.store.nutsvolts.com/home.php?cat=105

ALL ELECTRONICS CORPORATION

Electronic Parts & Supplies Since 1967

5 CD-ROMs & Hat Special
Only \$105.95 (includes shipping)
www.servomagazine.com

For the ElectroNet online, go to
www.nutsvolts.com and click **Electro-Net**



Follow along with this series!
Joe's book & kits are available in our
webstore at www.nutsvolts.com

Arduino, Some Loose Ends

by Joe Pardue

We are nearing the end of our Workshops that introduce the Arduino Projects Kit (available from Nuts & Volts and Smiley Micros). This month, we will look at several seemingly unrelated topics that we will need to understand before next month's article on simple motor speed control. We will learn about external interrupts, using the Arduino IDE Serial Monitor to get real data from the PC serial port to the Arduino board, and optical isolation of voltages.


Using External Interrupts To Detect Edges

One of the things you might want a microcontroller to do is perform a service only when a certain external event occurs. For instance, you could put an IR laser beam across a door and have the microcontroller monitor the beam so that when someone passes through the door breaking the beam, the microcontroller turns on the lights (or drops a bucket of water on the intruder's head or some such action). If this is the only thing the microcontroller has to do, then


it can be dedicated to polling the sensor full time in the loop() function where it would repeatedly run an `isItTrippedYet()` function that checks the sensor. Polling would drive a person nuts (think of driving kids who are yelling: 'are we there yet,' 'are we there yet,' 'are we there yet'...) but fortunately microcontrollers don't (yet) care what they are doing, so don't feel sorry for them if you give them a really boring task. Anyway, it's not like they can retaliate (yet).

Consider the case where a system has lots of other tasks to perform (maybe it's monitoring dozens of doors and the water levels in all the drop buckets). If it is polling each sensor, then someone could enter the room and be beyond the drop zone before the system even knows they are there. It is very common to conceptually divide up a microcontroller's work into two groups: one group of routine tasks that can be done any old time and another group of special tasks that

■ FIGURE 2. Edge Detection Schematic.

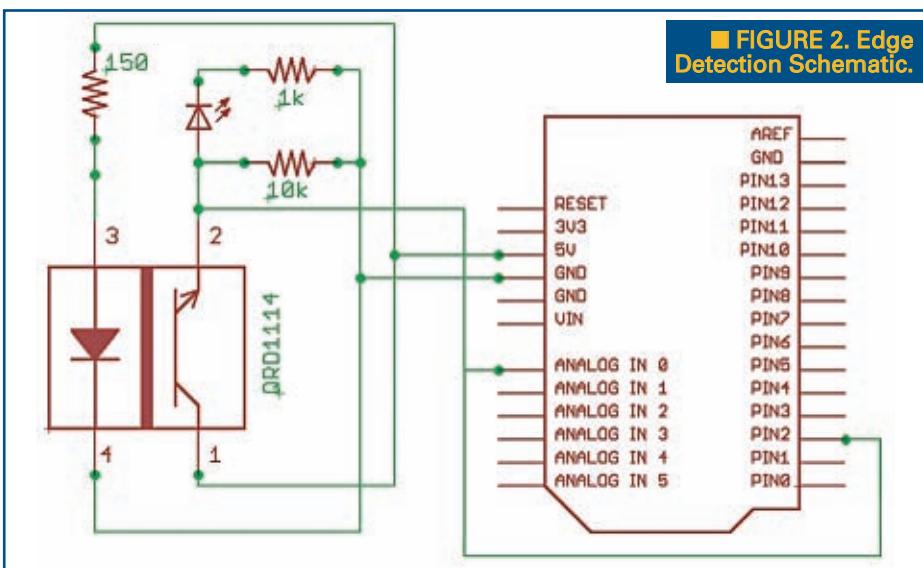

■ FIGURE 2. Edge Detection Schematic.

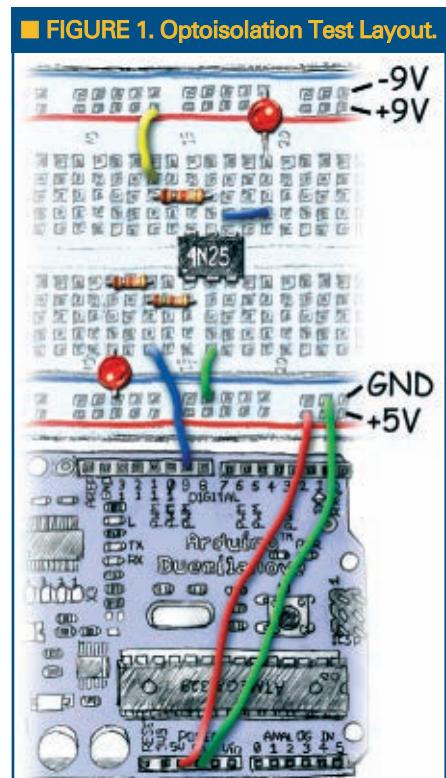



must be done immediately when an external event occurs. It is so common, in fact, that most microcontrollers have built-in interrupt peripheral circuitry to accomplish the task.

This circuitry monitors a pin voltage and when a certain condition happens such as 'was high, now low,' it generates an interrupt that causes the main program flow to halt, store what it was doing in memory, and then the system runs the function that was assigned to the interrupt. When that function finishes, the system state is restored and the main program runs again.

You mainly deal with interrupts in one of two ways. If a simple task is all that is required and the rest of the program doesn't need to know about it, then the interrupt service routine can sneak in, handle it, then sneak back out without the main code ever knowing. If, however, a complex task that takes a lot of time away from the main program (yes, it is all relative) needs to be performed, then the interrupt routine should set a flag (change the value of a variable that both it and the main program can see) so that the main program can check that flag as part of the loop() and deal with the consequences of the interrupt when it gets time.

The Arduino library function attachInterrupt(interrupt, function, mode) simplifies the chore of setting up and using an external interrupt. The 'interrupt' parameter is either 0 or 1 (for the Arduino digital pin 2 and 3, respectively). The 'function' parameter is the name of the function you want to call when the interrupt occurs (the interrupt service routine). The 'mode' parameter is one of four constants to tell the interrupt when it should be triggered:

LOW: Trigger when the pin is low.

CHANGE: Trigger when the pin changes value.


RISING: Trigger when the pin rises from low to high.

FALLING: Trigger when the pin falls from high to low.

Hopefully, you still have your IR detector set up on the breadboard from before (see Workshop 15; Figures 7, 8, and 9). All you need to do in the hardware is move the signal wire from the Arduino Analog pin 0 to the Digital pin 2 as shown in **Figure 2**, then run the Edge_Detect_Interrupt software. In the former setup, we used the ADC to measure an analog voltage, but this time all we will sense is that the voltage is high enough to represent a digital ON or low enough to represent a digital OFF.

Run the Edge_Detect_Interrupt software and waggle your finger in front of the sensor to get a count like shown in **Figure 3**. Next month, we will use this concept to detect the passing of black and white stripes on a motor

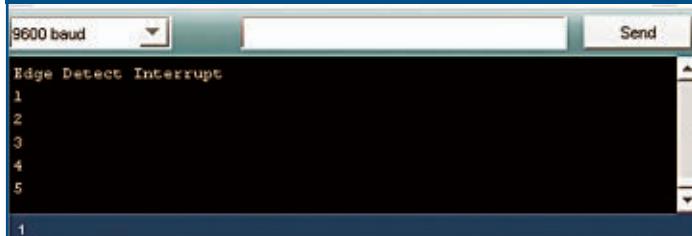■ **FIGURE 3. Edge Detect Interrupt Counter.**



encoder wheel to control the speed of that motor.

Edge Detect Interrupt Software

```
// Edge_Detect_Interrupt
// Joe Pardue 6/28/09

volatile int count = 0;

void setup()
{
  // setup the serial port
  Serial.begin(9600);

  // say hello
  Serial.println("Edge Detect Interrupt");

  // attach interrupt 0 (pin 2) to the
  // edgeDetect function
  // run function on falling edge interrupt
  attachInterrupt(0,edgeDetect, FALLING);
}

void loop()
{
// do nothing
}

// on each interrupt
// increment and show the count
void edgeDetect()
{
  count++;
  Serial.print(count);
  Serial.println();
}
```

Getting Real With Serial Input

The Arduino IDE provides a simple Serial Monitor (PC side serial terminal program) and some serial communications functions that allow you communicate with the Arduino board. These functions do a good job in sending serial text from the Arduino to the PC, but (IMHO) not such a hot job of receiving data from the PC. The Serial.available() function tells you when there is a character available on the serial port, and the Serial.read() function will fetch that character for you. However, the Arduino does not provide (that I know of) any Arduino-like simplified way to deal with those characters once you've got them.

I contrast this weakness of sorts to a real strength of the C programming language: The C Standard Libraries contain a wealth of functions for dealing with data input over a serial port. I want to emphasize that you can use those C libraries with the Arduino IDE, but that kind-of defeats the purpose of Arduino. I touched on this a bit in an earlier article where I differentiated between TAW (The Arduino Way) and ACW (A C Way), so my approach will be to show what you can do with TAW and save the C libraries for later discussion of ACW. I will present an Arduino program that uses logic that mimics one of those C library functions – atoi() (ascii to integer) – that will allow us to input a sequence of numeric characters using the Arduino Serial Monitor and then convert those characters to an integer data value from 0 to 65535. This will be used next month to set the motor speed.

In Workshop 13, we built a Number_Commander that allowed us to pick a tune to play by entering a numeric

character in the Arduino IDE Serial Monitor. While that was cool, it limited us to 10 choices based on input of the characters from 0 to 9. We weren't actually looking at the numbers 0 to 9, but the ASCII character code that represents those numbers. This is an important distinction because the numeric characters are coded with values that are not the same as what we would normally think of as the value of that

character. The character '0' is not coded with a value of 0, but with an ASCII code value of 48. Each subsequent numeric character (1 to 9) is coded as 49 to 57. The ASCII values of 0 to 9 are codes for the communication device (for instance, the ASCII code 7 was used to ring a bell; other low numbered codes were used to do things like advance printer paper or return the print head to the left). There are historic reasons for this coding scheme, but for now just look at an ASCII chart (www.asciitable.com) and accept that when doing serial communications, sending numbers from 0 to 127 actually represents the characters or actions shown in the chart.


The Arduino IDE Serial Monitor allows you to send characters from your PC keyboard, but if you want to send a real number, say 127, then we have to have some way of receiving the characters '1', '2', and '7' and some end-of-number character such as '!' so that the software can know that number sequence has ended. We write a program on the Arduino that stores numeric characters until it sees a '!', then converts those characters to the number they represent. For instance, we could send six characters (42356!) and then convert those characters to an integer with a numeric value of 42,356.

Rather than spend a lot of space with further explanations, we'll just look at the program `ASCII_To_Integer`. Please be aware that this program can be easily spoofed with bad input, but for learning purposes it will suffice.


If you want a real 'computer programming' moment, first think about how you would collect a sequence of numeric characters and convert them to a number. Then, walk through this code with a pencil and piece of paper – especially the `ATOI` algorithm that extracts the number from the character string. The guys that came up with stuff like this were not only clever, they wrote some amazingly efficient code.

```
// ASCII_To_Integer 8/1/09 Joe Pardue
// Duplicates (somewhat) the C Standard Library
// function atoi() algorithm using Arduino.
// Note that there is no filtering of the input
// so if you enter something other than an integer
// value from 0! to 65535!, well, good luck.
```

```
int myInput = 0;
```

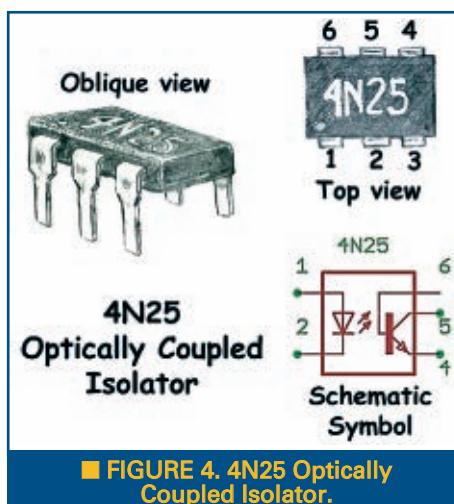

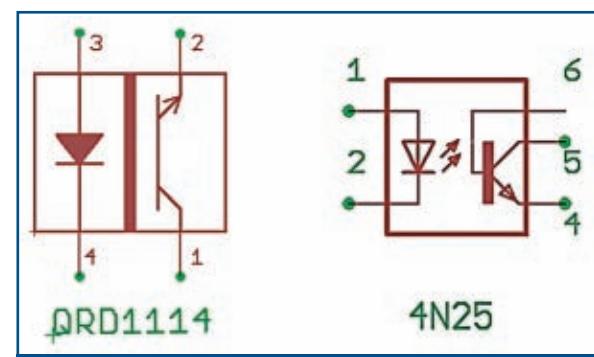■ FIGURE 4. 4N25 Optically Coupled Isolator.



■ FIGURE 5. QRD1114 and 4N25 schematic symbols.

```
int myNum[6];
int myCount = 0;
int i = 0;
int n = 0;

void setup()
{
    Serial.begin(9600);
    Serial.println("ASCII_To_Integer");
}

void loop()
{
    // get characters until receiving '!'
    while( myInput != '!' ) getNum();

    // convert end-of-number character '!' to 0
    myInput = 0;
    myNum[~myCount] = 0;

    // convert ASCII string to integer
    ATOI();


    // clean up and do it all again
    clearAll();
}

// Put serial characters in a character array
void getNum()
{
    if(Serial.available())
    {
        myInput = Serial.read();
        // put the character in the array
        myNum[myCount++] = myInput;
    }
}

void ATOI()
{
    // algorithm from atoi() in C standard library
    n = 0;
    for(i = 0; myNum[i] >= '0' && myNum[i] <= '9'; ++i)
        n = 10 * n + (myNum[i] - '0');

    // show the number
    Serial.print("You sent: ");
    Serial.println((unsigned int)n,DEC);
}

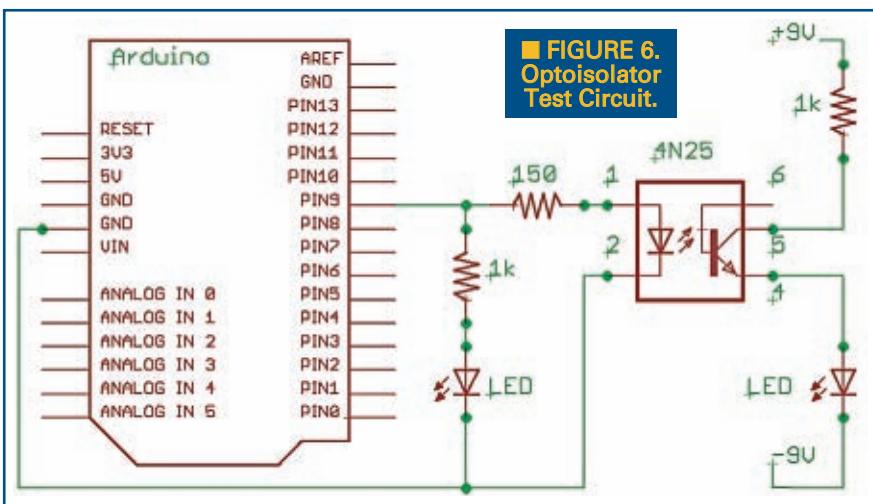void clearAll()
{
    myCount = 0;
    for(i = 0; i < 6; i++)
    {
        myNum[i] = 0;
    }
    Serial.flush();
}
```



■ FIGURE 6.
Optoisolator
Test Circuit.

Optical Isolation of Voltage

Have you ever had an EKG and noticed that those wires patched to your chest on either side of your heart go to a machine that is plugged directly into a wall socket capable of providing mains voltage? You might even have gotten so excited about the prospect of being electrocuted in the doctor's office that you were able to make the EKG go wild with all kinds of crazy beeps.

There are many ways to assure that voltages stay separated. The two main ones are electromagnetic

isolation with transformers and optical isolation with LED/phototransistor pairs. We will look at the latter as a way to connect a signal between a microcontroller at five volts to a motor at nine volts so that we can prevent the digital equivalent of a coronary in our microcontroller.

Figure 4 provides a drawing and schematic symbol for our optical isolator. You can see that the QRD1114 IR Reflective Object Sensor we looked at in Workshop 15 and the 4N25 Optically Coupled Isolator that we are about to look at have similar schematic symbols (see **Figure 5**). Note that the main difference is that the QRD1114 shows a dark bar

between the LED (emitter) and the phototransistor (detector) subcomponents. These parts are nearly identical from an electronic perspective. The primary difference is the packaging.

The QRD1114 detector is shielded from the emitter and can only 'see' the IR if it is reflected back to the device. The 4N25 emitter 'shines' directly onto the detector. The QRD1114 detector will pass a current proportional to the reflected IR, thus the signal level is dependent on the external reflective object, while the 4N25 directly responds to the amount of IR coming from the emitter – it can produce a current through pins 5 and 6 directly proportional to a current through pins 1 and 2. If you did something really dumb like connect a wire from a wall socket to pin 1 on the 4N25, you'd fry the LED. However, none of that voltage would pass through to the device connected to pins 4 or 5. This gives us a way to transfer the information in a signal from one circuit to another using light and without having any electrical connection between those circuits.

In next month's Workshop, we will use this device to isolate a PWM signal at one voltage level, five volts from our Arduino, and scale it to another voltage level (nine volts) for our motor driver.

Optical Isolation Component, Schematic, and Layout

Our hardware demonstration of these concepts uses a five volt signal from the Arduino pin 9 on the emitter side that is converted by the 4N25 to a nine volt signal on the detector side. Wire this up as shown in the schematic in **Figure 6**, and the drawing in **Figure 1**.

Optical Isolation Source Code

To test this with software, use the `ASCII_To_Integer` program shown earlier and add just three lines of code. The first two you should add at the top of the file in the variables list are:

```
int value = 0; // variable to keep the actual
// value
int ledpin = 9; // light connected to digital
// pin 9
```

Add the third line shown below between the ATOI() and clearAll() functions in the loop() function. The full code is in PWM_Test in this month's source code download on the *Nuts & Volts* website.

```
// convert ASCII string to integer
ATOI();
```

```
// control the brightness of an LED
analogWrite(ledpin, n);
```

```
// clean up and do
// it all again
clearAll();
```

The integer received from the PC ('n') is converted to a PWM signal on the Arduino pin 9. The PWM will cause the LED brightness to be proportional to the input value (within limits). We will discuss PWM in more detail next month when we use it to control the speed of a DC motor.

The LED on the left is directly driven by the Arduino pin 9 through a 1K ohm resistor and that pin also drives the IR LED in the 4N25 through a 150 ohm

resistor. The isolated LED is driven by +9 volts through a 1K ohm resistor to pin 5 of the 4N25, through the phototransistor, out pin 4 to the LED.

And that's it for loose ends. Next month, we tie this all together and control the speed of a DC motor. **NV**

Did you know that if you're a paid subscriber to *Nuts & Volts*, you can get the online version for **FREE**?

Go to
www.nutsvolts.com

Give a *Gift*, GET a *Gift*!

Give a one year (12 issues)
 subscription to a friend and receive
 a **FREE** one year subscription for
 another friend or yourself!

Go to
www.nutsvolts.com
 to enter your gift order!

Be sure to use promotion code **Y9WXMS** when ordering.

U.S. Price
 1 Yr – \$26.95



Subscribe online or call:

877-525-2539 (toll free) / 818-487-4545 (outside US)

ELECTRONIX EXPRESS

RSR 3MHZ SWEEP FUNCTION GENERATORS
 6 Waveform Functions, Int/Ext Counter, lin/log sweep
MODEL FG-30 MODEL FG-32
 (No Digital Display) (5 Digit Display)
 \$135⁰⁰ \$195⁰⁰

BENCH DMM WITH RS232 INTERFACE
MODEL DM9803R
 True RMS, digital and bar graph display, AC/DC Cap, Res, frequency functions. Includes software, AC or DC operation.
 \$139⁹⁵

SWITCHES

8 POS DIP (V17DIP8SS)	.90
Toggle Mini SPDT (17TOGSD-M)	1.40
Toggle Mini DPDT (17TOGDD-M)	\$1.55

INSTEK OSCILLOSCOPE
MODEL GOS-620
 Dual Channel – 20MHz (INCLUDES PROBES)

\$305⁰⁰

DC POWER SUPPLIES

MODEL HY3003 – DIGITAL DISPLAY	\$95 ⁰⁰
MODEL HY3003-3 – TRIPLE OUTPUT	\$184 ⁰⁰
Two 0-30 VDC, 0-3 Amp variable outputs plus 5V 3A fixed. Digital Display.	

DIGITAL MULTIMETER
 32 Ranges – 3 1/2 Digit
MODEL MY-64 \$33⁹⁵
 AC/DC Volt/Current, Res. Cap., Frequency. Rubber Holster Included

POTENTIOMETERS

Cermet (STS Series)	85¢	75¢	65¢
Multiturn (MTT Series)	85¢	75¢	55¢
Panel Mount (PMA Series)	\$1.15	80¢	70¢
Standard Values Available			

Weller® SOLDERING STATION

#1 BEST SELLING	\$46 ⁵⁰
STATION	
MODEL WLC 100	
0603WLC100	

ALLIGATOR LEADS

SET OF 10	\$3 ⁵⁰
SOUND SENSOR CAR	
REQUIRES SOLDERING	
Reverses direction whenever it detects noise, or touches an obstacle.	
\$995	
#3221881	

HSR 3-WIRE IRON

#060509	\$6 ⁵⁰
DIGITAL MULTIMETER	\$6 ⁵⁰
10+	
SUPER ECONOMY MODEL 820B	\$7.50
1-9	
#01DM820B	

Visit Our Website At
<http://www.elexp.com>

ROTARY TOOL KIT \$35⁹⁵
 Variable speed tool (37,000 RPM) with accessory kit in a hard plastic carry case.
 #29DR101

MORE Low-Priced Items In Our FREE 350+ Page Catalog

TERMS: Min. \$20 + shipping. School Purchase Orders, VISA / MC, Money Order, Prepaid. NO PERSONAL CHECKS, NO COD. NJ Residents: Add 7% Sales Tax.

In NJ: 732-381-8020
 FAX: 732-381-1006


365 Blair Road • Avenel, NJ 07001
 800-972-2225

<http://www.elexp.com>
 email: electron@elexp.com

We have over 170 related titles in our webstore!!

The Nuts & Volts **WEBSTORE**

CD-ROMS SPECIALS

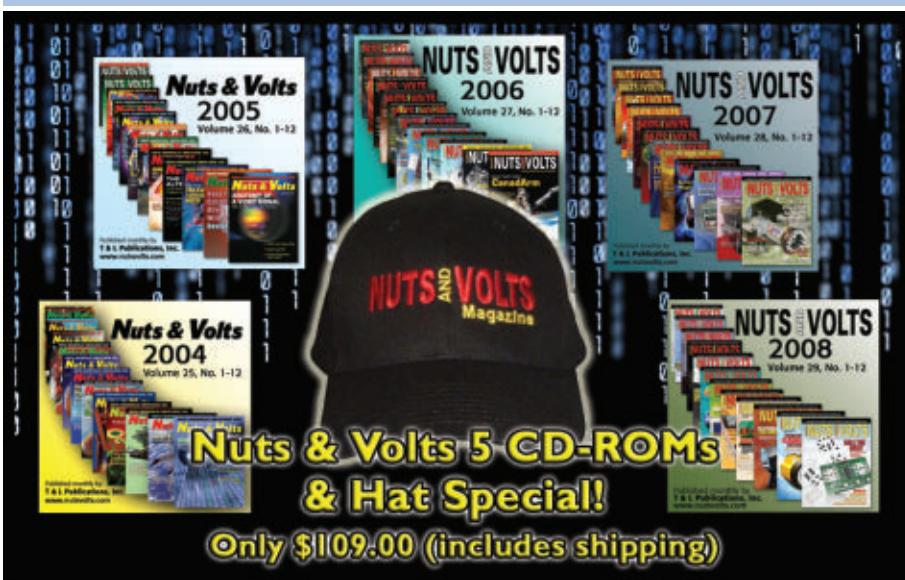


Nuts & Volts 5 CD-ROMS & Hat Special!

Only \$109.00 (includes shipping)

The Amateur Scientist 3.0 The Complete Collection

by Bright Science, LLC

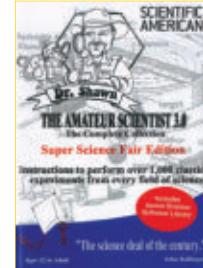There are 1,000 projects on this **CD**, not to mention the additional technical info and bonus features. It doesn't matter if you're a complete novice looking to do your first science fair project or a super tech-head gadget freak; there are enough projects on the single CD-ROM to keep you and 50 of your friends busy for a lifetime!



Reg \$26.99
Sale Price \$23.95

ELECTRONICS

Beginner's Guide to Embedded C Programming Volume 2 by Chuck Hellebuyck


In this "Volume 2," Chuck takes the reader to the next level by introducing how to drive displays, how to use interrupts, how to use serial communication, and how to use the internal hardware peripherals of the PIC16F690 microcontroller such as SPI, PWM, and timers.

When you have finished reading this book and completed the projects, you'll be well beyond the title of Beginner!

\$39.95

The components that are added to the PICKit 2 that Chuck uses in his new book can also be purchased through the Nuts & Volts Webstore.

\$12.95

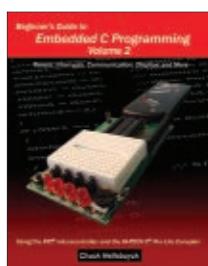


Build Your Own Electronics Workshop

by Thomas Petruzzellis

YOUR DREAM ELECTRONICS LAB IS WAITING INSIDE!

This value-packed resource provides everything needed to put together a fully functioning home electronics workshop! From finding space to stocking it with components to putting the shop into action — building, testing, and troubleshooting systems — popular electronics author Tom Petruzzellis' *Build Your Own Electronics Workshop* has it all! And the best part is, this book will save you money, big time!


Reg \$29.95 Sale Price \$24.95

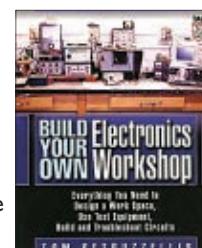

Encyclopedia of Electronic Circuits, Volume 7

by Rudolf F. Graf / William Sheets
NEW IN THE BESTSELLING SERIES!
ONE THOUSAND MORE LEADING-EDGE CIRCUIT DESIGNS!

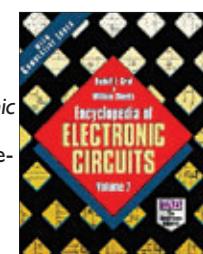Designed for quick reference and on-the-job use, the *Encyclopedia of Electronic Circuits, Volume 7*, puts over 1,000 state-of-the-art electronic and integrated circuit designs at your fingertips. Organized alphabetically by circuit type, this all-new collection includes the latest designs from industry giants such as Advanced Micro Devices, Motorola, Teledyne, General Electric, and others.



\$39.95

Running Small Motors with PIC Microcontrollers

by Harprit Singh Sandhu

The only comprehensive guide to using PIC microcontrollers to drive small motors.

Running Small Motors with PIC Microcontrollers contains more than 2,000 lines of PICBASICPro code and dozens of circuit diagrams with the focus on controlling motors. Hands-on tutorials, program listings, and resources are included.




Op Amps for Everyone, Third Edition

by Bruce Carter and Ron Mancini

OP AMPS FOR EVERYONE provides the theoretical tools and practical know-how to get the most from these versatile devices - this new edition substantially updates coverage for low-speed and high-speed applications, and provides step by step walkthroughs for design and selection of op amps and circuits.


\$79.95*

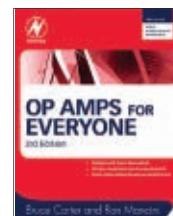

Haywired

by Mike Rigsby


Construct a no-battery electric car toy that uses a super capacitor, or a flashlight that can be charged in minutes, then shines for 24 hours. Written for budding electronics hobbyists, author Mike Rigsby offers helpful hints on soldering, wire wrapping, and multimeter use. Each project is described in step-by-step detail with photographs and circuit diagrams. Includes websites listing suppliers and part numbers.

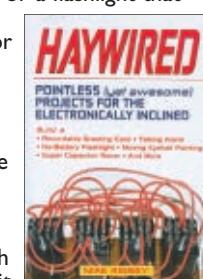

\$16.95

Order online @ www.nutsvolts.com
Or CALL 1-800-783-4624 today!

BOOK & KIT COMBOS

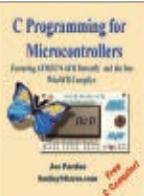


From the
Smiley Workshop
**C Programming for
Microcontrollers**
by Joe Pardue


Book \$44.95

Do you want a low cost way to learn C programming for microcontrollers? This 300 page book and software CD show you how to use ATMEL's AVR Butterfly board and the FREE WinAVR C compiler to make a very inexpensive system for using C to develop microcontroller projects.

Combo Price \$99.95 Plus S/H

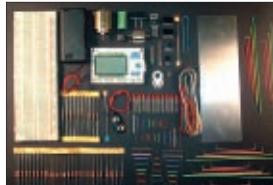

Kit \$66.95

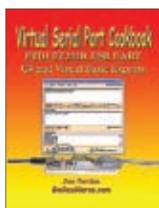

Virtual Serial Port Cookbook
by Joe Pardue

As talked about in the
Nuts & Volts June issue,
"Long Live The Serial Port"

Book \$44.95



Kit \$69.95

This is a cookbook for communicating between a PC and a microcontroller using the FTDI FT232R USB UART IC. The book has lots of software and hardware examples. The code is in C# and Visual Basic Express allowing you to build graphical user interfaces and add serial port functions to create communications programs.


The Virtual Serial Port Parts Kit and CD

(also available, above right)

Reg. Price \$ 114.90


Subscriber Price \$109.95 Plus S/H

Getting Started Combo

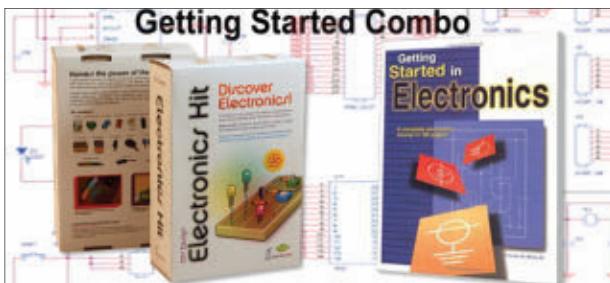

The Getting Started Combo includes: Getting Started in Electronics by author Forrest Mims and the DIY Electronics Kit. In his book, Mims teaches you the basics and takes you on a tour of analog and digital components. He explains how they work and shows you how they can be combined for various applications. The DIY Electronics Kit allows for the hands-on experience of putting circuits together — the kit has over 130 parts! No soldering is required and it includes its own 32 page illustrated manual. **Combo Price \$62.95 Plus S/H**

CD-ROMS

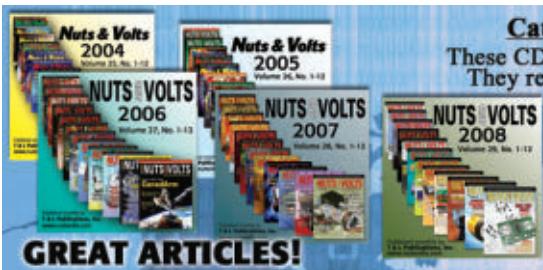

GREAT ARTICLES!

Catch up on 2003-2008 back issues
These CD-Roms are PC and MAC compatible.
They require Adobe Acrobat Reader Ver.6.

Acrobat Reader Ver. 7 included on disc.

\$24.95

More offers go to:
www.nutsvolts.com



GREAT PROJECTS!

THE EVIL GENIUS SERIES



**If you like projects,
The Evil Genius Series
is for you!**

We have all 26 in stock
and ready to ship.

Look for special offers.
<http://store.nutsvolts.com>

CALL 1-800-783-4624 today!

Or Order online @ www.nutsvolts.com

PROJECTS

Christmas Tree Kit



The microprocessor controlled Xmas Tree comes with eight preprogrammed light display sequences. All you need is a soldering iron, a couple of batteries, and you'll be ready to show off your electronic tree!

To see a demo video please visit www.nutsvolts.com

Subscriber's Price \$38.95

Non-Subscriber's Price \$41.95

"Double Wide" Sun Tracker Kit



The Double Wide Sun Tracker is one of the great projects from the new series of articles by John Gavlik, *Experimenting with Alternative Energy*, In Parts 4 and 5, he teaches you how to get the most out of your PVs within the full day of sunlight. For kit details, please view our webstore.

Subscriber's Price \$94.95

Non-Subscriber's Price \$99.95

A Nuts & Volts exclusive kit.

Arch-Ball Clock PCB & MCU



This unique clock allows the hobbyist to be involved with a little wood working, as well as the electronics side of the project.

We just supply you with the custom shaped printed circuit board and the programmed MCU. You'll have to go digging in your workshop for the other components and wood.

Subscriber's Price \$25.75

Non-Subscriber's Price \$28.25

Arch templates can be downloaded from the [Nuts & Volts](http://www.nutsvolts.com) website.

NixieNeon Clock Kit



Using Neon and Nixie bulbs, this clock displays the precision movement of time and is programmable to display "Time Chaos" at different intervals. The NixieNeon Clock then resets itself to the correct time in an eye-catching ballet of luminosity.

The PCB is 7.25"x 7.25" and consists of over 400 components.

Subscriber's Price \$186.00

Non-Subscriber's Price \$195.95

PCBs can be bought separately.

Transistor Clock Kit



If you like electronic puzzles, then this kit is for you! There are no integrated circuits; all functionality is achieved using discrete transistor-diode logic. The PCB is 10"x11" and harbors more than 1,250 components!


For more info, see page 42, this issue.

Reg \$225.95

Sale Price \$199.95

PCBs can be bought separately.

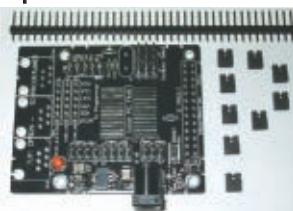8 Bit PIC® Microcontroller Development SchmartModule A



This PIC Microcontroller Development board supports 116 different 8 bit SOIC PIC Microcontrollers. This board is fully populated except for the PIC. You hand-solder the PIC using the "EZ" technology from Schmart Board, configure the jumpers for your PIC part number, and start programming.

For more on "EZ" technology, please see this product in our webstore. **\$14.95**

Nixie Tube Clock Kit



Cherry Wood Clock Case

Nixie tube clocks fuse the spirit, drama, and eerie beauty of cold war technology with modern inner works to create uncommon handcrafted timepieces.

Now with optional case choices!

Get more info @

www.nutsvolts.com

Subscriber's Price \$146.95

Non-Subscriber's Price \$159.95

Kit includes article reprint, complete instructions and parts list.

Das BlinkenBoard Kit

This kit includes a preprogrammed ATtiny84 microcontroller that sports eight software PWM channels to control motor speed and light brightness. Jumper selectable patterns can be used to operate motors, solenoid valves, relays. Expand your board with GNU/GPL software updates to be featured in upcoming NV articles.



Subscriber's Price \$32.45

Non-Subscriber's Price \$35.95

PCBs can be bought separately.

Retro Game Kit



Build your own
"BLAST from the Past!"

This is sure to be a hit for all ages! Easy to build in an evening and will give you many more fun filled evenings mastering the Retro Rover or Retris games.

Games come preprogrammed on individual MCUs

Reg \$44.95 Sale Price \$29.95

Limited Time Offer


Attention Subscribers ask about your discount on prices marked with an *

The Nuts & Volts **WEBSTORE**

ALTERNATIVE ENERGY SECTION

The Complete Idiot's Guide to Solar Power for Your Home by Dan Ramsey / David Hughes

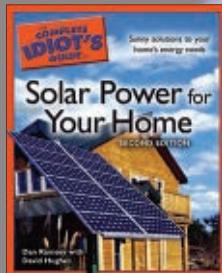The perfect source for solar power — fully illustrated. This book helps readers understand the basics of solar power and other renewable energy sources, explore whether solar power makes sense for them, what their options are, and what's involved with installing various on- and off-grid systems. **\$19.95**



Do you know how many watts (YOUR MONEY) are going down the drain from "THE PHANTOM DRAW?"


If you are interested in your own power usage we at *Nuts & Volts Magazine* believe that this is the best way to help you determine your electrical energy use in ON and OFF home appliances. To order call 1 800 783-4624 or online www.nutsvolts.com \$29.95 plus S&H



Renewable Energies for Your Home by Russel Gehrke

Simple and Inexpensive Renewable Energy Solutions for Your Home.

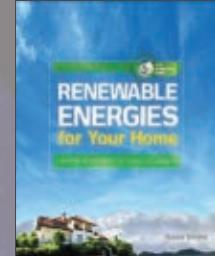
It's not always easy being green, and sometimes it costs more than you'd expect to get an eco-friendly home improvement project up and running. *Renewable Energies for Your Home* gives you sustainable home energy solutions that won't drain your wallet or the power grid. Filled with step-by-step instructions and helpful photos and illustrations. **\$24.95**



Build Your Own Plug-In Hybrid Electric Vehicle by Seth Leitman


A Step-by-Step Guide to Building a Plug-In Hybrid Electric Vehicle from the ground up

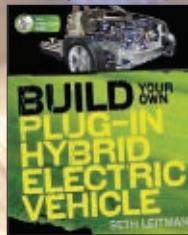Build Your Own Plug-In Hybrid Electric Vehicle puts you in the driver's seat when it comes to hitting the road in a reliable, economical, and environmentally friendly ride. Inside, you'll find complete details on the hybrid powertrain and all the required components, including the motor, battery, and chassis. **\$24.95**



REEL Power Renewable Energy Education Lab

LEARNONLINE.COM

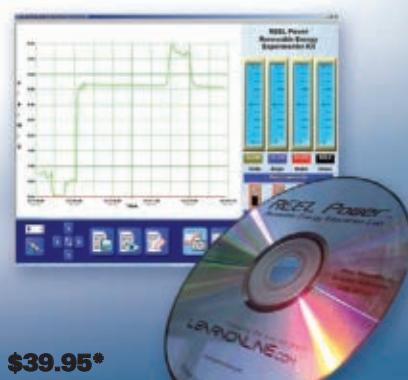


\$39.95*

Build Your Own Electric Motorcycle by Carl Vogel

A practical guide for building an electric motorcycle from the ground up.

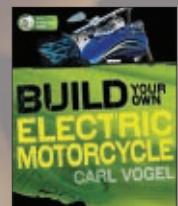Complete with hundreds of step-by-step pictures, charts, and graphs for the latest and most efficient technologies, this new TAB Green Guru Guide shows you how to build an electric motorcycle from scratch. Written by an electric vehicle expert, *Build Your Own Electric Motorcycle* provides current data on all required materials, components, and specifications. **\$24.95**



Making PIC Microcontroller Instruments and Controllers by Harprit Sandhu

Harness the power of the PIC microcontroller unit with practical, common-sense instruction from an engineering expert. Through eight real-world projects, clear illustrations, and detailed schematics, *Making PIC Microcontroller Instruments and Controllers* shows you step-by-step how to design and build versatile PIC-based devices. **Reg \$49.95**
Sale Price \$42.95



SPECIAL OFFER

Enter into the world of PICs & Programming with this great combo!

Combo Price
\$155.00

For complete details visit our webstore @ www.nutsvolts.com

CLASSIFIEDS

SURPLUS

SURPLUS ELECTRONIC PARTS & ACCESSORIES

Over 13,000 Items in Stock.	Cables	Hardware	Relays	Switches
Connectors	LEDs	Semiconductors	Test Equipment	
Displays	Motors	Service Manuals	Tools	
Fans	Potentiometers	Speakers	VCR Parts	

Surplus Material Components
SMC ELECTRONICS
www.smcelectronics.com

No Minimum Order.
Credit Cards and PAYPAL Accepted.
Flat \$4.95 per order USA Shipping.

COMPONENTS

 **RF PARTS™ CO.**
Tubes, Transistors, Power Components
Email: rfp@rfparts.com • Web: www.rfparts.com
800-737-2787 Fax 888-744-1943

Nixie Power



2-16V In, 4-8W / 150-200VDC Out
0.95" x 0.95" x 0.35"
\$9.95 (Shipping included)

www.tayloredge.com/nixie

SCSI

I-U320 50Pin-68Pin-80Pin
1 to 8 Bay Case Enclosures
Adapters Cables Terminators
Low Prices - Qty Discounts!
(Also FireWire, USB, Video)
www.mcpb.com

Brilldea

pioneer of prototyping goods
+RGB LED Ribbon
+RGB LED Pixels
+LED Painter
+Parallax Propeller
www.brilldea.com

 **LEDs**
Super Brights from 20¢
RGB Color Mixing 30 Pack \$6.99
Assortment 120 Pack \$24.99
Shipping from \$3.00
Alan-Parekh.com/Store

www.servomagazine.com

KITS/PLANS

High Quality
Electronic Kits & Modules
\$29.95
KIT

CK1122
Dual Bidirectional
H-Bridge Motor Controller

FM Transmitters
Timers
Audio Amplifiers
Motor Controllers
PIC Programmers

Custom Designs
www.canakit.com

50 MHz auto ranging frequency
Counter. Pic microprocessor.
Viewing from 1Hz-50MHz
Complete kit
\$49.95 + \$5.95 S&H
Order:  www.Invent-Electronics.com
Or: 304-203-5957

Electronic Kits

- Fun and Educational
- Discount White and Blue LEDs
- Quantity Discounts


www.bakatronics.com

SOLAR PRODUCTS/KITS

BATTERY DESULFATORS

www.wizbangplus.com

LCDs/DISPLAYS

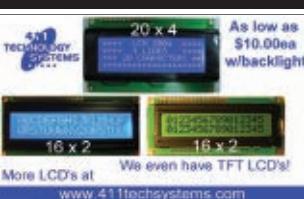

BOOKS

Books

PIC® Microcontroller
sq-1.com

Stepper Motors
stepperstuff.com

CNC
cncintro.com

SQUARE 1
ELECTRONICS
(208) 664-4115
Hayden, ID USA

MICROCONTROLLERS

The incredible expandIO-USB... controls circuits totally over USB!

- No drivers needed
- Windows/Mac/Linux
- No MCU coding!

Mouser / Farnell / DigiKey



DigitalShortcut.com "Web servers for everybody"

Xilinx Spartan3AN + W5300 or LPC2148 +W5300

- easily add 100 Mbit/s Ethernet to almost anything
- solid, easy to comprehend hardwired TCP/IP stack from WIZnet, 128kB of network buffers
- free tools, fast demo http server included



Development platforms **\$87/ea**

VIDEO AGC/SYNC PROCESSING PROJECT

AVR RISC Microcontroller-Based
Instruction Manual CD's
Printed Circuit Boards
Pre-programmed Microcontrollers
Free Patent Application Information
www.jlkelectronics.com

QKITS.COM



1-888-GO 4 KITS

MicroStamp11

World's Smallest 68HC11 Microcontroller Module!



- tiny, light-weight module
- choice of 8K or 32K EEPROM
- SCI, SPI, pulse accumulator
- generate pulses, PWM, etc.
- measure time, frequency, etc.
- 14 digital I/O lines + interrupts
- use Assembler, BASIC, or C
- lots of code examples/tutorials
- easy Windows code-loading
- Starter Packages from \$49

www.MicroStamp11.com

www.nutsvolts.com

CLASSIFIEDS

THE OWNERSHIP, MANAGEMENT, AND CIRCULATION STATEMENT OF NUTS & VOLTS MAGAZINE, Publication Number: 1528-9885 is published monthly. Subscription price is \$26.95. 7. The complete mailing address of known office of Publication is T&L Publications, Inc., 430 Princeland Ct., Corona, Riverside County, CA 92879-1300. Contact Person: Tracy Kerley. Telephone: (951) 371-8497. 8. Complete Mailing address of Headquarters or General Business Office of Publisher is T&L Publications, Inc., 430 Princeland Ct, Corona, CA 92879. 9. The names and addresses of the Publisher, and Associate Publisher are: Publisher, Larry Lemieux, 430 Princeland Ct., Corona, CA, 92879; Associate Publisher, Robin Lemieux, 430 Princeland Ct., Corona, CA 92879. 10. The names and addresses of stockholders holding one percent or more of the total amount of stock are: Jack Lemieux, 430 Princeland Ct., Corona, CA 92879; Larry Lemieux, 430 Princeland Ct., Corona, CA 92879; Audrey Lemieux, 430 Princeland Ct., Corona, CA 92879. 11. Known Bondholders, Mortgagees, and other security holders: None. 12. Tax Status: Has not changed during preceding 12 months. 13. Publication Title: Nuts and Volts 14. Issue Date for Circulation Data: October 2008-September 2009. 15. The average number of copies of each issue during the proceeding twelve months is: A) Total number of copies printed (net press run): 48,512 B) Paid/Requested Circulation (1) Mailed Outside County subscriptions: 34,638 (2) Mailed In-County subscriptions: 0 (3) Paid Distribution Outside the Mail including Sales through dealers and carriers, street vendor, and counter sales and other paid distribution outside USPS: 6,361 (4) Paid Distribution by other classes of mail through the USPS: 0; C) Total Paid Distribution: 40,999; D) Free or Nominal Rate Distribution by mail and outside the mail (1) Free or Nominal Rate Outside-County Copies: 0 (2) Free or Nominal Rate In-County Copies: 0 (3) Free or Nominal Rate Copies Mailed at other classes through the USPS: 0 (4) Free or Nominal Rate Distribution Outside the mail: 358; E) Total Free or Nominal Rate Distribution: 358; F) Total Distribution: 41,357; G) Copies not distributed: 7,155; H) Total: 48,512; Percent paid circulation: 99.13%. Actual number of copies of the single issue published nearest the filing date is September 2009; A) Total number of copies printed (net press run): 44,297; B) Paid/Requested Circulation (1) Mailed Outside County subscriptions: 32,204 (2) Mailed In-County subscriptions: 0 (3) Paid Distribution Outside the Mail including Sales through dealers and carriers, street vendor, and counter sales and other paid distribution outside USPS: 6,007 (4) Paid Distribution by other classes of mail through the USPS: 0; C) Total Paid Distribution: 38,211; D) Free or Nominal Rate Distribution by mail and outside the mail (1) Free or Nominal Rate Outside-County Copies: 0 (2) Free or Nominal Rate In-County Copies: 0 (3) Free or Nominal Rate Copies Mailed at other classes through the USPS: 0 (4) Free or Nominal Rate Distribution Outside the mail: 0; E) Total Free or Nominal Rate Distribution: 0; F) Total Distribution: 38,211; G) Copies not distributed: 6,086; H) Total: 44,297; Percent paid circulation: 100.0%. I certify that these statements are correct and complete. Larry Lemieux, Publisher - 9/29/09.

Did you know that if you're a paid subscriber to Nuts & Volts, you can get the online version for **FREE**? Go to www.nutsvolts.com.

HARDWARE WANTED

DEC EQUIPMENT WANTED!!!

Digital Equipment Corp. and compatibles. Buy - Sell - Trade

CALL KEYWAYS 937-847-2300 or email buyer@keyways.com

WANTED
used - surplus - obsolete
radios, tvs, capacitors, inductors
transistors, RF parts, meters, dials
heatsinks, switches, transformers
antennas, test equipment, crystals
tubes, connectors, motors, manuals
www.SecondHandRadio.com

PROFESSIONAL SERVICES

RICHARD N. KRAJEWSKI

Editor

201-659-0041
richardkrajewski.com

MISCELLANEOUS FOR SALE

WANT TO BUY ...

Electronic distributing or manufacturing company

Anything considered. Inventory, equipment, fixtures, entire company. Call ISE at no cost or obligation.

PH: 956-444-0004 (toll free) 888-351-5550
tommy@iseliquidator.com www.iseliquidator.com

DESIGN/ENG SERVICES

* Circuit board layouts * Prototype assemblies

WWW.OSPREYELECTRONICS.COM

Convert your sketch or print into a quality pcb for a reasonable price. Visit us on the web or call Osprey Electronics at (208) 664 1089 (USA)

FLEXREV China Direct Manufacturing

Turn Key or Subassemblies
Components, Enclosures, Keypads

\$0.007 per soldering point
2 layer PCBs \$0.14/in²
Small jobs welcome

FLEXREV.COM

GADGETS

GREEN LASER POINTER

.93 mile range
\$22.89 Free Shipping
www.gadgetcentral.ca

ROBOTICS

\$29.95 MaxSonar-EZ1 (MSRP)

High Performance Ultrasonic Range Finder
- serial, analog voltage & pulse width outputs
- lowest power - 2mA
- narrow beam
- very easy to use!
www.maxbotix.com

PCB SOFTWARE

EXCLUSIVE U.S. DISTRIBUTOR



YOUR COMPLETE SOLUTION!

- PCB Design
- PCB Simulation
- CAD/CAM Menu

121747, Hobby Vers., \$175
121743, Pro. Version, \$275

www.KELVIN.com

AUDIO/VIDEO



www.4ATV.com

Miniature 2.4GHz Wireless T/R
\$199/kit
- Quarter size transmitter
- 300 ft standard transmit radius
- 4 channel manually selectable
- Power supplies included
More Wireless stuff available
Call: (847) 202-0010



www.4ATV.com

2.4GHz 1 Watt Signal Booster
\$129/kit
- 10-40 mW Input
- 1 W Output
- SMA connector
- Power Supply included
BT-100
Call: (847) 202-0010

**Give a Gift,
GET a Gift!**

Give a one year (12 issues) subscription to a friend and receive a **FREE** one year subscription for another friend or yourself!

Go to
www.nutsvolts.com
to enter your gift order!

Be sure to use promotion code **Y9WXMS** when ordering.


U.S. Price
1 Yr - \$26.95



Subscribe online or call:

877-525-2539 (toll free) / 818-487-4545 (outside US)

TECH FORUM

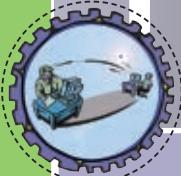

This is a READER-TO-READER Column.

All questions **AND** answers are submitted by *Nuts & Volts* readers and are intended to promote the exchange of ideas and provide assistance for solving problems of a technical nature. Questions are subject to editing and will be published on a space available basis if deemed suitable by the publisher. Answers are submitted by readers and **NO GUARANTEES WHATSOEVER** are made by the publisher. The implementation of any answer printed in this column may require varying degrees of technical experience and should only be attempted by qualified individuals. Always use common sense and good judgement!

All questions and answers should be sent by email to forum@nutsvolts.com All diagrams should be computer generated and sent with your submission as an attachment.

QUESTIONS

To be considered, all questions should relate to one or more of the following:

- ① Circuit Design
- ② Electronic Theory
- ③ Problem Solving
- ④ Other Similar Topics
- Be brief but include all pertinent information. If no one knows what you're asking, you won't get any response (and we probably won't print it either).
- Include your Name, Address, Phone Number, and email. Only your Name, City, and State will be published with the question, but we may need to contact you.
- No questions will be accepted that offer equipment for sale or equipment wanted to buy.
- Selected questions will be printed one time on a space available basis.
- Questions are subject to editing.

ANSWERS

- Include in the subject line of your email, the question number that appears directly below the question you are responding to.
- Payment of \$25.00 will be sent if your answer is printed. Be sure to include your mailing address or we cannot send payment.
- Only your Name, City, and State, will be printed, unless you say otherwise. If you want your email address included, indicate to that effect.
- Comments regarding answers printed in this column may be printed in the Reader Feedback section if space allows.

>>> QUESTIONS

Power Supply

I am designing a project where weight is at a premium. I need some help designing a transformerless power supply that can deliver 12-14 volts at three amps. It needs to be auto switching 110/220 VAC. I designed a few projects in the past but they always had a transformer. I see things like laptop power supplies that don't have transformers. They put out three or four amps. How do they do it?

#11091

Patrick Ogden, UT

FM Receiver

I'm looking for an FM circuit with these features:

Fixed digital 95.5 MHz
Mono
Earbud output
Battery powered
Small as possible

#11092

Don Bartelson Merritt Island, FL

Bridge Rectifier Voltage Readings

Why, when I read the open circuit DC voltage with both sides of the output disconnected from the rectifier, I read the input voltage $\pm 10\%$? However, if I reconnect the load — a 90 VDC brake — and have the output switching device open, the measured DC output voltage at the rectifier is

approximately 30% greater than the disconnected output voltage.

#11093

**John Coonis
Los Angeles, CA**

Vehicle ECU Programming

I would like to know what kind of programming is used in a car ECU. Is it C, C++, Visual Basic, or something else?

#11094

**Mohahamad
Kuwait**

DC-to-DC Step-Up Transformer

I need to locate a DC-to-DC step-up transformer that goes from 120 to around 330 volts. It is for a DC-to-DC converter that will drive a laser diode and can be low wattage.

#11095

**Thomas Wagner
Coldwater, MI**

Wireless HVAC Fan Controller

I want to install a duct fan in my HVAC system to help regulate the temperature of a specific room. But the duct where the fan will go is in the attic and the main airhandler is in the basement. The fan runs on 120 VAC and pulls 2A. I need an affordable wireless system that would turn the duct fan on and off when the main airhandler turns on and off.

#11096

**Eric Peters
Martinsburg, WV**

Power Outage Monitor

From time to time, I experience

power outages when I am not at home. I would like to either build or purchase a device which connects to the AC power line and begins timing when the AC power drops and stops timing when the AC power is restored. The readout must indicate the time elapsed during the outage.

#11097 **Corby Grubb**
Alpha Audio Associates

Labeling Items

Can someone recommend the best way to put professional-looking text labels on a project enclosure, at a hobbyist price point? I've been using Brother P-Touch labels; while cheap, they don't have the visual impact that I'd like to have and don't work well in constrained spaces.

#11098 **W. Walker**
Swansea, IL

Performance of Battery and Super Capacitor

I'm working on an electric go-kart and need help predicting the performance of a combined battery and super capacitor. I need a formula that would show the current output of a small battery and a large capacitor. I'd want two battery types (lead acid, LiFePo4, etc.), so the formula needs to have variables for different battery characteristics. The new supercaps are in the range of 35-100 Farads.

There is one manufacturer that makes a 50 AH lead acid combined in parallel with a large (maybe) 35 Farad capacitor.

Ultimately, I want to know what will happen if I put this in my kart and accelerate for six or even 10 seconds.

#11099 **Cary Z**
Indianapolis, IN

>>> ANSWERS

[#6095 - June 2009] Triac Controlled Light Switch

I'm looking for a circuit to run a low wattage 120 volt incandescent light. The source will be a Parallax BASIC Stamp II microcontroller (5V @ 30 mA per I/O) and the circuit needs to be opto isolated. I'd like to use a triac if possible. The light will be off for

short periods of time (two to five seconds) and on for about a minute at a time.

#1 *Nuts & Volts* advertiser All Electronics (www.allelectronics.com) has two suitable solid-state relays (SSR) for less than \$5: SRLY-19 and SRLY-31. These parts have a 5 VDC compatible input, and an optically isolated triac output for switching the AC load.

The SRLY-19 input is 3-8 VDC and the output 24-140 VAC @ 1A. Wire the pins as follows: pin 4(-) to Stamp gnd; pin 3(+) to Stamp output; pin 2 (~) to AC; and pin 1(~) to lamp. The other side of the lamp goes to the other AC line. See the online catalog for a picture of the SSR. The SRLY-31 input is 4-10 VDC and the output 24-280 VAC @ 1.5A. Wire the pins as follows: (-) to Stamp gnd; (+) to Stamp output; (~) to AC; and (~) to lamp.

For controlling a heavier load, consider the three amp SRLY-20.

Dennis Crunkilton
Abilene, TX

#2 Figure 1 is a fairly straightforward solution taken right from the MOC3010 datasheet. The MOC3010 will keep your microcontroller optically isolated from mains. R1 will limit the current through the MOC3010 input diode and what your microcontroller sinks to approximately 13 mA. R2 limits the current through the output triac of the MOC3010 per the datasheet. The T801-600G is an eight amp triac capable of about a 900 watt load provided it is heatsunk properly. Exercise caution when working with

mains voltages and consider installing a fuse between the AC line and your incandescent lamp for safety. Both parts can be found at Mouser where you can also get the datasheets; www.mouser.com.

Mike Bernath
Denver, NC

[#6096 - June 2009] 24 Hour Counter

I need to build a 24 hour, battery-operated counter with a 2" readout that will have the capability to be manually adjusted up/down and reset to 0.

I have a small kitchen timer that will do what you ask. It can be set up to 99 hours, 59 minutes, and 59 seconds. It will count up and down, has four timer settings for program timing, a clock, and alarm. The manufacturer is Component Design Northwest, Inc., in Portland, OR. You can search for the above on the Internet. Click for Retailer, then click Timers. Click for Digital Hour/Minute /Second. Click for model PT1A.


I have had it for about 10 years, and other than changing the LR44 battery about every three years, it has not failed me yet.

John Lippert
Menomonee Falls, WI

[#7091 - July 2009] Wind Speed Controller

I need a circuit for several applications that need to be switched on/off (open/closed) by relay, depending on wind speed.

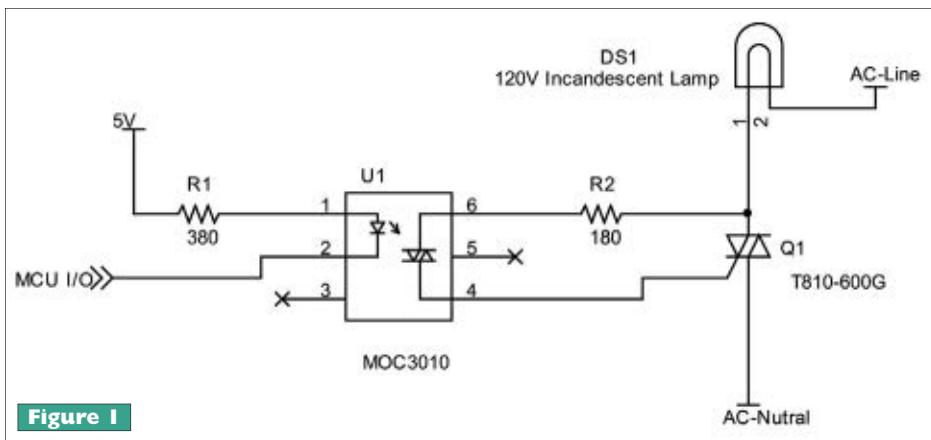The circuit needs to be able to set a minimum wind speed to activate and



a maximum wind speed to deactivate. Also, it needs variable activate and deactivate timers (about 30 seconds to five minutes) so that wind gusts will not activate/deactivate the circuit too rapidly.

There are several stand-alone wind speed devices on the market, as well as included in complete weather stations. They all seem to be wireless in nature and talk to some type of receiver monitor or computer. A stand-alone "wired" wind speed device to controller circuit would be preferred.

#1 A stand-alone wired wind speed alarm can be found at inspeed.com under "windswitch." You can add an external time delay relay like Ramsey Electronics #K2579 (www.ramseykits.com) if the built-in delay is not enough.

Bob Lindstrom
Broomfield, CO

#2 The easiest way to solve this is probably with a hot-wire anemometer. A mass flow sensor in a modern vehicle uses the same principle. Linear Technology (www.linear.com) has an application circuit for the LT1014 using a #328 bulb with the glass envelope removed as a wind speed sensor. A couple of comparators connected to this circuit should give you the desired result (look for window comparator circuits and timer circuits in the LM339 datasheet). You can use Linear Technologies LTspice IV to model the circuit.

Walter Heissenberger
Hancock, NH

[#7092 - July 2009] **Inventory Tracking**

We have been trying to find a better way to keep track of thousands of inventory items we have on campus. We would like to do this the cheapest and most effective way. Our budget right now is not that large. We have looked at a few applications from iTunes App store, but most of them are web based – "Info already on the web." I was wondering if RFID chips could do this sort of thing? We want to put the serial number, item name, and model number into either a barcode or

chip that can be stuck to the item. Is the RFID system able to do this or very inexpensive barcode software?

#1 RFID is practical and cost-effective. For the campus inventory system, tags – which are about the size of a postage stamp and about as thick (there's a little bump where the chip is located) – are available that could store a few bytes up to 3,000 bytes for less than \$1 each.

These tags can be written, read, and re-written over the life of the asset. The tags are "passive" meaning that they have no internal power supply. Portable reader/writers are available. Tag data can be security protected. I am personally working on a prototype, portable reader which should cost less than \$100.

John Higgins
via email

#2 A cheap and effective way to keep track of your inventory would be to label the inventory with barcodes. You can do this for free by downloading a barcode font from the several offered on the web. A search for "barcode font free" will locate these. Use any word processor with a label printing function to generate the inventory labels with your data, using the special barcode font for the barcodes. You can read the barcodes with a laser barcode scanner and "keyboard wedge," which you can find online by searching for "keyboard wedge barcode scanner." A "keyboard wedge" allows you to connect a barcode scanner inline with your keyboard. When a barcode is read, the wedge inserts the characters read into your inventory software, as if you had manually typed the characters on your keyboard. To use a keyboard wedge with a portable computer, use a "USB keyboard wedge scanner." You may use any inventory software that you wish, including free or shareware programs offered online, as no modifications need be made to the inventory software to use a wedge scanner. I looked at a few that might work for you that are freeware on [ZDNet](http://ZDNet.com) and download.com, simply searching for "inventory software." The

website at www.taltech.com/products/interface.htm has a good overview of complete barcode reading systems.

Howard Krausse
Willow Creek, CA

[#7093 - July 2009] **Simple Low Frequency Transmitter**

How would I build a low frequency (say 512 Hz), battery operated sine wave transmitter that was small enough to fit inside 1" PVC pipe? I'm not sure if a resistor, capacitor, or crystal is the best; how do you wind a coil antenna to match the frequency?

I sell a programmable Quad DDS chip that is very accurate in the audio range (512.00 Hz) and four outputs. It has a square wave output, but can be converted to triangle, then filtered to sine.

A 555 timer chip and a few other parts would be cheaper, but the freq will drift with temp change.

As far as the antenna goes, at that freq, just about any coil will work.

If you need a strong field, you can drive the coil with a cheap audio amp chip, like the LM386.

I can email you plans for most of this stuff; SteveMerrell@gmail.com

Steve
Tucson, AZ

[#8097 - August 2009] **Need LCD Datasheets**

I'm looking for datasheets or advice on how to use an LCD unit salvaged from a mid 1980's medical device. The PCB is labeled "PWB641C-CEM, OPTREX." There are 19 pins, two of which are "A" and "K" which I believe to be power for the backlight. The chips are "HD44105H" and two "HD44102CH."

Anyone can type ANY CHIP ID directly into any search engine and get information from many sources.

The 'link' below will give you the 'HD44102CH' chip.

<http://pdf1.alldatasheet.co.kr/datasheet-pdf/view/169419/HITACHI/HD44102CH.html>

John Mastromoro
Saint Johnsville, NY

**AMATEUR
RADIO AND TV**

Ramsey Electronics, Inc.26-27
Startek International33

**BATTERIES/
CHARGERS**

Cunard Associates33

**BUYING ELECTRONIC
SURPLUS**

Earth Computer Technologies33
HSC Electronic Supply3
Jaycar Electronics.....43

**CCD CAMERAS/
VIDEO**

Circuit Specialists, Inc.82-83
Ramsey Electronics, Inc.26-27

CIRCUIT BOARDS

AP Circuits60
Cunard Associates33
Dimension Engineering.....30
ExpressPCB39
Futurlec65
PCB Core8
PCB Pool25
Saelig Company, Inc.12

COMPONENTS

Cana Kit Corp.31
Electronix Express71
Front Panel Express LLC.....60
Fun Gizmos33
Futurlec65
HSC Electronic Supply3
Jameco4
Linx Technologies25
Mouser Electronics13

COMPUTER

Hardware
ActiveWire, Inc.33
Earth Computer Technologies33

Microcontrollers / I/O Boards

Abacom Technologies18
Fun Gizmos33
HobbyLab33
microEngineering Labs54
Mouser Electronics13
Net Media2

Parallax, Inc.Back Cover
Pololu Robotics & Electronics42
Solarbotics/HVW9
Technological Arts33
Trace Systems, Inc.9
XGameStation33

**DESIGN/
ENGINEERING/
REPAIR SERVICES**

Cana Kit Corp.31
Edsyn23
ExpressPCB39
Front Panel Express LLC.....60
PCB Pool25
Trace Systems, Inc.9

EDUCATION

Command Productions19
LearnOnLine, Inc.23
PAiA18
Technological Arts33
XGameStation33

EMBEDDED TOOLS

Mouser Electronics13
NetBurner7

ENCLOSURES

Integrated Ideas & Tech.38
Front Panel Express LLC.....60

KITS & PLANS

Cana Kit Corp.31
DesignNotes.com, Inc.33
Earth Computer Technologies33
Jaycar Electronics.....43
NetBurner7
PAiA18
QKITS33
Ramsey Electronics, Inc.26-27
Solarbotics/HVW9
XGameStation33

MISC./SURPLUS

All Electronics Corp.55
Front Panel Express LLC.....60
HSC Electronic Supply3
Surplus Gizmos24

MOTORS

Jameco4

PROGRAMMERS

Futurlec65
microEngineering Labs54
**RF TRANSMITTERS/
RECEIVERS**
Abacom Technologies18
Linx Technologies25

ROBOTICS

Budget Robotics32
Fun Gizmos33
HobbyLab33
Jameco4
Lemos International Co., Inc.19
Lynxmotion, Inc.25
Net Media2
Pololu Robotics & Electronics42
Solarbotics/HVW9

SATELLITE

Lemos International Co., Inc.19

SECURITY

Technological Arts33

SOLAR ENERGY

LearnOnLine, Inc.23

TEST EQUIPMENT

Circuit Specialists, Inc.82-83
DesignNotes.com, Inc.33
Dimension Engineering.....30
Edsyn23
HobbyLab33
Jaycar Electronics.....43
LeCroy5
Pioneer Hill Software12
Saelig Company, Inc.12
Startek International33
Trace Systems, Inc.9

TOOLS

Edsyn23
NetBurner7

VIDEO DISPLAY

Decade Engineering33

**WIRE, CABLE
AND CONNECTORS**

DesignNotes.com, Inc.33
Jameco4

Abacom Technologies18
ActiveWire, Inc.33
All Electronics Corp.55
AP Circuits60
Budget Robotics32
Cana Kit Corp.31
Circuit Specialists, Inc.82-83
Command Productions19
Cunard Associates33
Decade Engineering33
DesignNotes.com, Inc.33
Dimension Engineering.....30
Earth Computer Technologies ..33
Edsyn23
Electronix Express71
ExpressPCB39
Front Panel Express LLC.....60
Fun Gizmos33
Futurlec65
HobbyLab33
HSC Electronic Supply3
Integrated Ideas & Tech.38
Jameco4
Jaycar Electronics.....43
LearnOnLine, Inc.23
LeCroy5
Lemos International Co., Inc.19
Linx Technologies25
Lynxmotion, Inc.25
microEngineering Labs54
Mouser Electronics13
NetBurner7
Net Media2
PAiA18
Parallax, Inc.Back Cover
PCB Core8
PCB Pool25
Pioneer Hill Software12
Pololu Robotics & Electronics42
QKITS33
Ramsey Electronics, Inc.26-27
Saelig Company, Inc.12
Solarbotics/HVW9
Startek International33
Surplus Gizmos24
Technological Arts33
Trace Systems, Inc.9
XGameStation33



ESD Safe SMD & Thru-Hole Rework Station



A GREAT VALUE on an SMD/solder station combo
INCLUDES THREE NOZZLES!

An SMT rework station & soldering station in one handy unit! Perfect for shops & labs dealing with today's SMT board designs. OEM manufactured just for Circuit Specialists Inc., so we can offer the best price possible! This multi-purpose station is perfect for all your surface mount and thru-hole requirements. The ESD safe soldering iron uses a ceramic heating element for fast heat up & stable temperature control. A separate aluminum constructed soldering iron holder is included (not shown in picture) The comfort grip handle make it easy to use all day, while the easy-off connector make it convenient to move out of the way when not using, or easy to replace if needed. The temperature is controlled by a centrally located knob. The hot air soldering is controlled by two adjustable knobs which allow you to achieve a temperature range from 100°C to 500°C / 212°F to 932°F. One knob is for air flow, the other for the temperature. Comes complete with 3 hot air nozzles. You get a 2.5mm, (straight single, item # A1124), 4.4mm (straight single, item # A1130), and a 9.0mm nozzle (straight single, item # A1197). This is a fantastic value!



Item # CSI906

\$99.00

ESD Safe, CPU Controlled, SMD Hot Air Rework Station



What every shop or lab needs to deal with today's SMD designed circuit boards. OEM manufactured just for Circuit Specialists Inc., so we can offer the best price possible! A multi-technology assembly and repair station. A wide selection of nozzles are also available.

- CPU Controlled
- Built-in vacuum parts handling wand
- Air Pump: Diaphragm special-purpose lathe pump
- Capability: 23L/min (Max)
- Temperature Range: 100°C-480°C/212°F-896°F
- 15-Minute Stand-By temperature "sleep" mode
- Power: 110/120 VAC, 320 W maximum

Item #
CSI825A++

\$99.00



One Dollar Upgrade !!

Wow! Now that's a lot for only a Dollar more!!

You get the CSI2205D DMM pre-fitted into our 45-1 Protective Case for only one dollar more than the price of the CSI2205D alone.

The CSI2205D Micro Control Unit auto-ranging DMM is designed for measuring resistance, capacitance, DC &

True RMS AC voltage, DC & True RMS AC current, frequency, duty cycle and temperature, along with the ability to test diodes, transistors and continuity.

Regular Price \$59.00



The 45-1 case is ideal for transporting small electronics & other delicate items.

Regular Price \$29.00

\$88.00 if purchased Separately!
Save \$28.00!!!

Item# CSI2205D-BUNDLE

\$60.00

Aardvark

Wireless Inspection Camera
With Color 3.5" LCD Recordable Monitor
Your Extended Eyes & Hands!



RECORDS
Still Pictures
& Video

See It!

Clearly in narrow spots,
even in total darkness or
underwater.

Find It!

Fast. No more struggling
with a mirror & flash light.

Solve It!

Easily, speed up the solution
with extended accessories.

Record It!

With the 3.5" LCD recordable monitor, you can capture pictures or record video for documentation.

Full specifications at
www.CircuitSpecialists.com



The Aardvark Wireless Inspection Camera is a video borescope with a 3.5 inch color LCD monitor and a 3ft flexible shaft. The flexible shaft makes the Aardvark great for inspecting hard to reach or confined areas like sink drains, AC Vents, engine compartments or anywhere space is limited. The monitor is wireless and may be separated from the main unit for ease of operation. Still pictures or video can also be recorded and stored on a 2GB MicroSD card (included). The Aardvark comes with attachable mirror, magnet and hook accessories to make seeing or retrieving small items easier. The Aardvark's monitor also has connections for composite video output for a larger monitor/recorder and USB interface for computer connection. Also included is an AC adapter/charger, video cable and USB cable. Optional 3 ft flexible extensions are available to extend the Aardvark's reach (Up to 5 may be added for a total reach of 18 feet!).



Item #
AARDVARK

\$229.00

3ft Extension AARDVARK-EXT \$24.95

60MHz Hand Held Scopemeter with Oscilloscope & DMM Functions

Who Says

*you can't take it with you?
With the DSO1060 YOU CAN!*



- 60MHz Handheld Digital Scopemeter with integrated Digital Multimeter Support
- 60MHz Bandwidth with 2 Channels
- 150MSa/s Real-Time Sampling Rate
- 50Gs/s Equivalent-Time Sampling Rate
- 6,000-Count DMM resolution with AC/DC at 600V/800V, 10A
- Large 5.7 inch TFT Color LCD Display
- USB Host/Device 2.0 full-speed interface connectivity
- Multi Language Support
- Battery Power Operation (Installed)

Item #
DSO1060



\$549.00

34 Channel USB Logic Analyzer

The CS15034 is a sophisticated, portable, and easy-to-use 500MHz, 34-channel logic analyzer equipped with features found only in more expensive bench type instruments. Using advanced large-scale integrated circuits, integrated USB 2.0, CPLD, FPGA, high-frequency digital circuitry, embedded systems, and other advanced technology, make the CS15034 your best choice in pc-based logic analyzers. The CS15034

is suitable for electronic measurement engineers, college students in scientific research and development and teaching assistants.


- 34 input channels capable of simultaneously monitoring data and control information, and is capable of capturing narrow pulses and glitches that may be missed by other test equipment.
- Delay feature provides the ability to capture data around the waveform, both before and after the desired trigger signal. This allows the operator to view the data at multiple points in the data stream.
- Memory feature stores multiple data points for error analysis of the unit under test and to aid in locating defective components.
- Intuitive and flexible viewing screens to facilitate analysis of the system under test. Data can be displayed as binary, decimal, or hexadecimal values.
- Can be triggered in a variety of ways (rising edge, falling, edge or both), and also has an advanced trigger function that allows logic operations to be performed on the data before a trigger is generated. This provides the ability to trigger on a specific data byte or word from any of the monitored channels.



Item #
CS15034

\$329.00

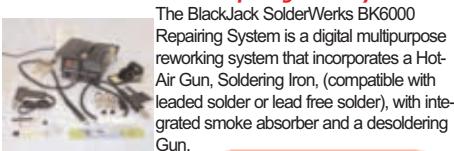
Premium All-In-One Repairing Solder System



Item# **BK6000**

\$199.00

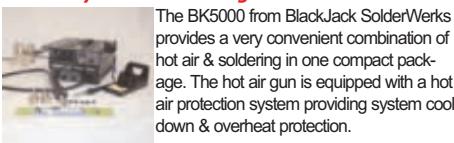
Hot Air System w/ Soldering Iron & Mechanical Arm



Item# **BK5000**

\$119.00

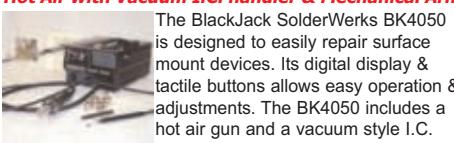
Hot Air with Vacuum I.C. Handler & Mechanical Arm



Item# **BK4050**

\$119.00

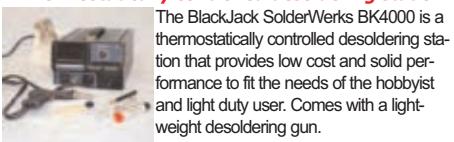
Thermostatically controlled desoldering station



Item# **BK4000**

\$119.00

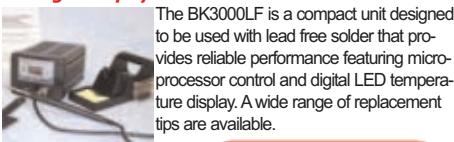
Digital Display Solder Station for Lead Free Solder



Item# **BK3000LF**

\$74.95


Compact Digital Display Solder Station

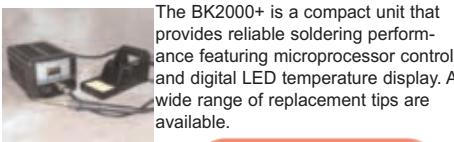

Item# **BK2000+**

\$56.95

Compact Soldering Station

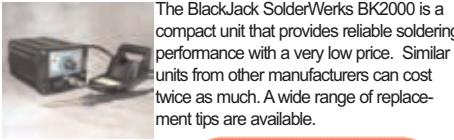

Item# **BK2000**

\$36.95

Close Focus Small Spot Size Infrared Thermometer TN01U

Featuring spot-on, dual-laser aiming, the TN01U close-focus, non-contact IR thermometer measures the temperature of electronic components as small as 0.1-in. with pin-point accuracy. Compact and lightweight, the instrument provides a large LCD and a bright dual-laser aiming system that allows for accurate aiming. Features include a measurement spot size of 2.5-mm in diameter at distances up to 18 mm, measurement range from -55°C to +220°C, (-67-428 deg F) an accuracy of $\pm 2\%$ of reading or $\pm 2^\circ\text{C}$ whichever is greater, a repeatability of $\pm 0.2^\circ\text{C}$, display resolution of 0.1°C, and a response time of 1s. Operating with two AAA batteries providing 18 hours of continuous use, the instrument measures. This is the most advanced infrared thermometer manufactured today providing fast, accurate, non-contact component temperature measurements for hardware designers, Test, QA and Service professionals.

Item # **TN01U**

\$129.00

CircuitSpecialists.com
1000's of Items Online!
1-800-528-1417
Fax: 480-464-5824
Since 1971



Dual Output DC Bench Power Supplies

High stability digital read-out bench power supplies featuring constant voltage & current outputs. Short-circuit & current limiting protection is provided. SMT PC boards and a built-in cooling fan help ensure reliable performance & long life. All 3 Models have a 1A/5VDC Fixed Output on the rear panel.



Item #:	Price 1-4	Price 5+
CSI3003X-5 0-30V/0-3A	\$119.00	\$112.00
CSI5003X5 0-50V/0-3A	\$127.00	\$119.00
CSI3005X5 0-30V/0-5A	\$129.00	\$122.00

Temperature Controlled Reflow Oven

The HHL3000 Reflow Oven is a highly versatile tool used for reflowing and preheating different surface Mount technology (SMT) components and printed circuit boards (PCB's). The system utilizes a microcontroller to effectively and efficiently manage the working temperature while facilitating the duration of the heating process. A bright LED display clearly displays the time and temperature along with a fully digital control panel for ease of use and monitoring.

The HHL3000 makes use of infrared (IR) heat wave technology to distribute heat evenly on the component and PCB. Included is an integrated temperature sensor that allows positioning in such a way that the measurement of the actual temperature of PCB and components can be obtained. This minimizes damage to the PCB and its components due to thermal shock or low level temperature conditions.


FUNCTIONS and FEATURES

- * Microprocessor-controlled equipment.
- * Direct PCB temperature measurement, improves accuracy and lessens damage or distortion.
- * Five (5) temperature and time control points with automatic slope adjustment. Configurable to suit different solder paste and circuit boards.
- * Two (2) default profiles suitable with most common solder paste specifications.
- * Quick and easy resetting of control points for precise tuning of reflow profiles.
- * Built-in safety feature of industry standard 0.01°C/s to 3°C/s rising slope.
- * Fully digital panel controls and readout of time and temperature for monitoring and ease of use.
- * Highly compatible with lead-free applications.

Item# **HHL3000**

\$949.00

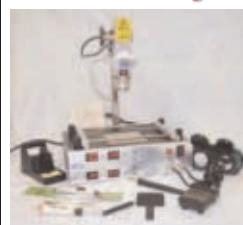3 in 1 FOCUSED Infrared Soldering/Repair System



The CSI720 Three in One Focused Infrared Welding System generates heat through a concentrated infrared heat wave, providing precise soldering without movement of surrounding components.

ESD Safe, Focused Infrared Welding Station

For reworking BGAs, micro BGAs, QFPs, PLCCs, SOICs, small SMD and other circuit board components. Unit produces a concentrated infrared heat wave, for precision soldering. Infrared soldering eliminates movement of surrounding components, and marks on reworked PCBs, both associated with standard hot air reworking.

3 in 1 Repairing System Combines the function of an Infrared Welding Tool, Soldering Iron and Pre-heater.

Full Digital Control with LED Displays Allows precision setting of welding temperature & time, soldering iron and pre-heating temperatures.

Closed loop temperature control For instant and precise process adjustments.

Adjustable Infrared Tool Post Stable and adjustable Infrared welding tool holder for increased precision soldering and hands free operation.

Adjustable Eye shield & Welding Goggles To protect users from harmful light rays.

Uses infrared heat wave technology instead of the conventional hot air, effectively solves the major problem being encountered when using the hot air gun, which is the movement of surrounding components while reworking.

Item # **CSI720**

\$1,399.99

Triple Output DC Bench Power Supplies

•Output: 0-30VDC x 2 @ 3

or 5 Amps & 1fixed output

@ 5VDC@3A

•Stepped Current:

30mA +/- 1mA



Item #:	Price 1-4	Price 5+
CSI3003X3 0-30Vx2@3A	\$198.00	\$193.00
CSI3005XIII 0-30Vx2@5A	\$259.00	\$244.00

New Products!



Say It Module (#30080; \$79.99) Provides voice recognition for built-in pre-programmed commands or up to 32 user defined commands. Good for robots, home automation, etc. GUI software for the BASIC Stamp®2 microcontroller and example code for the Boe-Bot® is available.



Propeller Servo Controller USB (#28830; \$39.99) Control up to 16 servos (32 servos with 2 controllers) with this network-ready module. Propeller-based and open-source.



P8X32A-Q44 Schmartboard Kit (#27150; \$39.99)

Learn surface-mount soldering and then program on this convenient development platform for the multicore Propeller chip. Kit includes surface-mount and through-hole package options for select components.



7.2 V Motor, Bracket and Wheel Kit (#570-00070; \$99.99) Lightweight and sturdy aluminum brackets specifically designed to make mounting the included all-metal 7.2 VDC motors a breeze. Giving your robot rugged mobility has never been easier!



433 MHz RF Transceiver (#27982; \$39.99) Send serial data wirelessly between microcontrollers or to a PC. The low power consumption makes this module ideal for use in battery powered applications. Line of sight range up to 2500 feet (depending on operating conditions).



MMA7455 3-Axis Accelerometer Module (#28526; \$34.99)

This low-power sensor measures acceleration along its X, Y, and Z axes. Module has wide supply voltage compatibility range (2.2 - 5.5 V), selectable sensitivity ($\pm 2g$, $\pm 4g$, $\pm 8g$), user-configurable interrupts, and user-settable registers to calibrate each axis.

To see all the new products visit www.parallax.com
Order online or call our Sales Department toll-free at
888-512-1024 (Monday-Friday, 7 a.m. - 5 p.m., PT).

Prices subject to change without notice. BASIC Stamp and Boe-Bot are registered trademarks of Parallax Inc. Propeller, Parallax, and the Parallax logo are trademarks of Parallax Inc.

PARALLAX www.parallax.com
Friendly microcontrollers, legendary resources.